

Chapter 1

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris


FROM ZERO TO ONE
FROM ZERO TO ONE

Chapter 1 :: Topics

- **Background**
- **The Game Plan**
- **The Art of Managing Complexity**
- **The Digital Abstraction**
- **Number Systems**
- **Logic Gates**
- **Logic Levels**
- **CMOS Transistors**
- **Power Consumption**

Background

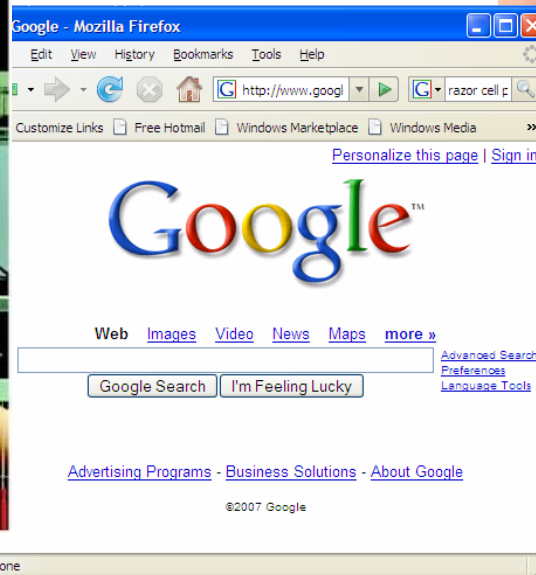- Microprocessors have revolutionized our world
 - Cell phones, Internet, rapid advances in medicine, etc.
- The semiconductor industry has grown from \$21 billion in 1985 to \$300 billion in 2011



FROM ZERO TO ONE
FROM ZERO TO ONE

The Game Plan

- Purpose of course:
 - Understand what's under the hood of a computer
 - Learn the principles of digital design
 - Learn to systematically debug increasingly complex designs
 - Design and build a microprocessor


The Art of Managing Complexity

- Abstraction
- Discipline
- The Three –y's
 - Hierarchy
 - Modularity
 - Regularity

FROM ZERO TO ONE
FROM ZERO TO ONE

Abstraction

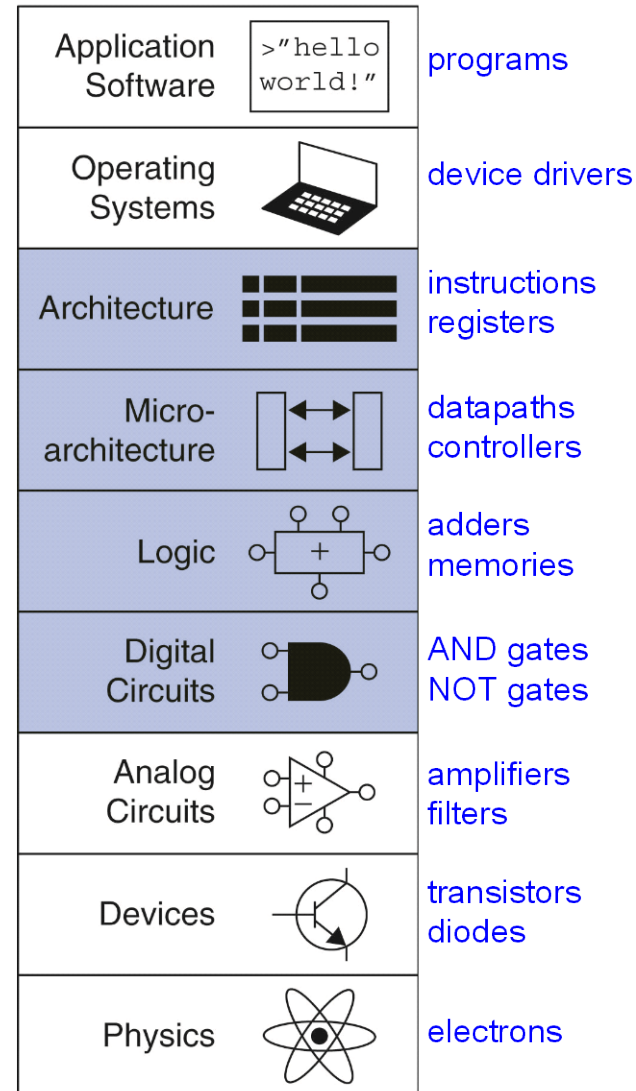- Hiding details when they aren't important



Discipline

- Intentionally restrict design choices
- Example: Digital discipline
 - Discrete voltages instead of continuous
 - Simpler to design than analog circuits – can build more sophisticated systems
 - Digital systems replacing analog predecessors:
 - i.e., digital cameras, digital television, cell phones, CDs

The Three -y's

- **Hierarchy**
- **Modularity**
- **Regularity**


The Three -y's

- **Hierarchy**
 - A system divided into modules and submodules
- **Modularity**
 - Having well-defined functions and interfaces
- **Regularity**
 - Encouraging uniformity, so modules can be easily reused

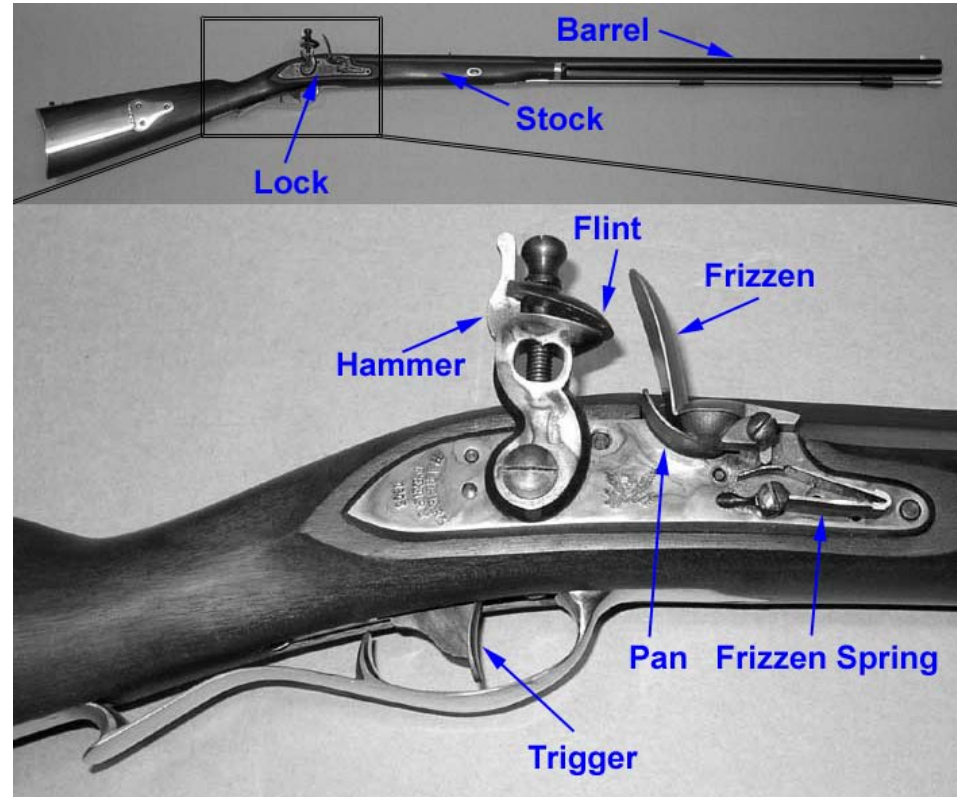Example: The Flintlock Rifle

- **Hierarchy**


- **Three main modules:** lock, stock, and barrel
- **Submodules of lock:** hammer, flint, frizzen, etc.



FROM ZERO TO ONE
FROM ZERO TO ONE

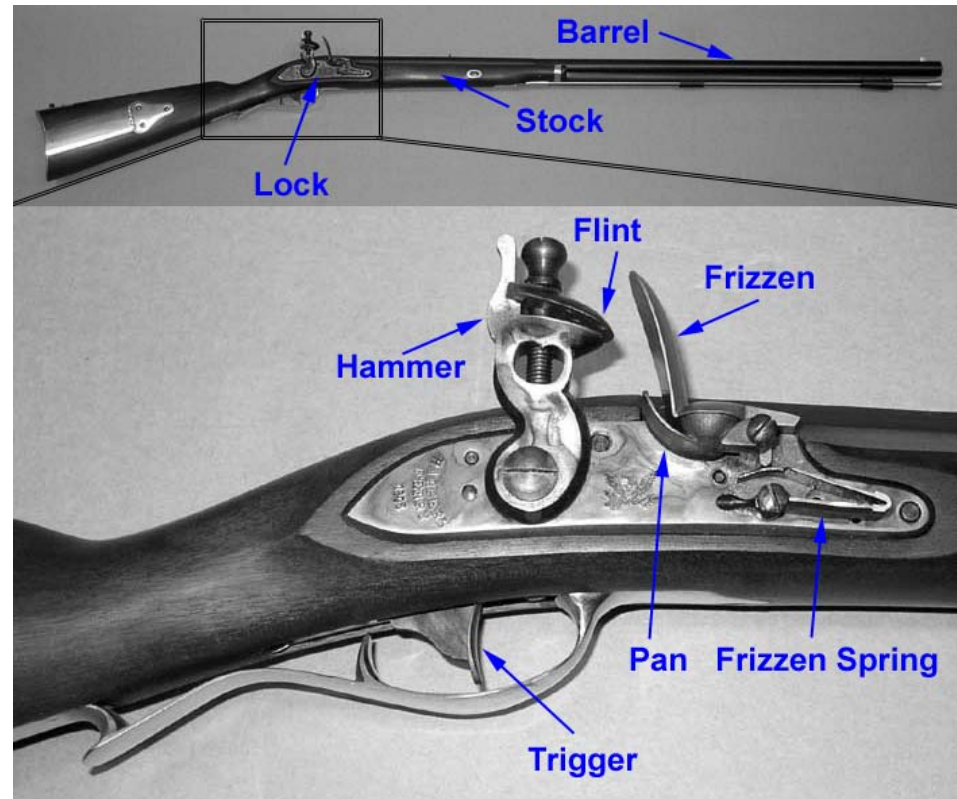Example: The Flintlock Rifle

- **Modularity**
 - **Function of stock:** mount barrel and lock
 - **Interface of stock:** length and location of mounting pins
- **Regularity**
 - Interchangeable parts




The Digital Abstraction

- Most physical variables are **continuous**
 - Voltage on a wire
 - Frequency of an oscillation
 - Position of a mass
- Digital abstraction considers **discrete subset** of values

The Analytical Engine

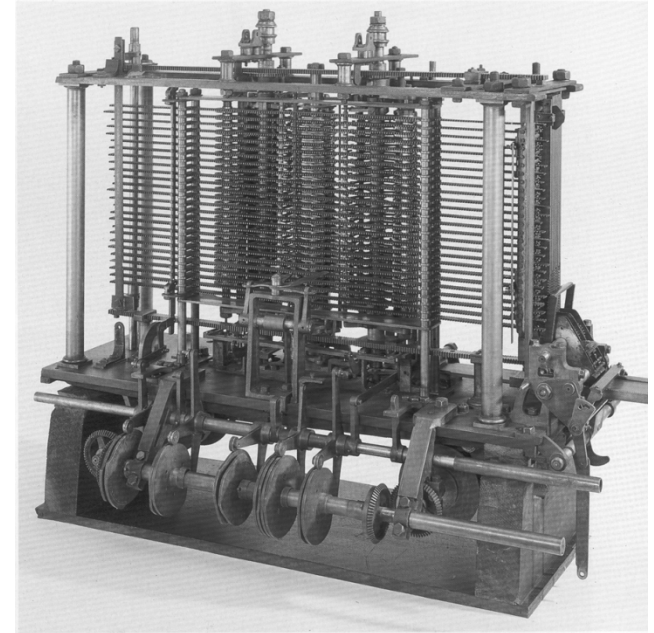- Designed by Charles Babbage from 1834 – 1871
- Considered to be the first digital computer
- Built from mechanical gears, where each gear represented a discrete value (0-9)
- Babbage died before it was finished




Digital Discipline: Binary Values

- **Two discrete values:**
 - 1's and 0's
 - 1, TRUE, HIGH
 - 0, FALSE, LOW
- **1 and 0:** voltage levels, rotating gears, fluid levels, etc.
- Digital circuits use **voltage** levels to represent 1 and 0
- ***Bit:*** Binary digit

George Boole, 1815-1864

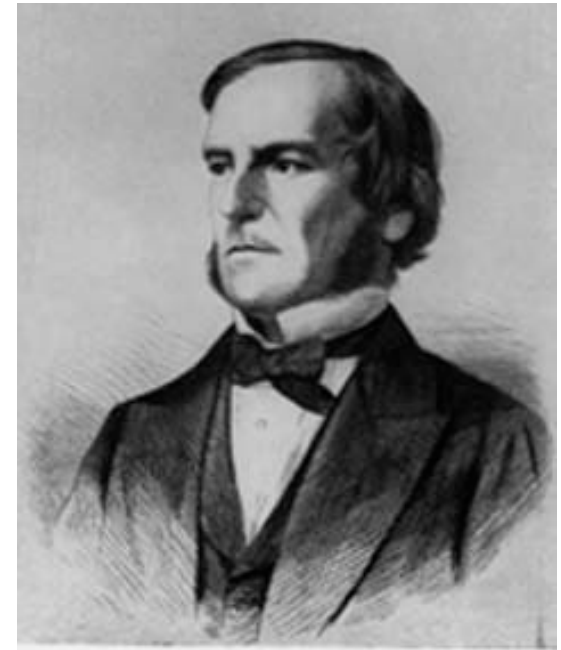- Born to working class parents
- Taught himself mathematics and joined the faculty of Queen's College in Ireland
- Wrote *An Investigation of the Laws of Thought* (1854)
- Introduced binary variables
- Introduced the three fundamental logic operations: AND, OR, and NOT



GEORGE BOOLE

Scanned at the American
Institute of Physics

Number Systems

- Decimal numbers

1's column
10's column
100's column
1000's column

$$5374_{10} =$$

- Binary numbers

1's column
2's column
4's column
8's column

$$1101_2 =$$

Number Systems

- Decimal numbers

1's column
10's column
100's column
1000's column

$$5374_{10} = 5 \times 10^3 + 3 \times 10^2 + 7 \times 10^1 + 4 \times 10^0$$

five three seven four
thousands hundreds tens ones

- Binary numbers

1's column
2's column
4's column
8's column

$$1101_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 13_{10}$$

one one no one
eight four two one

Powers of Two

- $2^0 =$

- $2^1 =$

- $2^2 =$

- $2^3 =$

- $2^4 =$

- $2^5 =$

- $2^6 =$

- $2^7 =$

- $2^8 =$

- $2^9 =$

- $2^{10} =$

- $2^{11} =$

- $2^{12} =$

- $2^{13} =$

- $2^{14} =$

- $2^{15} =$

Powers of Two

- $2^0 = 1$
- $2^1 = 2$
- $2^2 = 4$
- $2^3 = 8$
- $2^4 = 16$
- $2^5 = 32$
- $2^6 = 64$
- $2^7 = 128$
- $2^8 = 256$
- $2^9 = 512$
- $2^{10} = 1024$
- $2^{11} = 2048$
- $2^{12} = 4096$
- $2^{13} = 8192$
- $2^{14} = 16384$
- $2^{15} = 32768$
- Handy to memorize up to 2^9

Number Conversion

- Decimal to binary conversion:
 - Convert 10011_2 to decimal

- Decimal to binary conversion:
 - Convert 47_{10} to binary

Number Conversion

- Decimal to binary conversion:
 - Convert 10011_2 to decimal
 - $16 \times 1 + 8 \times 0 + 4 \times 0 + 2 \times 1 + 1 \times 1 = 19_{10}$
- Decimal to binary conversion:
 - Convert 47_{10} to binary
 - $32 \times 1 + 16 \times 0 + 8 \times 1 + 4 \times 1 + 2 \times 1 + 1 \times 1 = 101111_2$

Binary Values and Range

- N -digit decimal number
 - How many values?
 - Range?
 - Example: 3-digit decimal number:
- N -bit binary number
 - How many values?
 - Range:
 - Example: 3-digit binary number:

Binary Values and Range

- N -digit decimal number
 - How many values? 10^N
 - Range? $[0, 10^N - 1]$
 - Example: 3-digit decimal number:
 - $10^3 = 1000$ possible values
 - Range: $[0, 999]$
- N -bit binary number
 - How many values? 2^N
 - Range: $[0, 2^N - 1]$
 - Example: 3-digit binary number:
 - $2^3 = 8$ possible values
 - Range: $[0, 7] = [000_2 \text{ to } 111_2]$

Hexadecimal Numbers

FROM ZERO TO ONE
FROM ZERO TO ONE

Hex Digit	Decimal Equivalent	Binary Equivalent
0	0	
1	1	
2	2	
3	3	
4	4	
5	5	
6	6	
7	7	
8	8	
9	9	
A	10	
B	11	
C	12	
D	13	
E	14	
F	15	

Hexadecimal Numbers

FROM ZERO TO ONE
FROM ZERO TO ONE

Hex Digit	Decimal Equivalent	Binary Equivalent
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111



Hexadecimal Numbers

- Base 16
- Shorthand for binary

Hexadecimal to Binary Conversion

- Hexadecimal to binary conversion:
 - Convert $4AF_{16}$ (also written $0x4AF$) to binary
- Hexadecimal to decimal conversion:
 - Convert $0x4AF$ to decimal

Hexadecimal to Binary Conversion

- Hexadecimal to binary conversion:
 - Convert $4AF_{16}$ (also written $0x4AF$) to binary
 - $0100\ 1010\ 1111_2$
- Hexadecimal to decimal conversion:
 - Convert $4AF_{16}$ to decimal
 - $16^2 \times 4 + 16^1 \times 10 + 16^0 \times 15 = 1199_{10}$

Bits, Bytes, Nibbles...

- Bits

10010110
└─┬─┘ └─┬─┘
most least
significant significant
bit bit

- Bytes & Nibbles

byte
┌───────────┐
10010110
└─────────┘
nibble

- Bytes

CEBF9AD7
└─┬─┘ └─┬─┘
most least
significant significant
byte byte

Large Powers of Two

- $2^{10} = 1 \text{ kilo} \approx 1000 \text{ (1024)}$
- $2^{20} = 1 \text{ mega} \approx 1 \text{ million (1,048,576)}$
- $2^{30} = 1 \text{ giga} \approx 1 \text{ billion (1,073,741,824)}$

Estimating Powers of Two

- What is the value of 2^{24} ?
- How many values can a 32-bit variable represent?

Estimating Powers of Two

- What is the value of 2^{24} ?

$$2^4 \times 2^{20} \approx \mathbf{16 \text{ million}}$$

- How many values can a 32-bit variable represent?

$$2^2 \times 2^{30} \approx \mathbf{4 \text{ billion}}$$

Addition

- Decimal

$$\begin{array}{r} 3734 \\ + 5168 \\ \hline \end{array}$$

- Binary

$$\begin{array}{r} 1011 \\ + 0011 \\ \hline \end{array}$$

Addition

- Decimal

$$\begin{array}{r} 11 \leftarrow \text{carries} \\ 3734 \\ + 5168 \\ \hline 8902 \end{array}$$

- Binary

$$\begin{array}{r} 11 \leftarrow \text{carries} \\ 1011 \\ + 0011 \\ \hline 1110 \end{array}$$

Binary Addition Examples

- Add the following 4-bit binary numbers

$$\begin{array}{r} 1001 \\ + 0101 \\ \hline \end{array}$$

- Add the following 4-bit binary numbers

$$\begin{array}{r} 1011 \\ + 0110 \\ \hline \end{array}$$

Binary Addition Examples

- Add the following 4-bit binary numbers

$$\begin{array}{r} 1 \\ 1001 \\ + 0101 \\ \hline 1110 \end{array}$$

- Add the following 4-bit binary numbers

$$\begin{array}{r} 111 \\ 1011 \\ + 0110 \\ \hline 10001 \end{array}$$

Overflow!

Overflow

- Digital systems operate on a **fixed number of bits**
- Overflow: when result is too big to fit in the available number of bits
- See previous example of $11 + 6$

Signed Binary Numbers

- Sign/Magnitude Numbers
- Two's Complement Numbers

FROM ZERO TO ONE
FROM ZERO TO ONE

Sign/Magnitude Numbers

- 1 sign bit, $N-1$ magnitude bits
- Sign bit is the most significant (left-most) bit
 - Positive number: sign bit = 0 $A : \{a_{N-1}, a_{N-2}, \dots, a_2, a_1, a_0\}$
 - Negative number: sign bit = 1 $A = (-1)^{a_{n-1}} \sum_{i=0}^{n-2} a_i 2^i$
- Example, 4-bit sign/mag representations of ± 6 :
 - +6 =
 - 6 =
- Range of an N -bit sign/magnitude number:

Sign/Magnitude Numbers

- 1 sign bit, $N-1$ magnitude bits
- Sign bit is the most significant (left-most) bit
 - Positive number: sign bit = 0 $A : \{a_{N-1}, a_{N-2}, \dots, a_2, a_1, a_0\}$
 - Negative number: sign bit = 1 $A = (-1)^{a_{n-1}} \sum_{i=0}^{n-2} a_i 2^i$
- Example, 4-bit sign/mag representations of ± 6 :
 - +6 = **0110**
 - 6 = **1110**
- Range of an N -bit sign/magnitude number:
 $[-(2^{N-1}-1), 2^{N-1}-1]$

Sign/Magnitude Numbers

- Problems:
 - Addition doesn't work, for example $-6 + 6$:

$$\begin{array}{r} 1110 \\ + 0110 \\ \hline 10100 \text{ (wrong!)} \end{array}$$

- Two representations of 0 (± 0):

1000

0000

Two's Complement Numbers

- Don't have same problems as sign/magnitude numbers:
 - Addition works
 - Single representation for 0

Two's Complement Numbers

- Msb has value of -2^{N-1}

$$A = a_{n-1} \left(-2^{n-1} \right) + \sum_{i=0}^{n-2} a_i 2^i$$

- Most positive 4-bit number:
- Most negative 4-bit number:
- The most significant bit still indicates the sign (1 = negative, 0 = positive)
- Range of an N -bit two's comp number:

Two's Complement Numbers

- Msb has value of -2^{N-1}

$$A = a_{n-1} \left(-2^{n-1} \right) + \sum_{i=0}^{n-2} a_i 2^i$$

- Most positive 4-bit number: **0111**
- Most negative 4-bit number: **1000**
- The most significant bit still indicates the sign (1 = negative, 0 = positive)
- Range of an N -bit two's comp number:

$$\left[-(2^{N-1}), 2^{N-1}-1 \right]$$

“Taking the Two’s Complement”

- Flip the sign of a two’s complement number
- Method:
 1. Invert the bits
 2. Add 1
- Example: Flip the sign of $3_{10} = 0011_2$

“Taking the Two’s Complement”

- Flip the sign of a two’s complement number
- Method:
 1. Invert the bits
 2. Add 1
- Example: Flip the sign of $3_{10} = 0011_2$

1. 1100

2. $\begin{array}{r} + 1 \\ \hline \end{array}$

$1101 = -3_{10}$

Two's Complement Examples

- Take the two's complement of $6_{10} = 0110_2$
- What is the decimal value of 1001_2 ?

Two's Complement Examples

- Take the two's complement of $6_{10} = 0110_2$

$$\begin{array}{r} 1. \ 1001 \\ 2. \ + \ 1 \\ \hline 1010_2 = -6_{10} \end{array}$$

- What is the decimal value of the two's complement number 1001_2 ?

$$\begin{array}{r} 1. \ 0110 \\ 2. \ + \ 1 \\ \hline 0111_2 = 7_{10}, \text{ so } 1001_2 = -7_{10} \end{array}$$

Two's Complement Addition

- Add $6 + (-6)$ using two's complement numbers

$$\begin{array}{r} 0110 \\ + 1010 \\ \hline \end{array}$$

- Add $-2 + 3$ using two's complement numbers

$$\begin{array}{r} 1110 \\ + 0011 \\ \hline \end{array}$$

Two's Complement Addition

- Add $6 + (-6)$ using two's complement numbers

$$\begin{array}{r} 111 \\ 0110 \\ + 1010 \\ \hline 10000 \end{array}$$

- Add $-2 + 3$ using two's complement numbers

$$\begin{array}{r} 111 \\ 1110 \\ + 0011 \\ \hline 10001 \end{array}$$

Sign-Extension

- Sign bit copied to msb's
- Number value is same

- **Example 1:**

- 4-bit representation of 3 = 0011
- 8-bit sign-extended value: 00000011


- **Example 2:**

- 4-bit representation of -5 = 1011
- 8-bit sign-extended value: 11111011

Number System Comparison

Number System	Range
Unsigned	$[0, 2^N-1]$
Sign/Magnitude	$[-(2^{N-1}-1), 2^{N-1}-1]$
Two's Complement	$[-2^{N-1}, 2^{N-1}-1]$

For example, 4-bit representation:

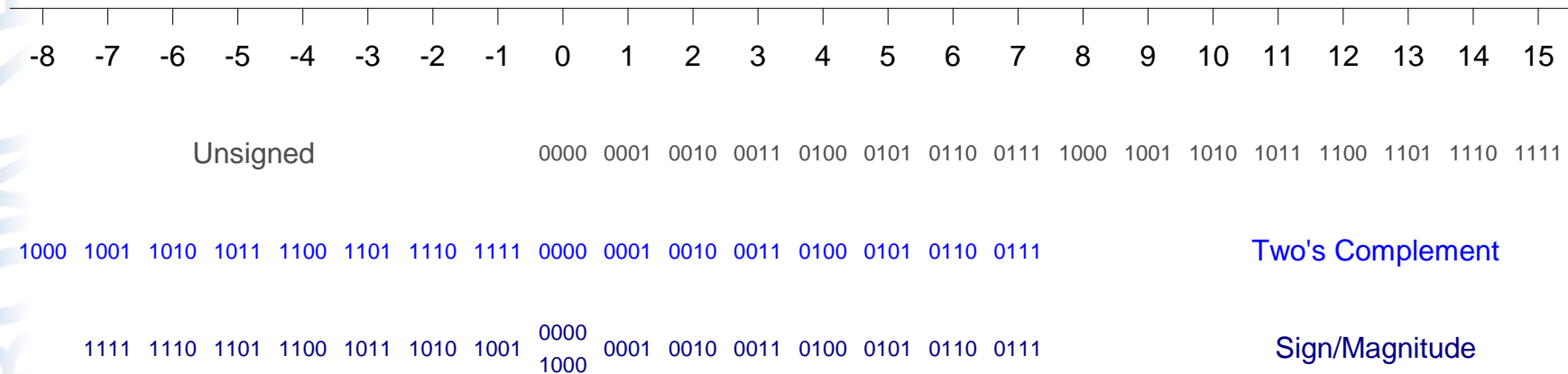


FROM ZERO TO ONE

Logic Gates

- **Perform logic functions:**
 - inversion (NOT), AND, OR, NAND, NOR, etc.
- **Single-input:**
 - NOT gate, buffer
- **Two-input:**
 - AND, OR, XOR, NAND, NOR, XNOR
- **Multiple-input**

Single-Input Logic Gates


NOT

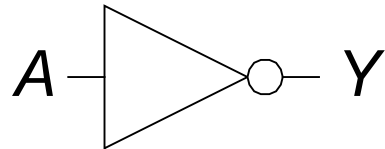

$$Y = \overline{A}$$

A	Y
0	1
1	0

BUF

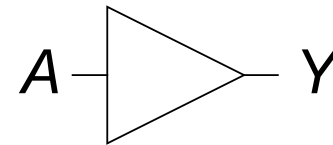


$$Y = A$$

A	Y
0	0
1	1

FROM ZERO TO ONE
FROM ZERO TO ONE

Single-Input Logic Gates


NOT

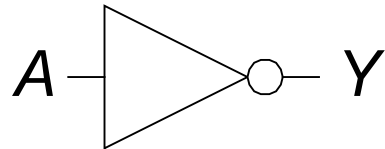

$$Y = \overline{A}$$

A	Y
0	1
1	0

BUF

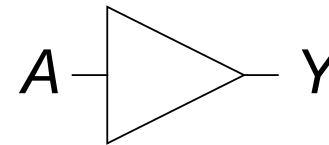


$$Y = A$$

A	Y
0	0
1	1

FROM ZERO TO ONE
FROM ZERO TO ONE

Two-Input Logic Gates


AND

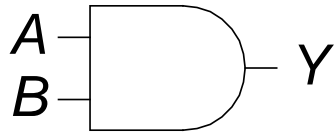

$$Y = AB$$

A	B	Y
0	0	
0	1	
1	0	
1	1	

OR

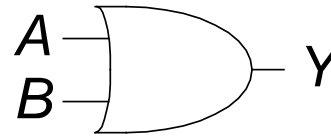


$$Y = A + B$$

A	B	Y
0	0	
0	1	
1	0	
1	1	

FROM ZERO TO ONE
FROM ZERO TO ONE

Two-Input Logic Gates


AND

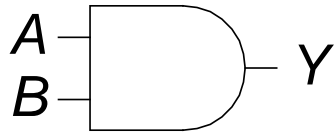

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR

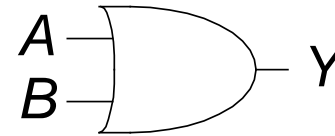


$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

FROM ZERO TO ONE
FROM ZERO TO ONE

More Two-Input Logic Gates


XOR

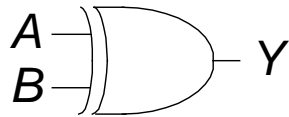

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


NAND

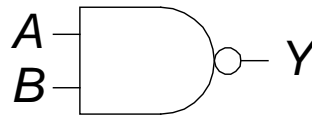

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR

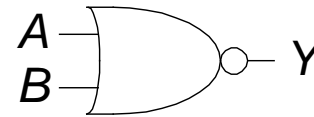

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

XNOR

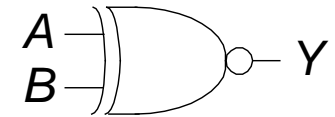


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

More Two-Input Logic Gates


XOR

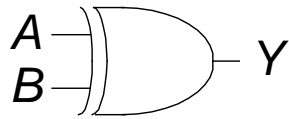

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


NAND

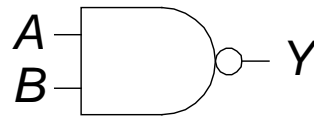

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR

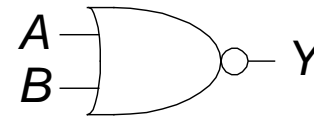

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

XNOR

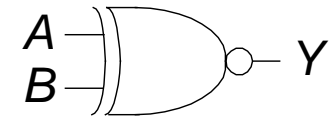


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Multiple-Input Logic Gates


NOR3

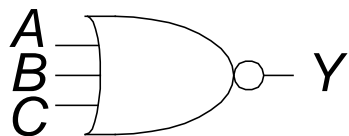

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

AND3

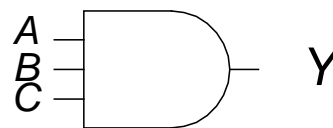


$$Y = ABC$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Multiple-Input Logic Gates


NOR3

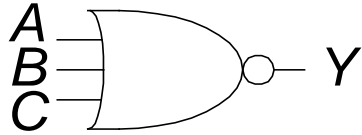

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

AND3

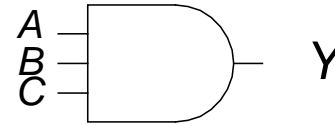

$$Y = ABC$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

- Multi-input XOR: Odd parity

FROM ZERO TO ONE
FROM ZERO TO ONE

Logic Levels

- Discrete voltages represent 1 and 0
- For example:
 - 0 = *ground* (GND) or 0 volts
 - 1 = V_{DD} or 5 volts
- What about 4.99 volts? Is that a 0 or a 1?
- What about 3.2 volts?

Logic Levels

- *Range* of voltages for 1 and 0
- Different ranges for inputs and outputs to allow for *noise*


What is Noise?

FROM ZERO TO ONE
FROM ZERO TO ONE



What is Noise?

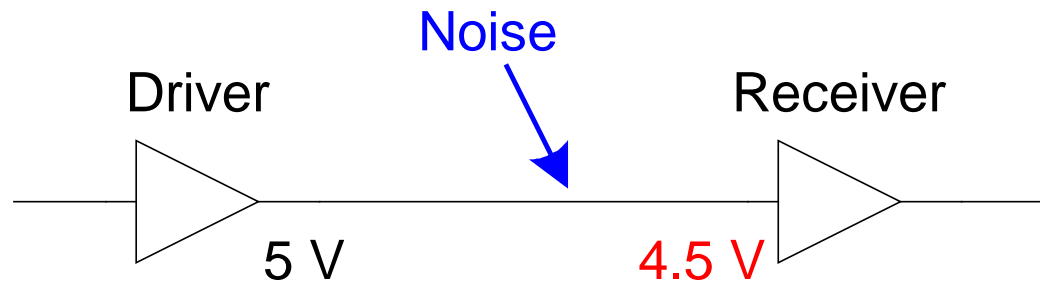- **Anything that degrades the signal**
 - E.g., resistance, power supply noise, coupling to neighboring wires, etc.
- **Example:** a gate (driver) outputs 5 V but, because of resistance in a long wire, receiver gets 4.5 V




The Static Discipline

- With logically valid inputs, every circuit element must produce logically valid outputs
- Use limited ranges of voltages to represent discrete values

Noise Margins

FROM ZERO TO ONE
FROM ZERO TO ONE

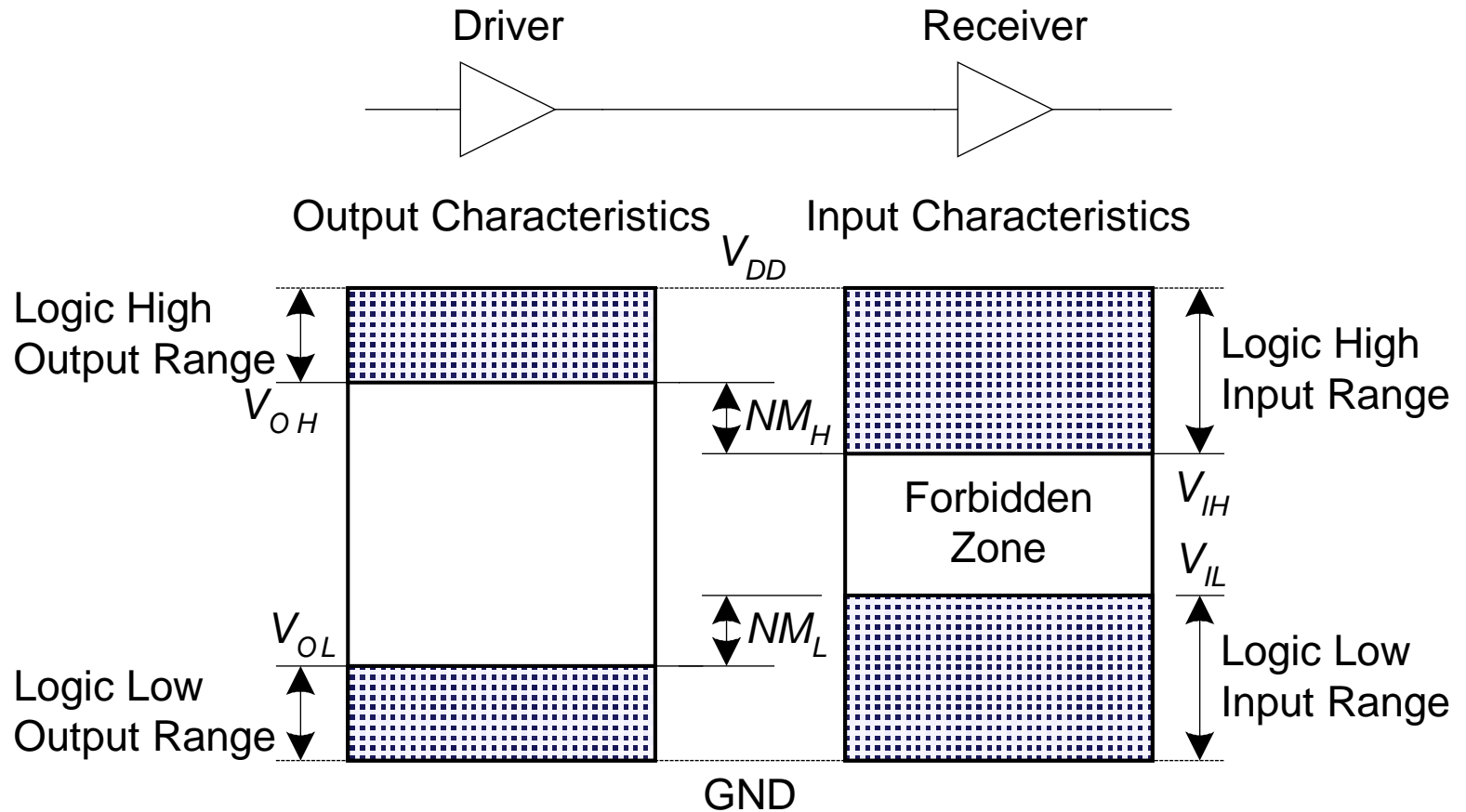


$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$


DC Transfer Characteristics

Ideal Buffer:

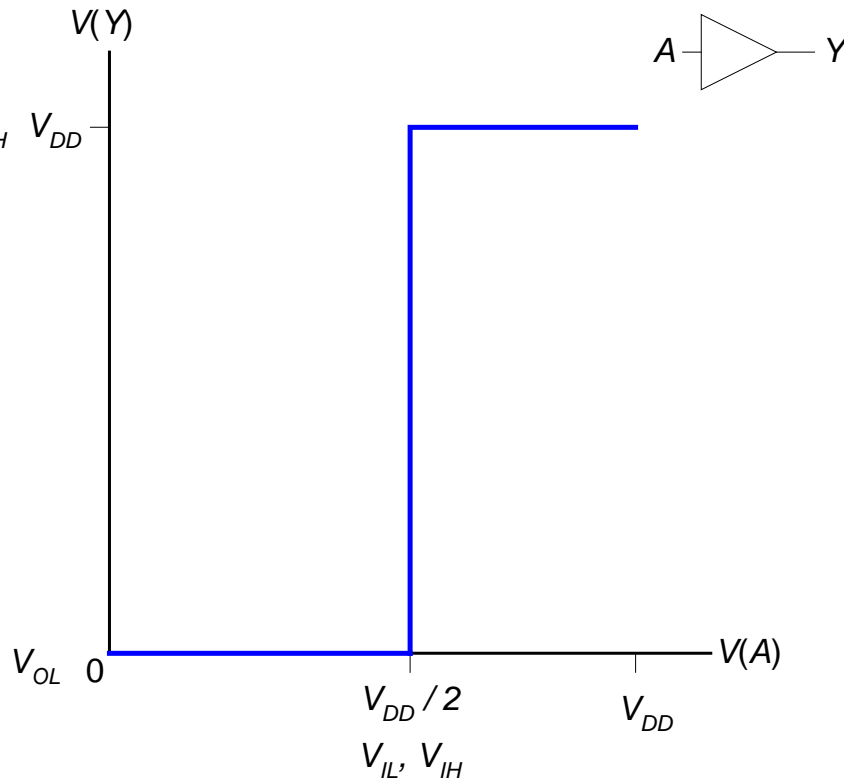

$$NM_H = NM_L = V_{DD}/2$$




Real Buffer:

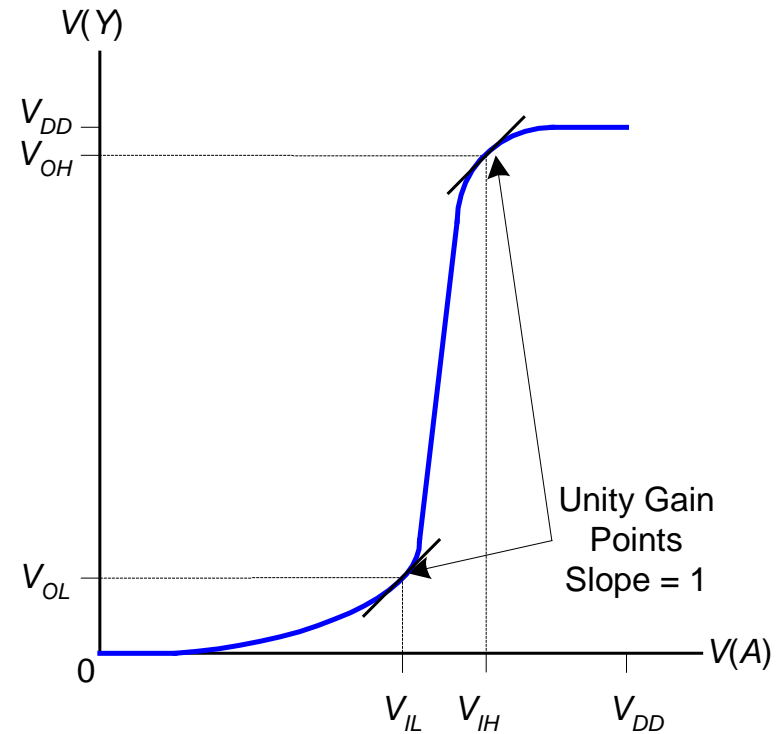

$$NM_H, NM_L < V_{DD}/2$$

DC Transfer Characteristics

FROM ZERO TO ONE
FROM ZERO TO ONE

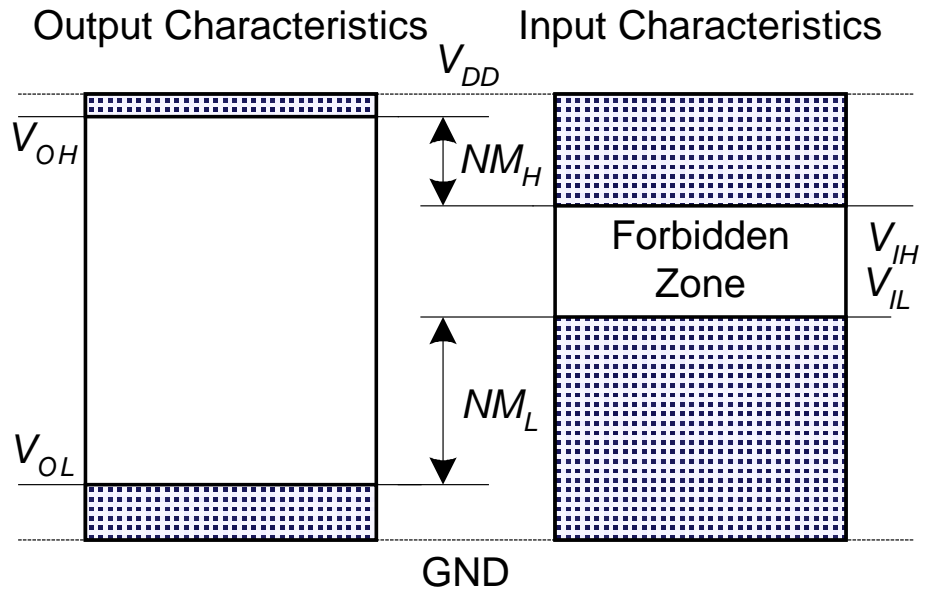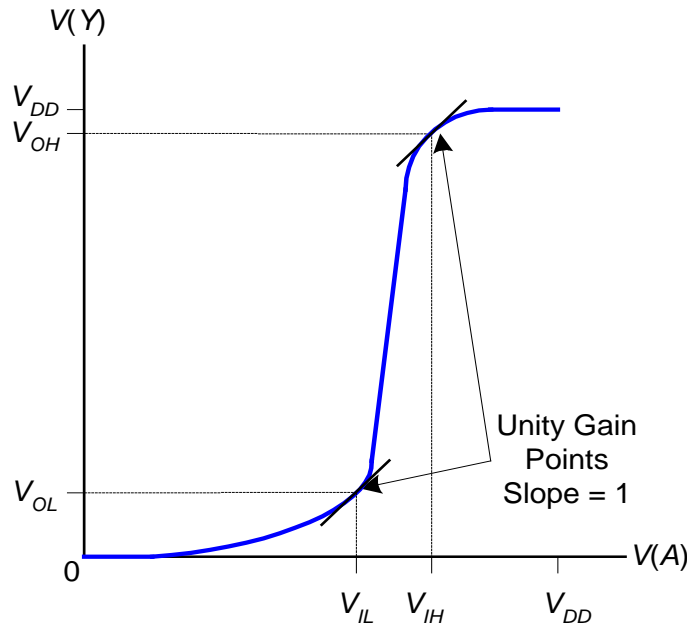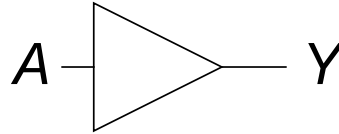

V_{DD} Scaling

- In 1970's and 1980's, $V_{DD} = 5\text{ V}$
- V_{DD} has dropped
 - Avoid frying tiny transistors
 - Save power
- 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V, ...
- Be careful connecting chips with different supply voltages

Chips operate because they contain magic smoke

Proof:

- if the magic smoke is let out, the chip stops working






Logic Family Examples

Logic Family	V_{DD}	V_{IL}	V_{IH}	V_{OL}	V_{OH}
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7

Transistors

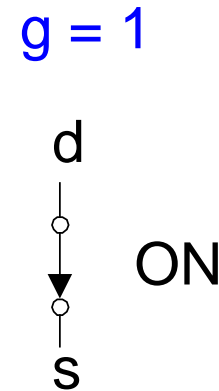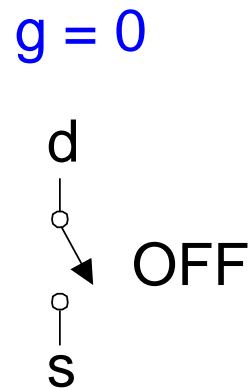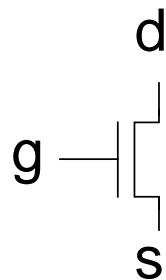- Logic gates built from transistors
- 3-ported voltage-controlled switch
 - 2 ports connected depending on voltage of 3rd
 - d and s are connected (ON) when g is 1




Robert Noyce, 1927-1990

- Nicknamed “Mayor of Silicon Valley”
- Cofounded Fairchild Semiconductor in 1957
- Cofounded Intel in 1968
- Co-invented the integrated circuit





Silicon

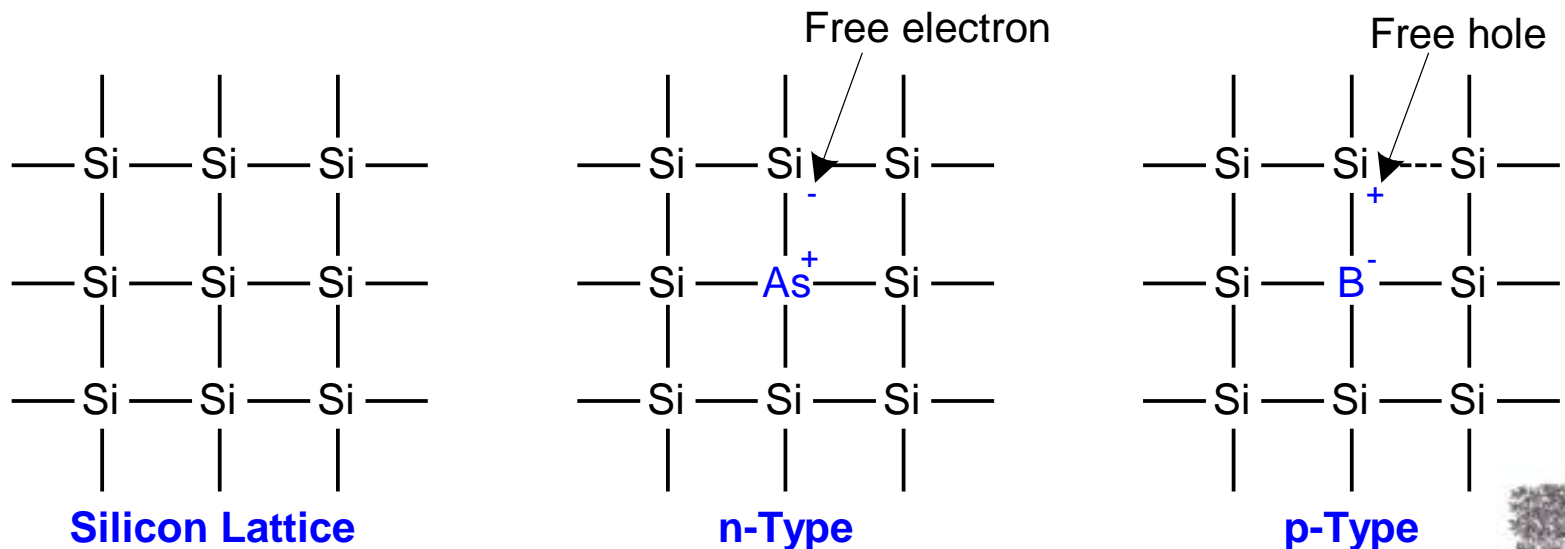- Transistors built from silicon, a semiconductor
- Pure silicon is a poor conductor (no free charges)
- Doped silicon is a good conductor (free charges)
 - n-type (free *n*egative charges, electrons)
 - p-type (free *p*ositive charges, holes)



MOS Transistors

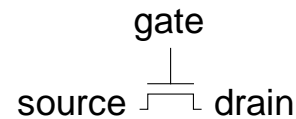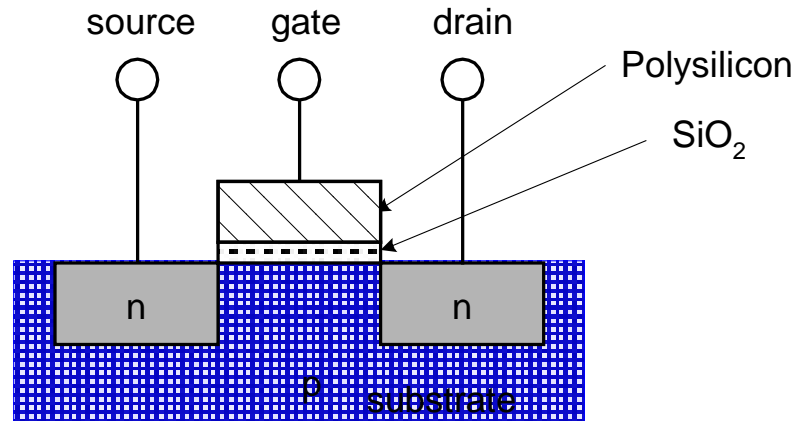- **Metal oxide silicon (MOS) transistors:**
 - Polysilicon (used to be **metal**) gate
 - **Oxide** (silicon dioxide) insulator
 - Doped **silicon**




nMOS

Transistors: nMOS


Gate = 0

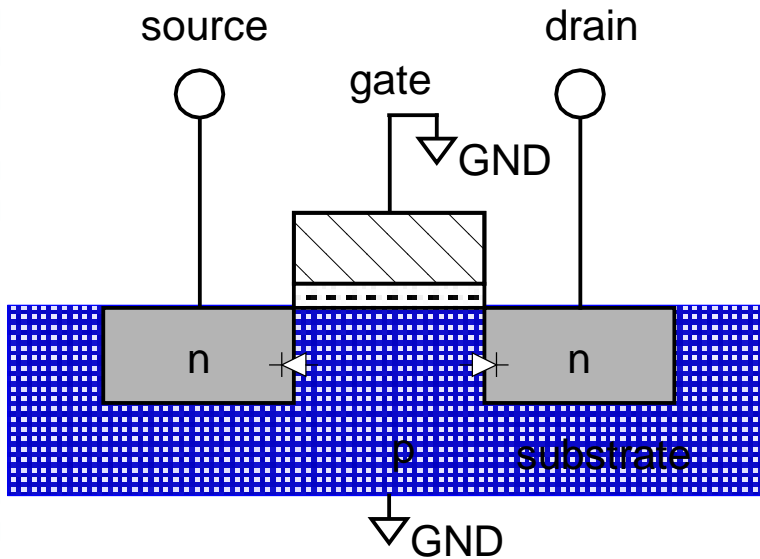OFF (no connection between source and drain)





Gate = 1

ON (channel between source and drain)

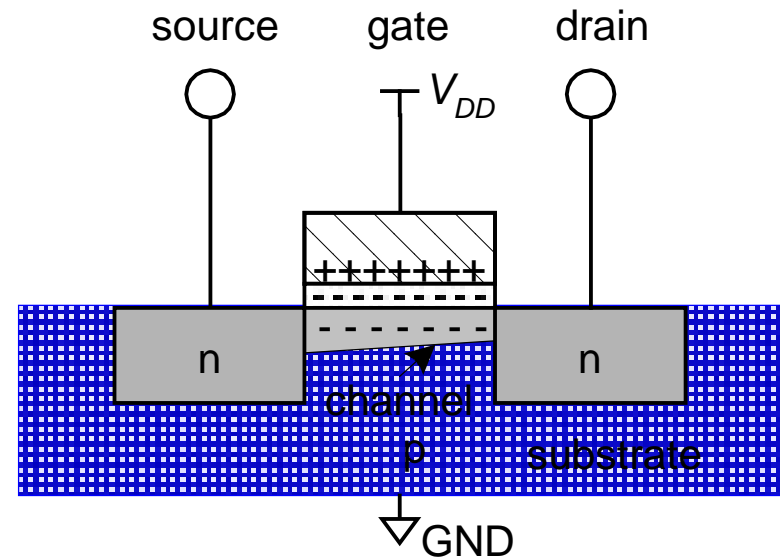

Transistors: pMOS

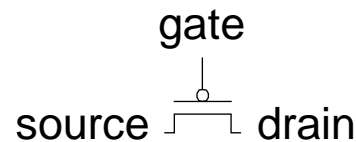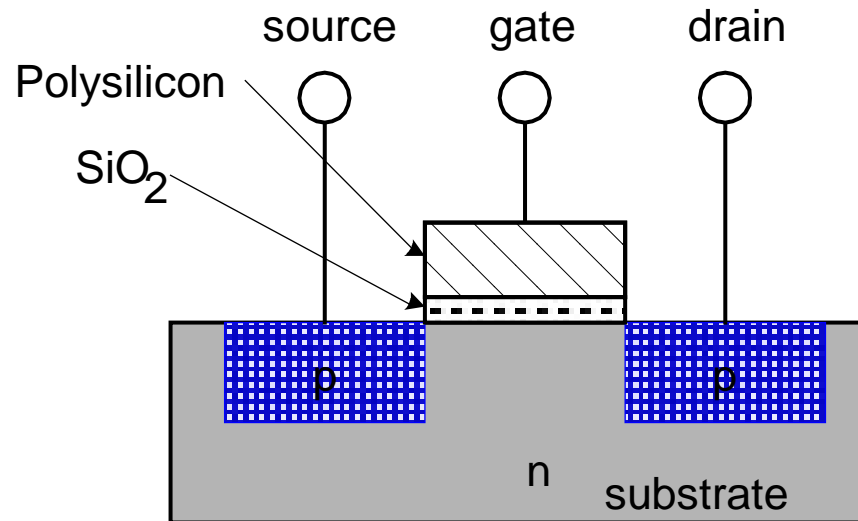
- pMOS transistor is opposite
 - ON when Gate = 0
 - OFF when Gate = 1




Transistor Function

FROM ZERO TO ONE
FROM ZERO TO ONE


nMOS

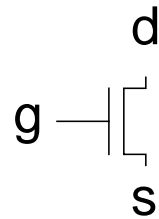




$g = 0$

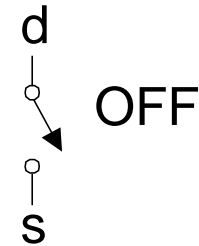

$g = 1$

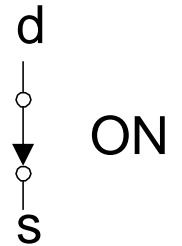


pMOS

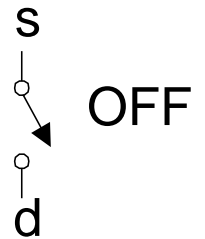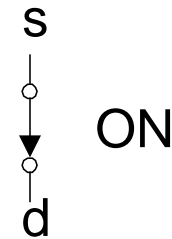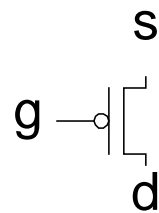


Transistor Function

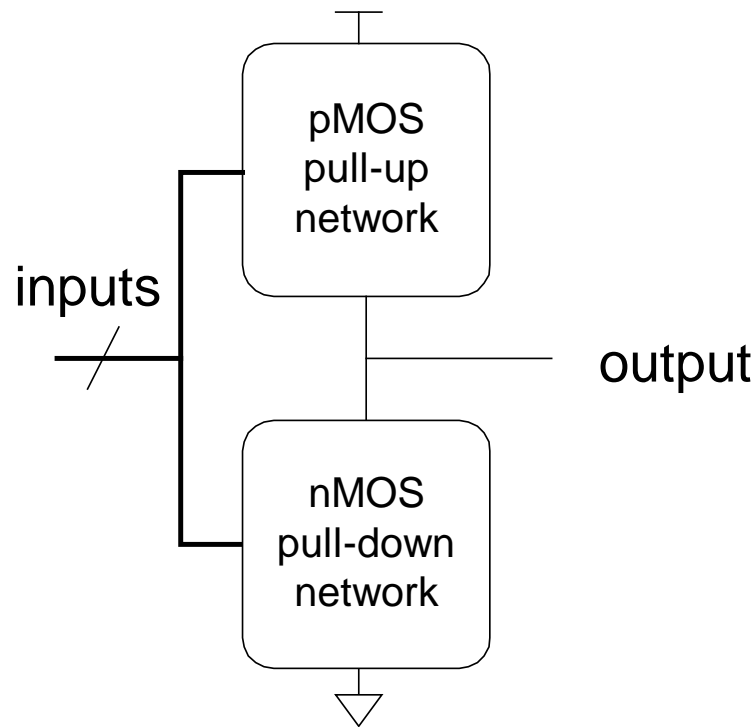- **nMOS:** pass good 0's, so connect source to GND
- **pMOS:** pass good 1's, so connect source to V_{DD}




CMOS Gates: NOT Gate

NOT

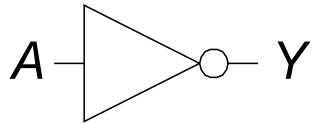

$$Y = \overline{A}$$


A	Y
0	1
1	0

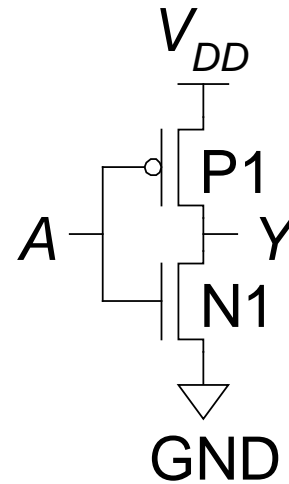

A	P1	N1	Y
0			
1			


CMOS Gates: NOT Gate

NOT

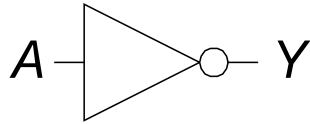

$$Y = \overline{A}$$

A	Y
0	1
1	0

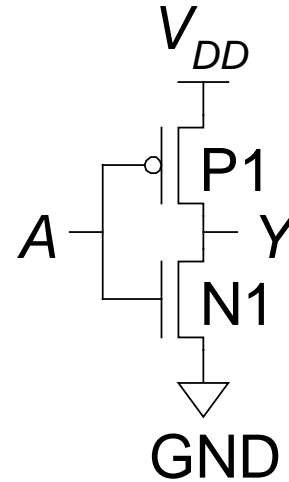


A	P1	N1	Y
0	ON	OFF	1
1	OFF	ON	0

FROM ZERO TO ONE
FROM ZERO TO ONE


CMOS Gates: NAND Gate

NAND

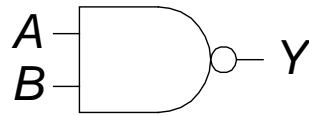

$$Y = \overline{AB}$$


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

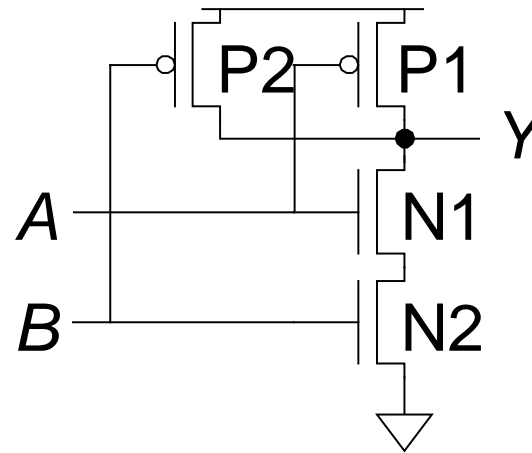

A	B	P1	P2	N1	N2	Y
0	0					
0	1					
1	0					
1	1					


CMOS Gates: NAND Gate

NAND

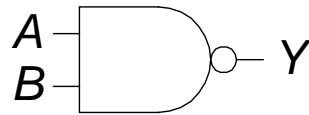

$$Y = \overline{AB}$$


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

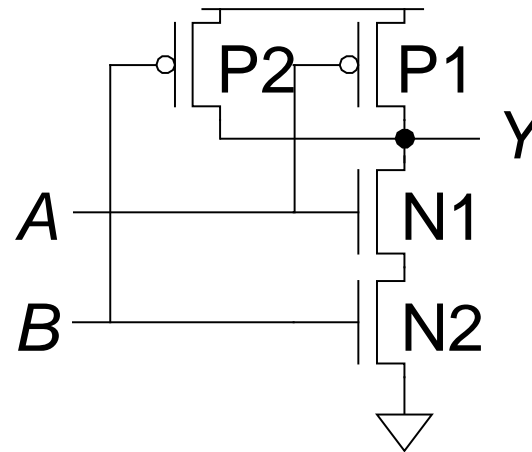

A	B	P1	P2	N1	N2	Y
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0

FROM ZERO TO ONE
FROM ZERO TO ONE

CMOS Gate Structure

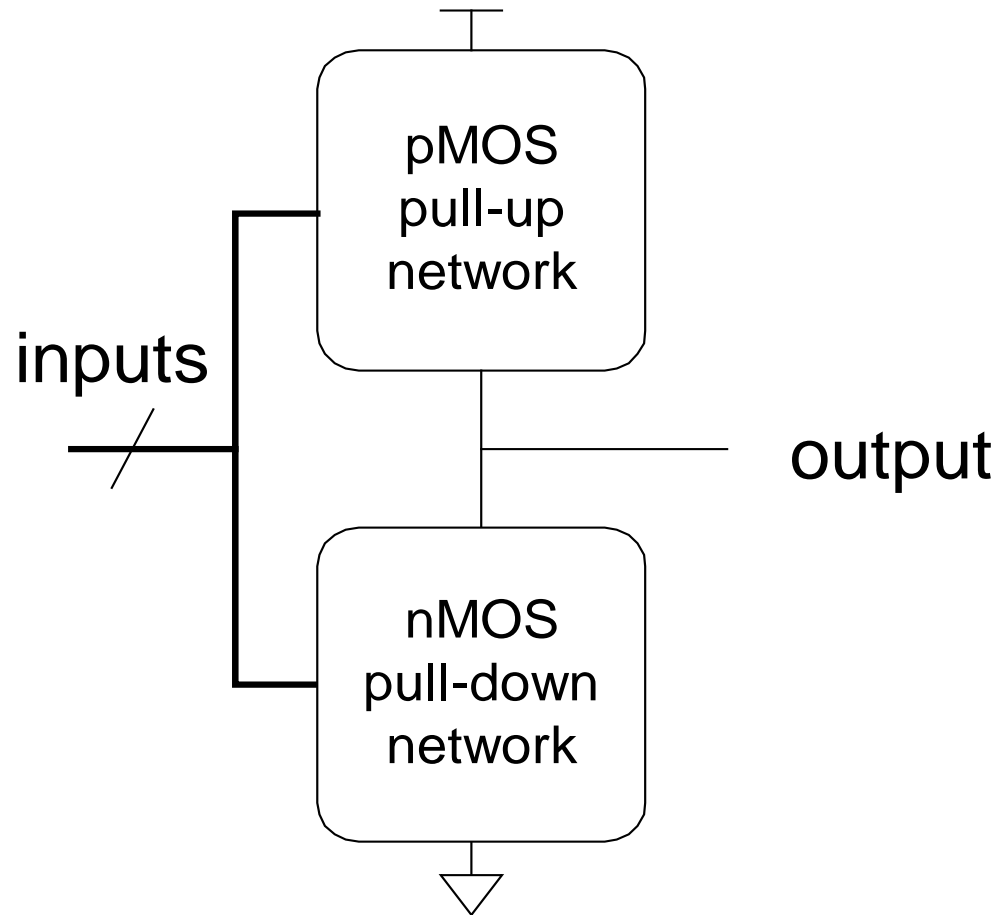

FROM ZERO TO ONE
FROM ZERO TO ONE

NOR Gate


How do you build a three-input NOR gate?

Other CMOS Gates

How do you build a two-input AND gate?


FROM ZERO TO ONE
FROM ZERO TO ONE

AND2 Gate

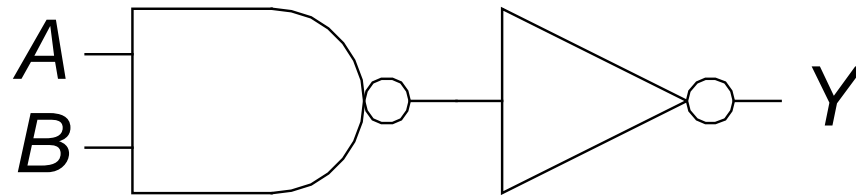


Transmission Gates

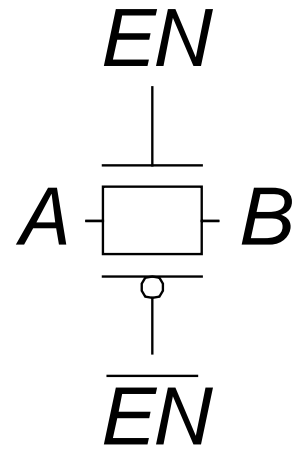- nMOS pass 1's poorly
- pMOS pass 0's poorly
- Transmission gate is a better switch
 - passes both 0 and 1 well
- When $EN = 1$, the switch is ON:
 - $EN = 0$ and A is connected to B
- When $EN = 0$, the switch is OFF:
 - A is not connected to B




Pseudo-nMOS Gates

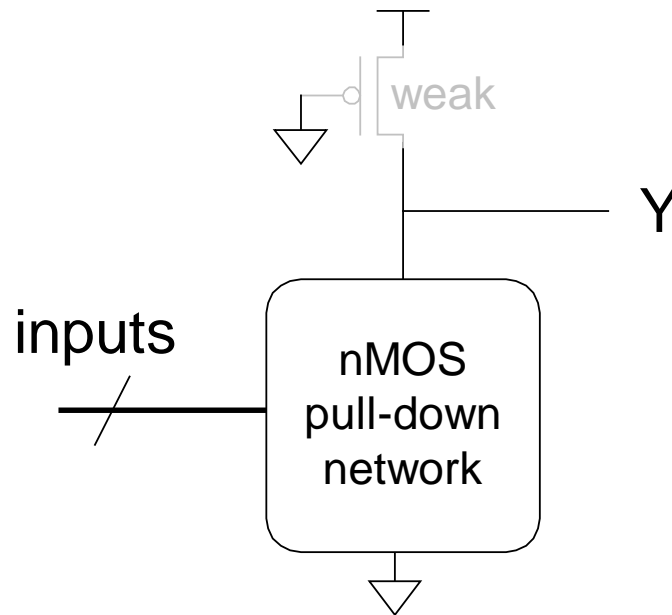- Replace pull-up network with *weak* pMOS transistor that is always on
- pMOS transistor: pulls output HIGH *only* when nMOS network not pulling it LOW




Pseudo-nMOS Example

Pseudo-nMOS NOR4

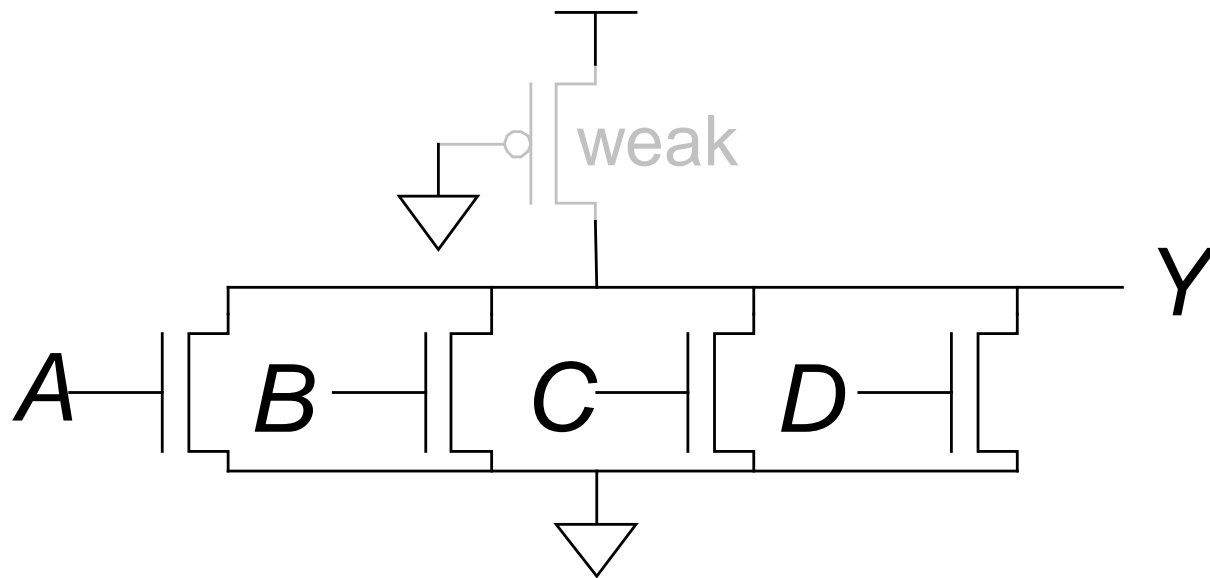


Gordon Moore, 1929-

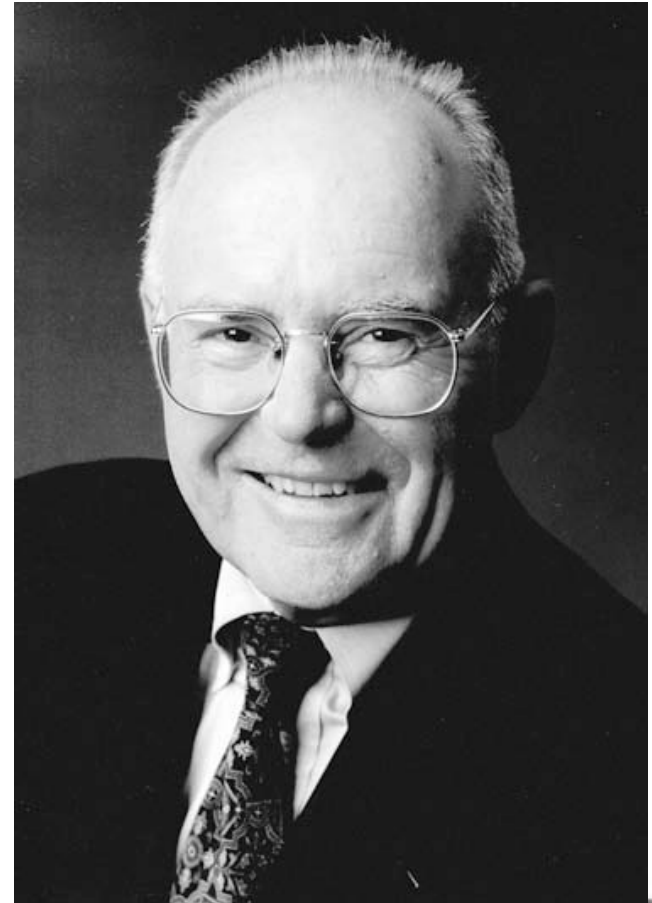- Cofounded Intel in 1968 with Robert Noyce.
- **Moore's Law:** number of transistors on a computer chip doubles every year (observed in 1965)
- Since 1975, transistor counts have doubled every two years.



FROM ZERO TO ONE
FROM ZERO TO ONE

Moore's Law

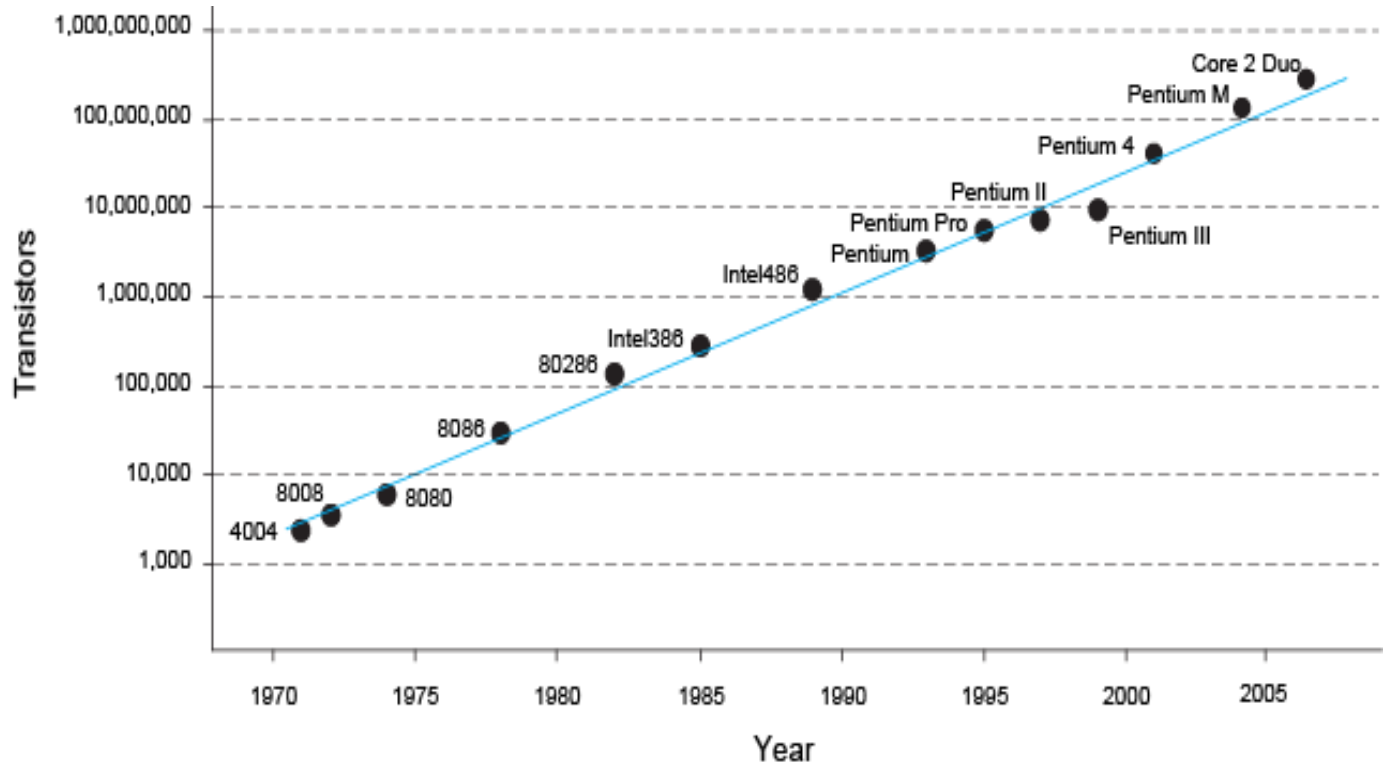

- *“If the automobile had followed the same development cycle as the computer, a Rolls-Royce would today cost \$100, get one million miles to the gallon, and explode once a year . . .”*

– Robert Cringley

Power Consumption

- Power = Energy consumed per unit time
 - Dynamic power consumption
 - Static power consumption

Dynamic Power Consumption

- **Power to charge transistor gate capacitances**
 - Energy required to charge a capacitance, C , to V_{DD} is CV_{DD}^2
 - Circuit running at frequency f : transistors switch (from 1 to 0 or vice versa) at that frequency
 - Capacitor is charged $f/2$ times per second (discharging from 1 to 0 is free)
- Dynamic power consumption:

$$P_{dynamic} = \frac{1}{2}CV_{DD}^2f$$

Static Power Consumption

- Power consumed when no gates are switching
- Caused by the *quiescent supply current*, I_{DD} (also called the *leakage current*)
- Static power consumption:

$$P_{static} = I_{DD}V_{DD}$$

Power Consumption Example

- Estimate the power consumption of a wireless handheld computer
 - $V_{DD} = 1.2 \text{ V}$
 - $C = 20 \text{ nF}$
 - $f = 1 \text{ GHz}$
 - $I_{DD} = 20 \text{ mA}$

Power Consumption Example

- Estimate the power consumption of a wireless handheld computer
 - $V_{DD} = 1.2 \text{ V}$
 - $C = 20 \text{ nF}$
 - $f = 1 \text{ GHz}$
 - $I_{DD} = 20 \text{ mA}$

$$\begin{aligned} P &= \frac{1}{2} C V_{DD}^2 f + I_{DD} V_{DD} \\ &= \frac{1}{2} (20 \text{ nF}) (1.2 \text{ V})^2 (1 \text{ GHz}) + \\ &\quad (20 \text{ mA}) (1.2 \text{ V}) \\ &= (14.4 + 0.024) \text{ W} \approx 14.4 \text{ W} \end{aligned}$$