

# CHAPTER 2



## **Logic Gates**

# Contents

---

- ❑ Boolean Variables & Truth Tables
- ❑ *OR Operation*
- ❑ *AND Operation*
- ❑ NOT Operation
- ❑ NOR Operation
- ❑ NAND Operation
- ❑ The Exclusive- OR Gate
- ❑ The Exclusive-NOR Gate
- ❑ INTEGRATED CIRCUIT LOGIC FAMILIES

# Boolean Variables & Truth Tables

---

LOGIC 0	LOGIC 1
False	True
Off	On
Low	High
No	Yes
Open Switch	Close Switch

A	B	$X = A+B$
0	0	0
0	1	1
1	0	1
1	1	1


# Inverter

---

## ■ Inverter

- The inverter (NOT circuit) performs the operation called inversion or complementation.
- The inverter changes one logic level to the opposite level.
- In terms of bits, it changes a 1 to a 0 and a 0 to a 1.
- Standard logic symbols for the inverter is,

 **Distinctive shape symbols with negation indicators**



# Inverter

---

## ■ Inverter Truth Table


INPUT	OUTPUT
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)

- A table such as this is called a truth table.
- When a HIGH level is applied to an inverter input, a LOW level will appear on its output.



# Inverter
 
## ■ Inverter

- When the input is LOW, the output is HIGH and vice versa.
- producing an inverted output pulse.
- Standard logic symbols for the inverter is,



**Input Pulse**

  


**output Pulse**

# Inverter

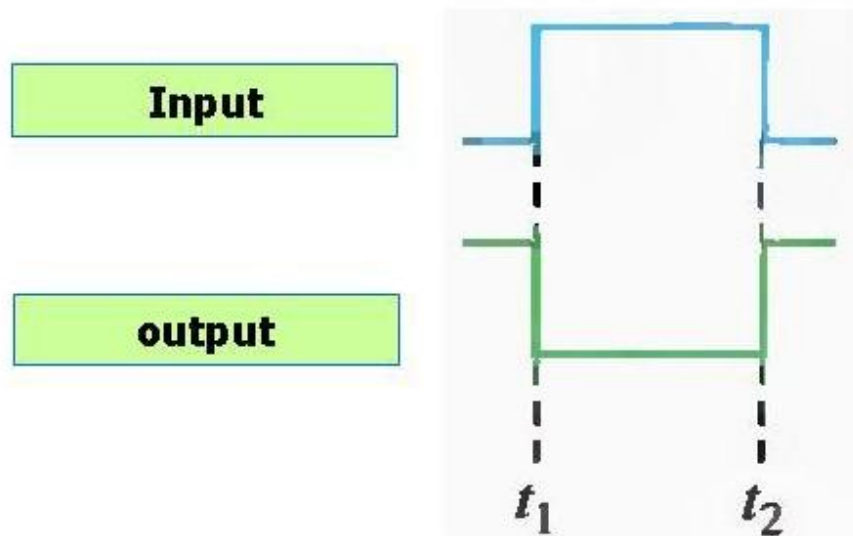
## Timing Diagram of Inverter

- timing diagram is basically a graph that accurately displays the relationship of two or more waveforms with respect to each other on a time basis. .




# Timing Diagram Example

---

 


=

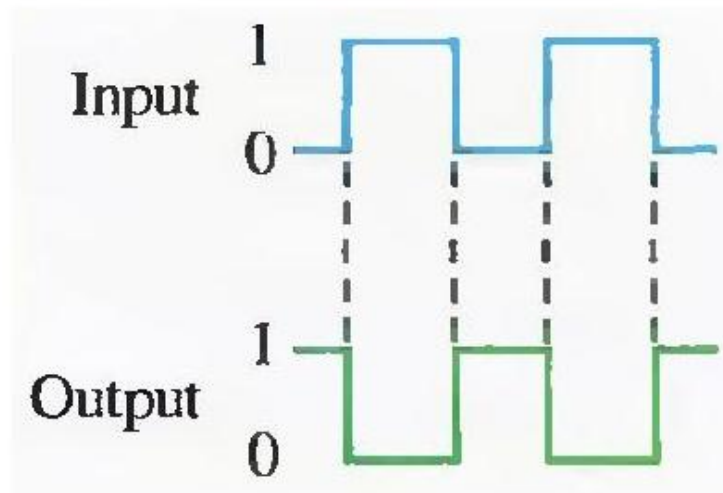



# Inverter


## Application of Inverter

 
 
# OR Gate

---


- An OR gate can have two or more inputs and performs what is known as logical addition.
- Standard logic symbols for the OR gate showing two input and single output.



- An OR gate can have any number of inputs greater than one.
- An OR gate produces a HIGH on the output when any of the inputs is HIGH.
- The output is LOW only when all of the inputs are LOW.


# OR Operation

Two Inputs OR Gate

 

A	B	$X = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Three Inputs OR Gate

 


A	B	C	$X = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

# Logic Expression of OR


The operation of a 2-input OR gate can be expressed as follows: If one input variable is A, if the other input variable is B, and if the output variable is X, then the Boolean expression is

$$X=A+B$$

 
Boolean expressions for OR gates with two, three, and four inputs,



$$A+B=X$$

 


$$A+B+C=X$$

 

$$A+B+C+D=X$$

# Timing Diagrams of OR gates

---

 


**When either input or both inputs are HIGH, the output is HIGH**

# An application: Alarm System

---

Open door/window sensors

**HIGH = open**  
**LOW = closed**

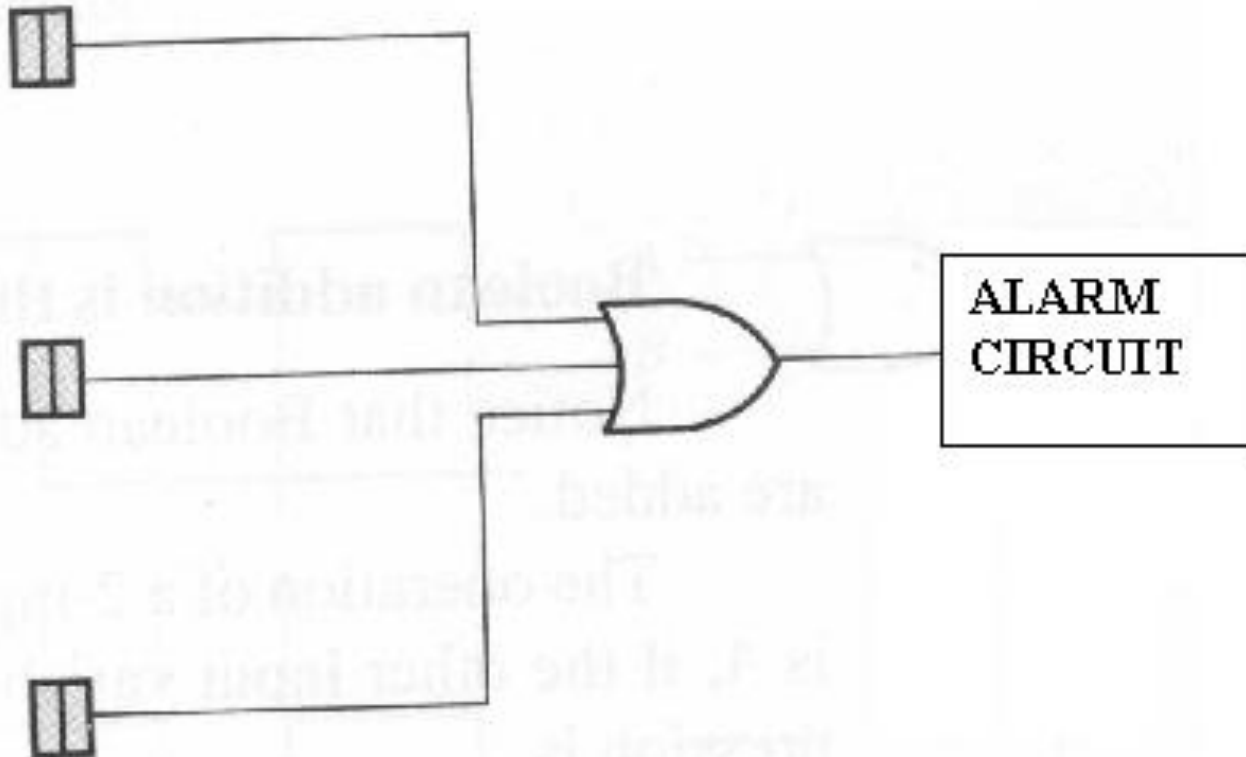


# AND Gate

---
 
## AND Gate

- The **AND gate** is one of the basic gates that can be combined to form any logic function.
- An **AND gate** can have two or more inputs and performs what is known as logical multiplication.
- The term gate is used to describe a circuit that performs a basic logic operation.
- The **AND gate** is composed of two or more inputs and a single output.
- Standard logical symbol of AND gate is,



# AND Gate

---

## ■ Operations of an AND Gate


- An AND gate produces a HIGH output only when all of the inputs are HIGH.
- When any of the inputs is LOW, the output is LOW.
- Therefore, the basic purpose of an AND gate is to determine when certain conditions are simultaneously true.



# AND Operation

Two Inputs AND Gate


INPUTS

 

OUTPUT  
 $X = A * B$

Three Inputs AND Gate

A  
B  
C  
INPUTS

 


$X = A * B * C$   
OUTPUT

A	B	$X = A * B$
0	0	0
0	1	0
1	0	0
1	1	1

A	B	C	$X = A * B * C$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

# Timing Diagrams of AND gates


---

 

# An application: A Seat Belt Alarm System


Ignition switch HIGH=ON  
LOW=OFF

Seat belt HIGH=Unbuckled  
LOW=Bucked

 

# NOR Operation

Two Inputs NOR Gate

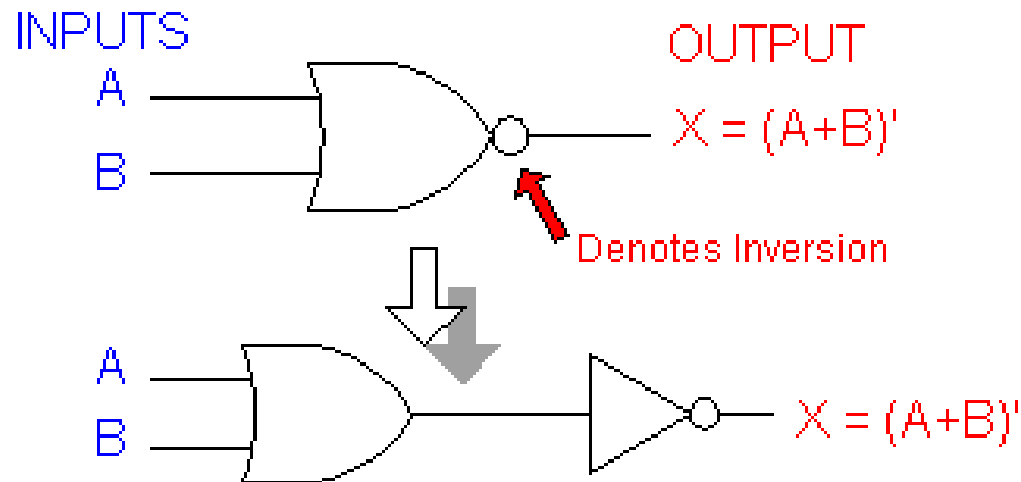


INPUTS		OR	NOR
A	B	$X = A+B$	$X = (A+B)'$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 
# Negative AND equivalent of a NOR gate

---

Standard symbols representing the two equivalent operations of the NOR gate.


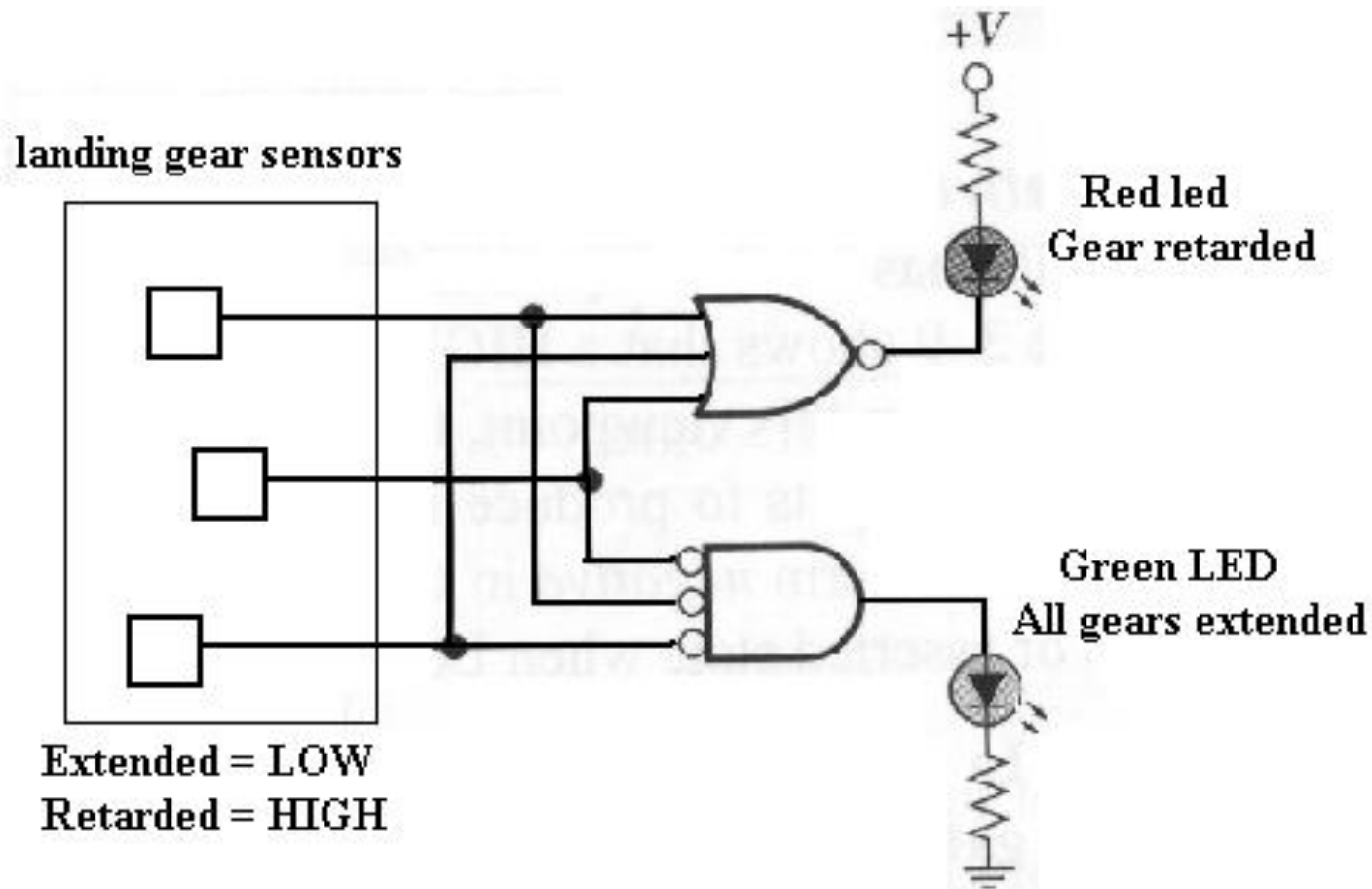
# An application: An aircraft landing indicator



# NAND Gate

---

The NAND gate is a popular logic element because it can be used as a universal gate.


NAND gates can be used in combination to perform the AND, OR, and inverter operations.

The term NAND is a contraction of NOT-AND and implies an AND function with a Complemented (inverted) output.

The standard logic symbol for a 2-input NAND gate and its equivalency to an AND gate followed by an inverter.

# NAND Operation

Two Inputs NAND Gate

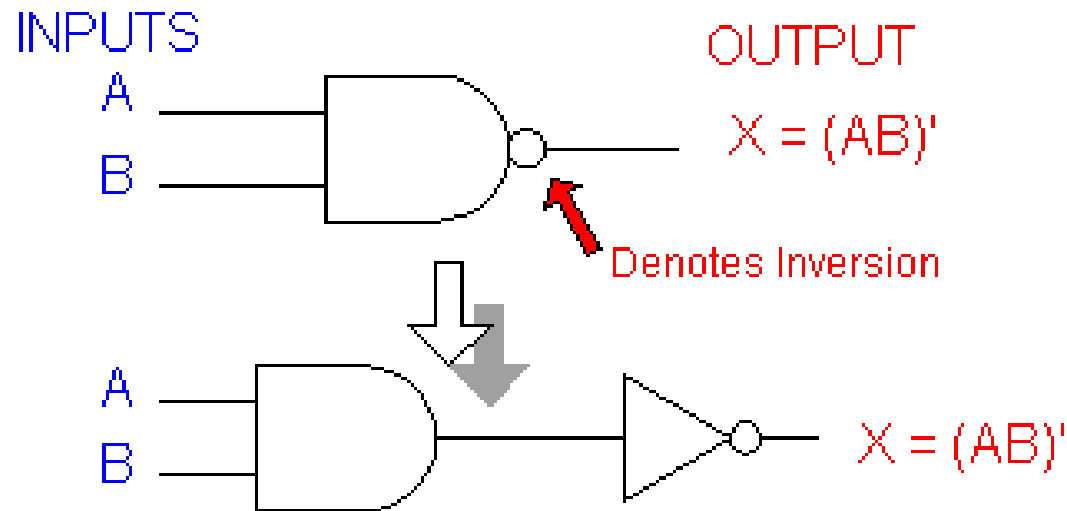

INPUTS		AND	NAND
A	B	$X = AB$	$X = (AB)'$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0



# Logic Expression for NAND Gate

---


The Boolean expression for the output of a 2-input NAND gate is,

$$X = \overline{AB}$$

two input variables A and B, are first ANDed and then complemented, as indicated by the bar over the AND expression.


# Negative OR Equivalent Operation of the NAND Gate

---

 


**NAND**

≡

 

**Negative-OR**

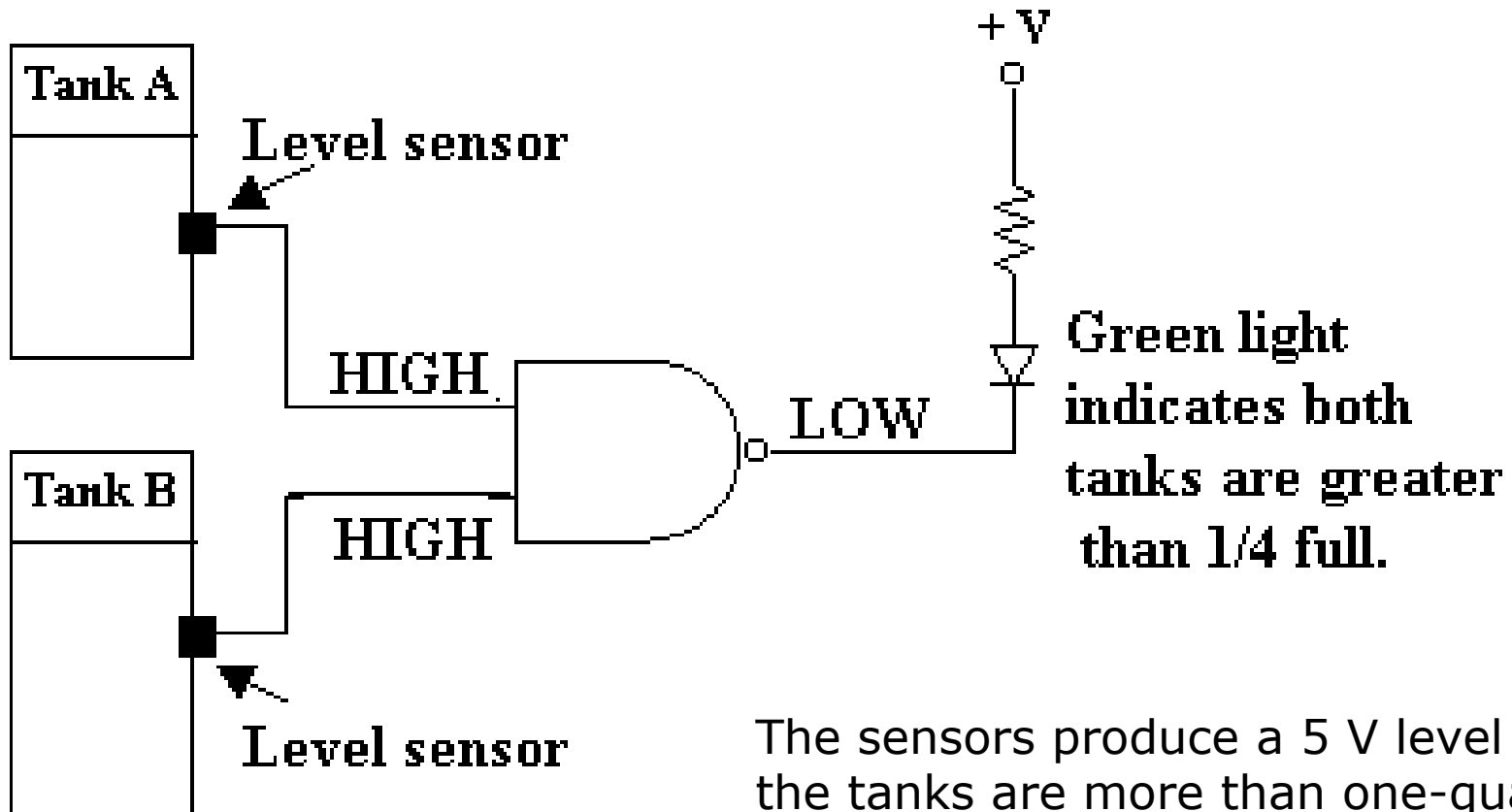
# An application: A Manufacturing Plant Tank Indicator



The sensors produce a 5 V level when the tanks are more than one-quarter full.

# The Exclusive- OR Gate


---

 

Inputs		output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

# The Exclusive-NOR Gate

---

 


- equivalence 0 coincidence X-NOR

Inputs		output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

# Timing diagram

---

 

# INTEGRATED CIRCUIT LOGIC FAMILIES

---

- **Diode Logic (DL)**
- **Resistor-Transistor Logic (RTL)**
- **Diode-Transistor Logic (DTL)**
- **Transistor-Transistor Logic (TTL)**
- **Emitter-Coupled Logic (ECL)**
- **CMOS Logic**

---

## □ **Fan-in**

- The number of standard loads drawn by an input to ensure reliable operation. Most inputs have a fan-in of 1.

## □ **Fan-out**

- The number of standard loads that can be reliably driven by an output, without causing the output voltage to shift out of its legal range of values.



# Comparison of performance characteristics of CMOS, TTL and ECL logic gates.

Technology	CMOS (silicon gate)	CMOS (metal gate)	TTL std	TTL LS	TTL S	TTL ALS	TTL AS	ECL
Device series	74HC	4000B	74	74LS	74S	74ALS	74AS	10KH
Power dissipation : Static		1 uW	10 mW	2 mW	19 mW	1 mW	8.5 mW	25 mW
At 100 kHz	0.17 mW	0.1 mW	10 mW	2 mW	19 mW	1 mW	8.5 mW	25 mW
Propagation delay time	8 ns	50 ns	10 ns	10 ns	3 ns	4 ns	1.5 ns	1 ns
Fan-out			10	20	20	20	40	

Std : standard

LS: Low power Schottky


S: Schottky

ALS: Advanced Low power Schottky

AS: Advanced Schottky

# IEEE symbols for logic gates

Figure A-2  
Distinctive- and rectangular-  
shape logic symbols.

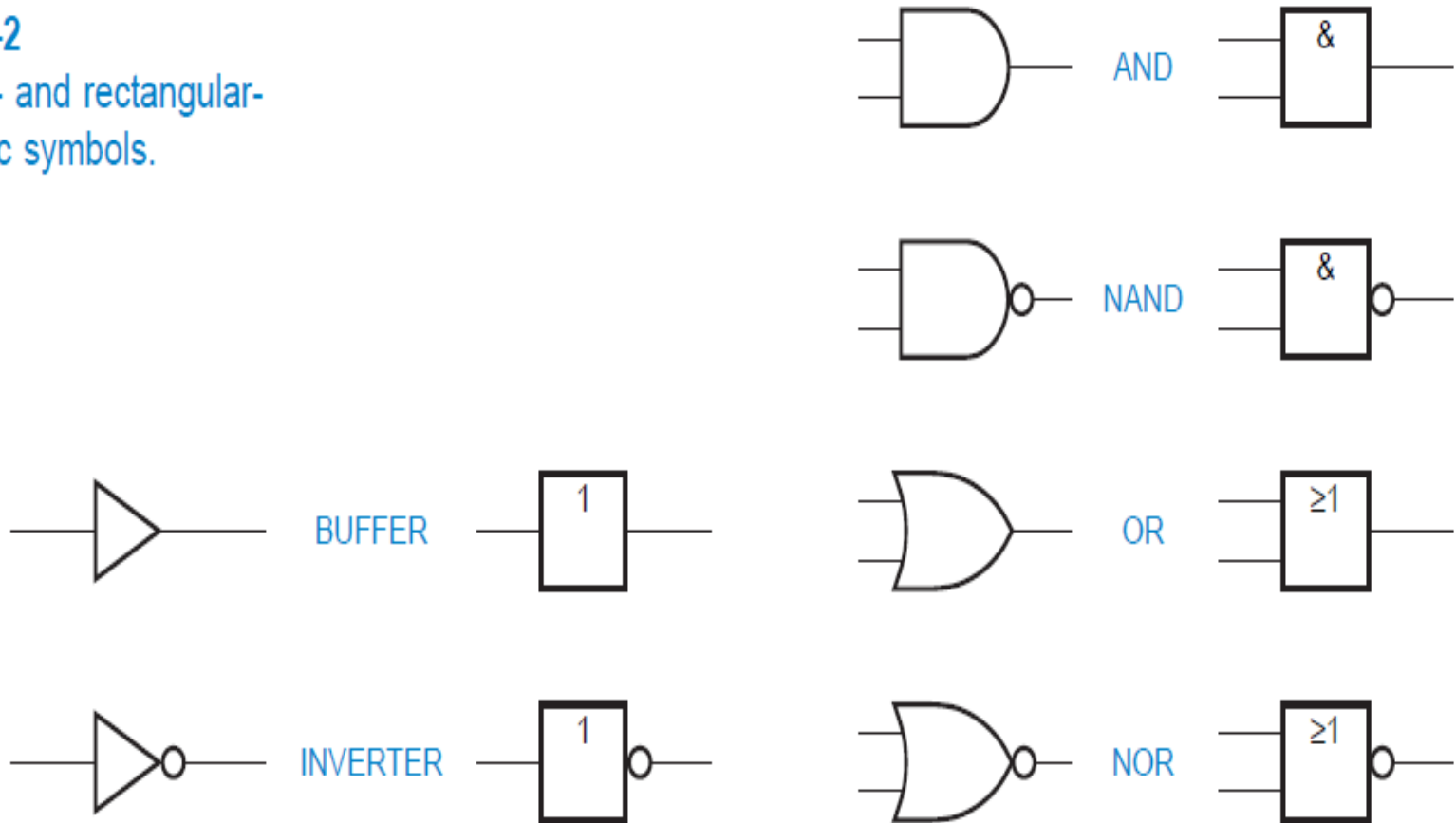

# QUESTIONS?

