

Quick Revision



Elementary Logic Gates




Name

Inverter
(NOT Gate)

AND Gate

OR Gate

Symbol

   

*Truth
Table*

A	Z
0	1
1	0

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

*Logic
Equation*

$$Z = A' = \bar{A}$$


$$Z = A \cdot B = AB$$

$$Z = A + B$$

Other Elementary Logic Gates

NAND Gate

(NOT AND)

 

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

$$Z = (A \cdot B)' = \overline{AB}$$

Name


Symbol

Truth Table

Logic Equation

NOR Gate

(NOT OR)

 

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

$$Z = (A + B)' = \overline{A+B}$$

Using Truth Table to Prove theorem

- DeMorgan's Theorems

T8a: $(X+Y)' = X' \cdot Y'$




T8b: $(X \cdot Y)' = X' + Y'$

a NOR gate is equivalent to an AND gate with inverted inputs


X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

a NAND gate is equivalent to an OR gate with inverted inputs

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

   

alternate logic symbols

 

Other Logic Gates



Name

Buffer

Exclusive-OR Gate
aka XOR Gate

Exclusive-NOR Gate
aka XNOR or NXOR Gate

Symbol

  

Truth Table

A	Z
0	0
1	1

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

Logic Equation

$$Z = A$$

$$Z = A \oplus B = \bar{A}B + A\bar{B}$$

$$Z = \overline{A \oplus B} = \bar{A}\bar{B} + AB$$



also denoted $Z = A \odot B$

Interesting Properties of XOR


- **Controlled inverter**
 - $X \oplus 0 = X$
 - $X \oplus 1 = X'$
- **XOR with one input inverted = XNOR**
 - $X \oplus Y' = X' \oplus Y = (X \oplus Y)'$
- **XNOR with one input inverted = XOR**
 - $(X \oplus Y')' = (X' \oplus Y)' = X \oplus Y$
- **Constant output**
 - $X \oplus X = 0$
 - $X \oplus X' = 1$

Exclusive-OR Implementation

 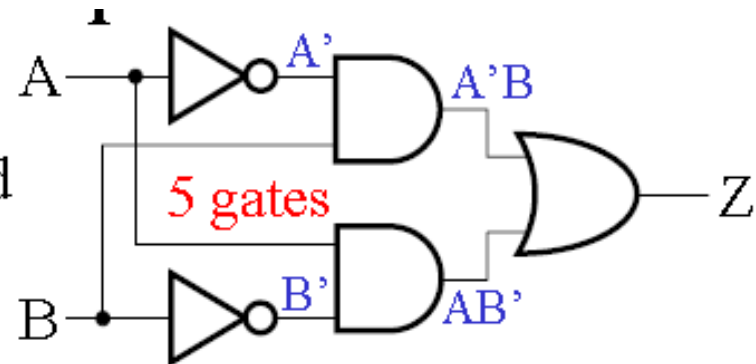- $Z = A'B + AB'$
- XOR & XNOR not considered elementary logic gates by many designers


 
$$\begin{aligned}
 Z &= ((A(AB)'')' (B(AB)'')')' \\
 &= \overline{\overline{A} \overline{AB}} \cdot \overline{\overline{B} \overline{AB}} = \overline{\overline{A} \overline{AB}} + \overline{\overline{B} \overline{AB}} \\
 &= A(\overline{A} + \overline{B}) + B(\overline{A} + \overline{B}) \\
 &= AA' + AB' + A'B + BB' = AB' + A'B
 \end{aligned}$$



$$\begin{aligned}
 Z &= ((A+B)' + AB)' = \overline{\overline{A+B} + AB} \\
 &= \overline{\overline{A+B}} \cdot \overline{AB} = (A+B)(\overline{A} + \overline{B}) \\
 &= AA' + AB' + A'B + BB' \\
 &= 0 + AB' + A'B + 0 = AB' + A'B
 \end{aligned}$$

Gate-level Representation

- SOP expressions

- AND-OR

- With inverters for complemented literals

$$Z = A'B'C + A'BC + ABC' + ABC$$

- aka 2-level AND-OR logic representation



- POS expressions

- OR-AND

- With inverters for complemented literals

$$Z = (A+B+C) \cdot (A+B'+C) \cdot (A'+B+C) \cdot (A'+B+C')$$

  - aka 2-level OR-AND logic representation



Common Combinational Logic Circuits

- Adders
 - Subtraction typically via 2s complement addition
- Multiplexers
 - *N control signals select 1 of up to $2N$ inputs as output*
- Demultiplexers
 - *N control signals select input to go to 1 of up to $2N$ outputs*
- Decoders
 - *N inputs produce M outputs (typically $M > N$)*
- Encoders
 - *N inputs produce M outputs (typically $N > M$)*
- Converter (same as decoder or encoder)
 - *N inputs produce M outputs (typically $N = M$)*

More Common Circuits

- Comparators

- Compare two *N-bit binary values*
 - Equal-to or Not-equal-to
 - Easiest to design
 - Greater-than, Less-than, Greater-than-or-equal-to, etc.
 - Require adders

- Parity check/generate circuit

- Calculates even or odd parity over *N bits of data*
- Checks for good/bad parity (parity errors) on incoming data

Adder

- Consider i^{th} column addition of 2 binary numbers (A and B)
 - $A_i + B_i + \text{Cin}_i = \text{Cout}_i + \text{Sum}_i$
 - Derive truth table
 - Populate K-maps
 - Obtain minimized SOPs
 - Draw logic diagram
 - Optimize with P&Ts

Truth Table

A	B	C	Co	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


		BC			
		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

$$\begin{aligned}
 S &= A'B'C + A'BC' \\
 &\quad + AB'C' + ABC \\
 &= A'(B \oplus C) + A(B \oplus C) \\
 &= A \oplus B \oplus C
 \end{aligned}$$

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

$$Co = BC + AC + AB$$


Adder

 

	BC			
A	00	01	11	10
0	0	0	1	0
1	0	1	1	1


$$\begin{aligned}
 Co &= A'BC + AB'C + AB \\
 &= C(A'B + AB') + AB \\
 &= C(A \oplus B) + AB
 \end{aligned}$$

 Taking advantage of common product terms between S and Co we see that we can use the XOR gate for $A \oplus B$ to reduce the gate count




Adder


referred to as a *full adder*

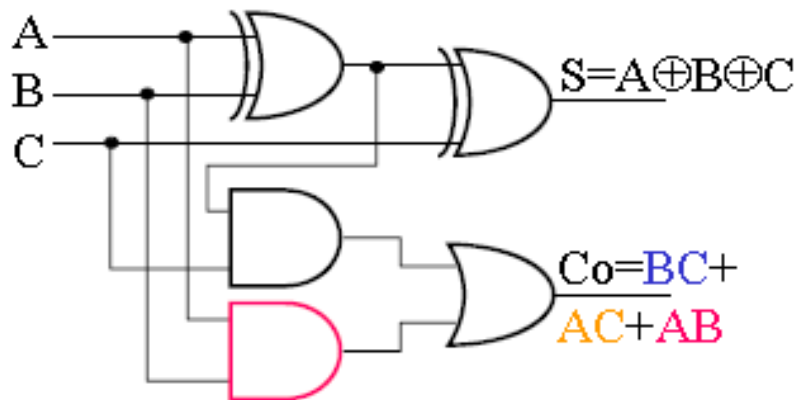

 we can let a block represent the full adder



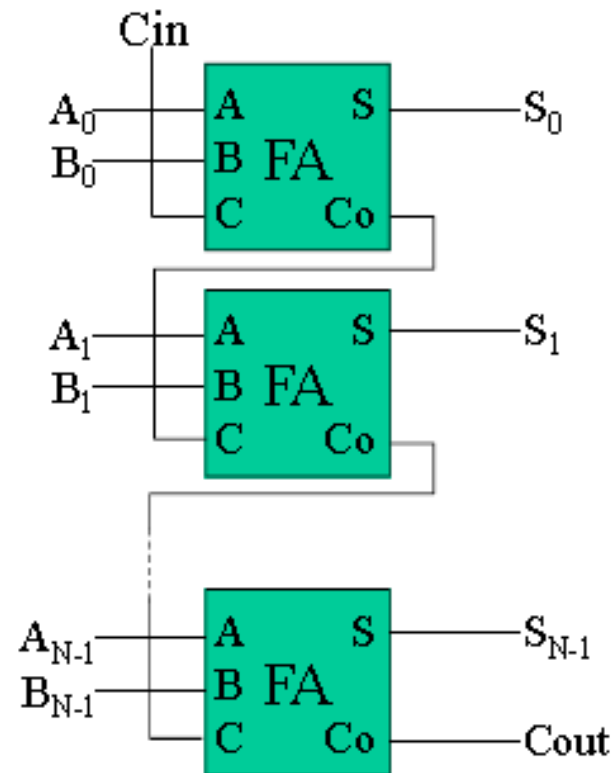now we can build an N -bit adder from N full adders



QUESTIONS?

