

CHW 469 : Embedded Systems

Instructor:

Dr. Ahmed Shalaby <http://bu.edu.eg/staff/ahmedshalaby14#>


<https://piazza.com/fci.bu.edu.eg/spring2017/chw469/home>

What ? Embedded Systems

- **An embedded system is an **electronic system** that:**
 - includes a microcomputer embedded or **hidden** inside.
 - has software programmed into **ROM**.
 - has software that is **not accessible to the user** of the device
 - is configured to perform a **specific** dedicated application (software solves only a limited range of problems)


General Purpose System

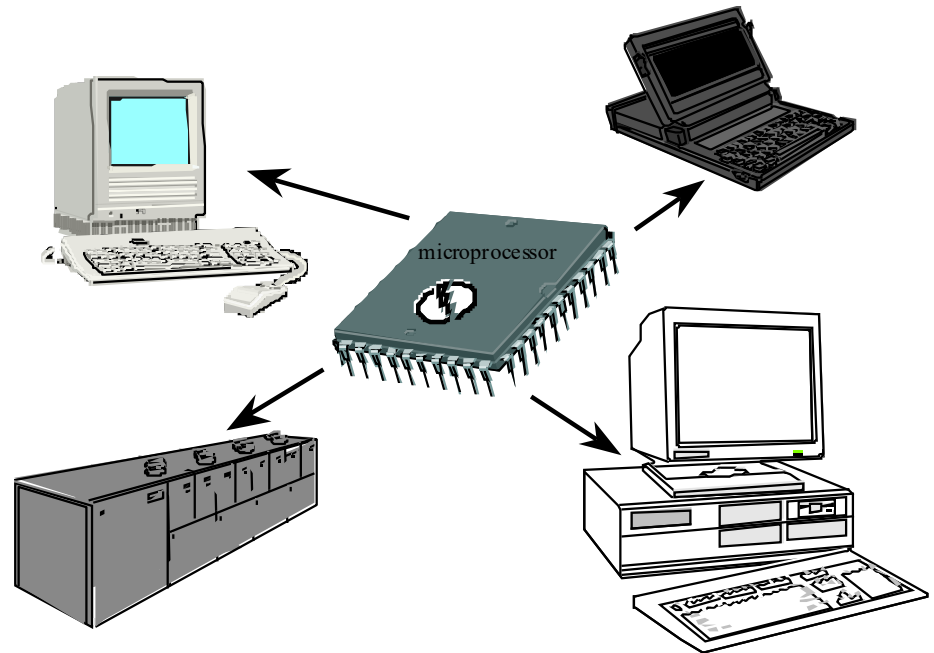- keyboard
- disk
- graphics display
- software useful for a wide variety of purposes
- software that can be changed by user



Embedded System

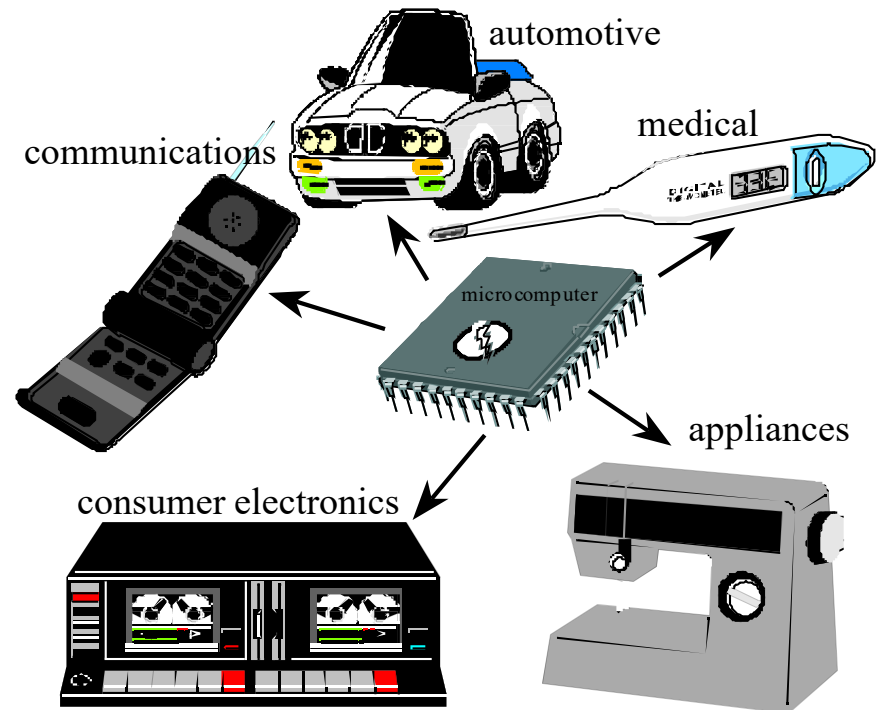- Accepts inputs,
- Performs calculations
- Generates outputs
- Runs in “real time.”





The **internet of things** (IoT)

- Embedded systems (sensors and actuators).
- Internet.

ICU Utilization System

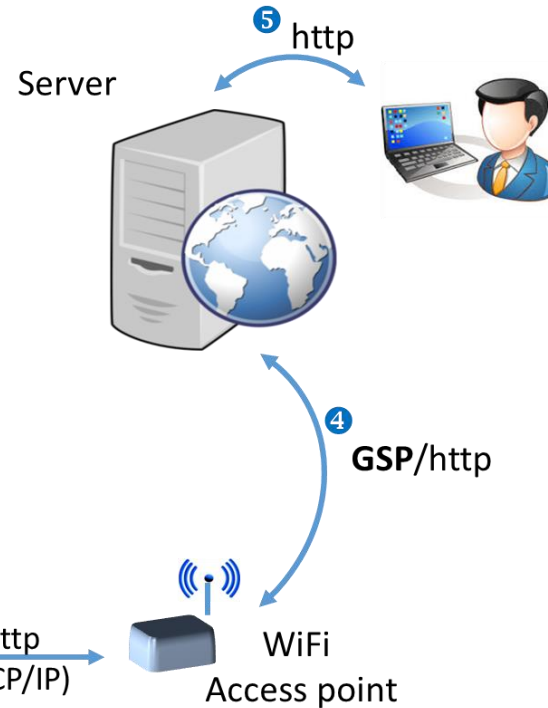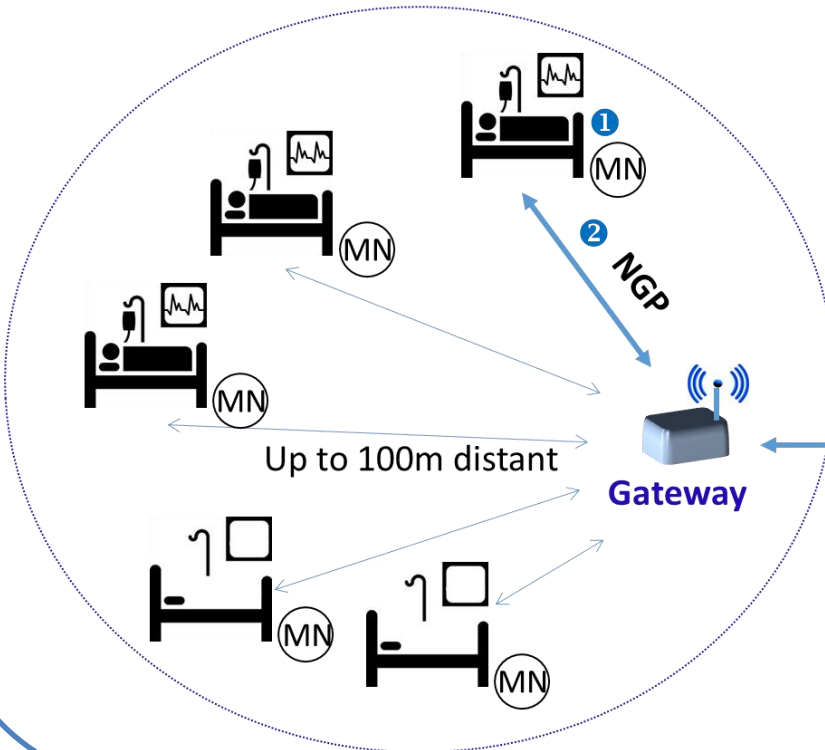Gateway coverage zone
inside Intensive Care Room



NGP = Node Gateway Protocol
GSP = Gateway Server Protocol

(MN) Monitoring Node – watch and report the activity of ICU

Embedded Systems “Big Ideas”

- **HW/SW Architecture**
 - Non processor centric view of architecture
 - Microcontroller, FPGA, analog circuits
- **Bowels of the “operating system”**
 - Specifically, the lower half of the OS
 - Concurrency, parallelism, synchronization
- **Real world design**
 - performance vs. cost tradeoffs, constraints
- **Analyzability**
 - how do you “know” that your drive-by-wire system will function correctly?
- **Application-level techniques**
 - Power Aware Programming




Review of Electronics

Ohm's Law

$$V = I * R \quad \text{Voltage} = \text{Current} * \text{Resistance}$$

$$I = V / R \quad \text{Current} = \text{Voltage} / \text{Resistance}$$
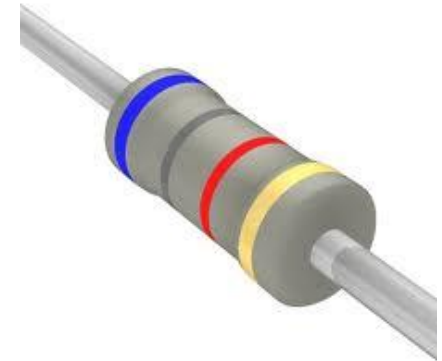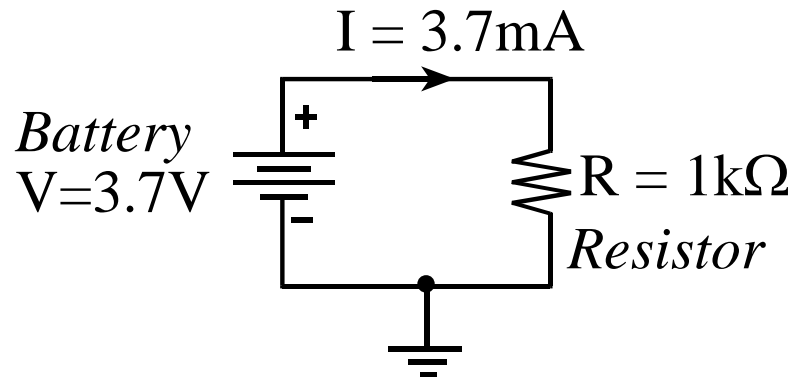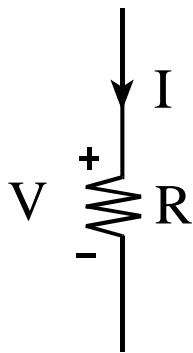
$$R = V / I \quad \text{Resistance} = \text{Voltage} / \text{Current}$$



$$P = V * I \quad \text{Power} = \text{Voltage} * \text{Current}$$

$$P = V^2 / R \quad \text{Power} = \text{Voltage}^2 / \text{Resistance}$$

$$P = I^2 * R \quad \text{Power} = \text{Current}^2 * \text{Resistance}$$




Review of Electronics (Cont...)

- **Voltage**: an electrical potential.
- **Current**: the flow of charge (electrons)
- **Power**: the rate of energy change.
- **Energy**: defines the amount of work that can be done
- **Resistance**: potential divided by flow

Review of Electronics (Cont...)

Kirchhoff's Current Law (KCL).

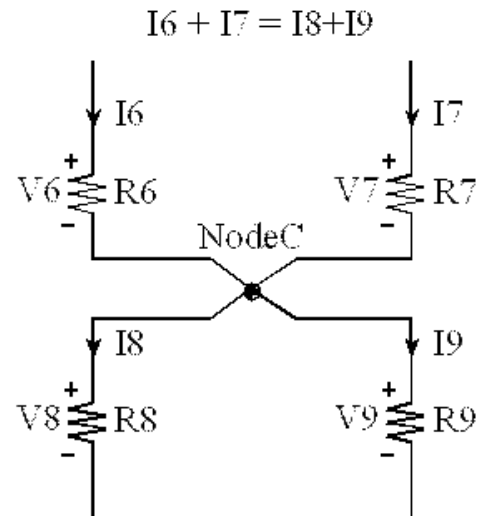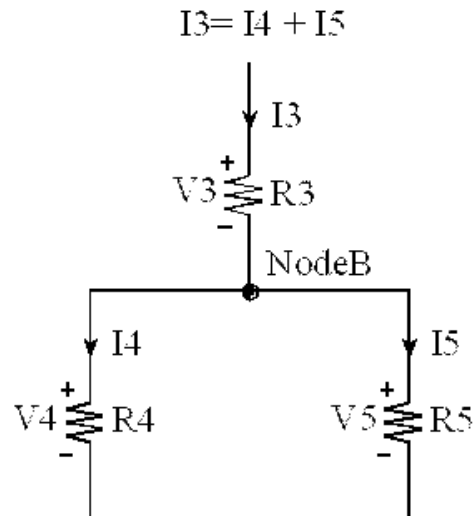
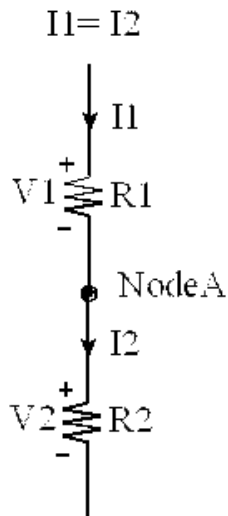
The sum of the currents **into a node** equal the sum of the currents **leaving the node**.



Review of Electronics (Cont...)

Kirchhoff's Voltage Law (KVL).

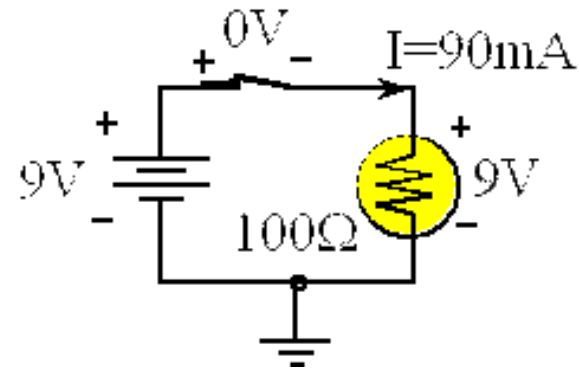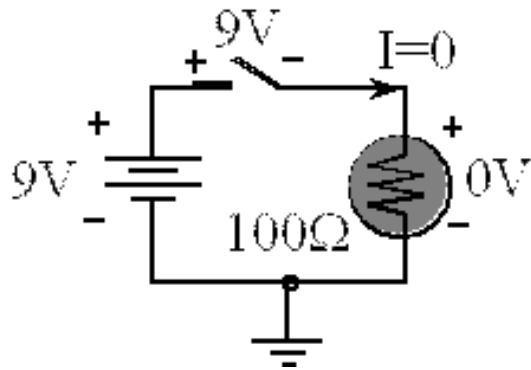The sum of the voltages **around the loop** is zero.




Review of Electronics (Cont...)

Series resistance

If resistor **R1** is in series with resistor **R2**, this combination behaves like one resistor with a value equal to **$R1+R2$**

Parallel resistance

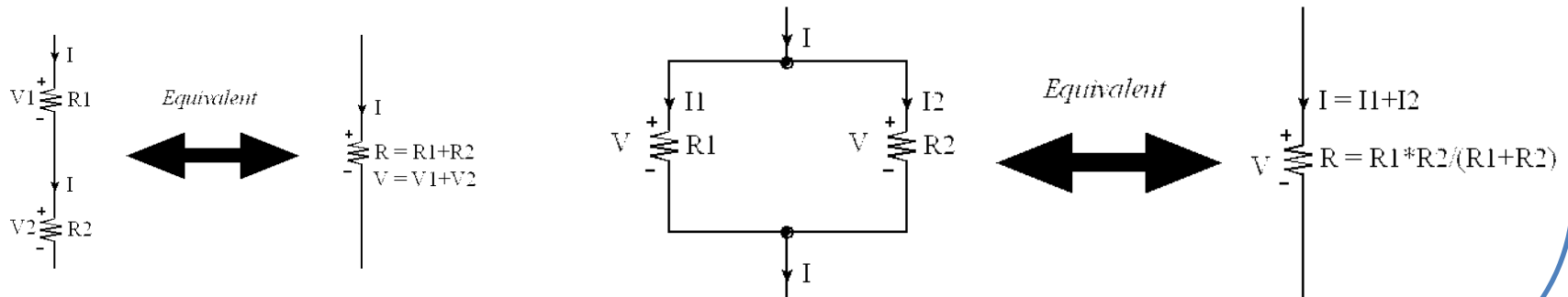
If resistor **R1** is in parallel with resistor **R2**, this combination behaves like one resistor with a value equal to **$R1*R2/(R1+R2)$**



Review of Electronics (Cont...)


Consider this 3-bit digital to analog converter. Define a 3-bit number n (0 to 7) which specifies the three switch positions. $n = 0$ means none are pushed. $n = 1$ means Sw0 is pushed. $n = 2$ means Sw1 is pushed. $n = 3$ means Sw1 and Sw0 are pushed. $n = 4$ means Sw2 is pushed. $n = 5$ means Sw2 and Sw0 are pushed. $n = 6$ means Sw2 and Sw1 are pushed. $n = 7$ means all are pushed.

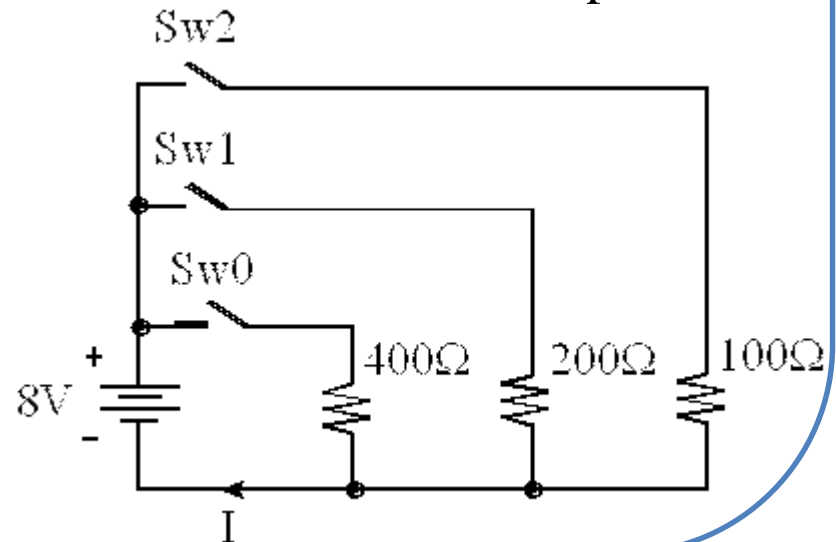Derive a relationship between the current I and the number n . Multiple choice



Review of Electronics (Cont...)

400	200	100	0	0	0	0	0	0	0	No- Current
400	200	100	1	0	0	400	0	0	400	0.02
400	200	100	0	1	0	0	200	0	200	0.04
400	200	100	1	1	0	400	200	0	133.3333	0.06
400	200	100	0	0	1	0	0	100	100	0.08
400	200	100	1	0	1	400	0	100	80	0.1
400	200	100	0	1	1	0	200	100	66.66667	0.12
400	200	100	1	1	1	400	200	100	57.14286	0.14

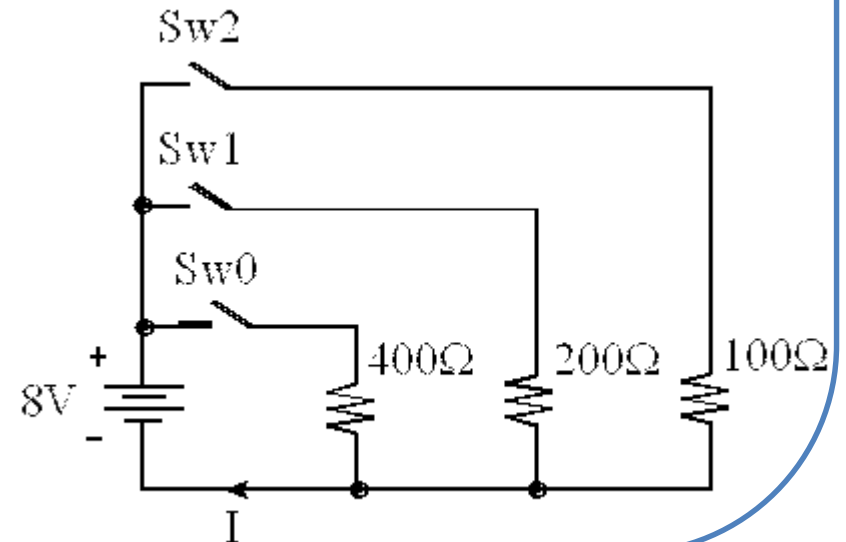

Review of Electronics (Cont...)

EXAMPLE : ANALOG INPUT = 6.428V, REFERENCE = 10.000V

