

# CS222: Computer Architecture

Instructor:

Dr Ahmed Shalaby <http://bu.edu.eg/staff/ahmedshalaby14#>

الاحترام - الادب - الاخلاق  
الطالب - المعيد - الدكتور

# Verilog HDL

- **FPGA.**
- **Verilog**
  - Introduction to Verilog HDL.
  - Verilog Basics.
  - Combinational modeling.
  - Sequential modeling.

# Digital System Implementation Spectrum


Hardware  
ASIC

## Reconfigurable Architectures
 
### Software

- $\mu$ Processor
- $\mu$ Controller
- DSP

- CPLD
- FPGA
- Customized Processors
- Coarse Grain
- Reconfigurable Array



# Reconfigurable Architectures

- Filed Programmable Devices
  - ❑ Simple
    - **Programmable logic Devices ( PLD )**
  - ❑ Complex
    - **Complex Programmable Logic Devices ( CPLD )**
    - **Field Programmable Gate Array ( FPGA )**


# Programmable logic Devices

## Logic Functions

$$y = (a \& b \& c)$$

$$x = (a \& b \& c) \mid (\bar{b} \& \bar{c})$$

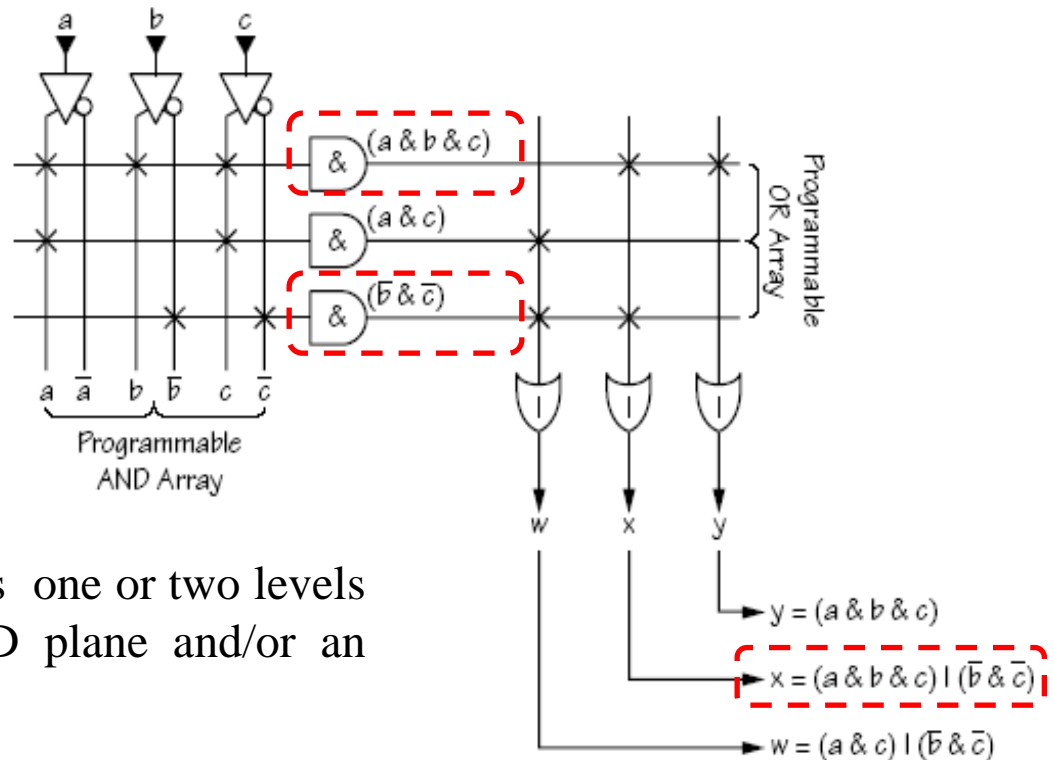
$$w = (a \& c) \mid (\bar{b} \& \bar{c})$$



Relatively small FPD that contains one or two levels of programmable logic—an AND plane and/or an OR plane.


 
# Complex PLD

- Arrangement of multiple SPLD-like blocks on a single chip.
- Programmable PLD Blocks, Programmable Interconnects



  
# FPGA

- Logic Functions implemented in Look Up Table.
- Flip-Flops (Register).
- Multiplexers


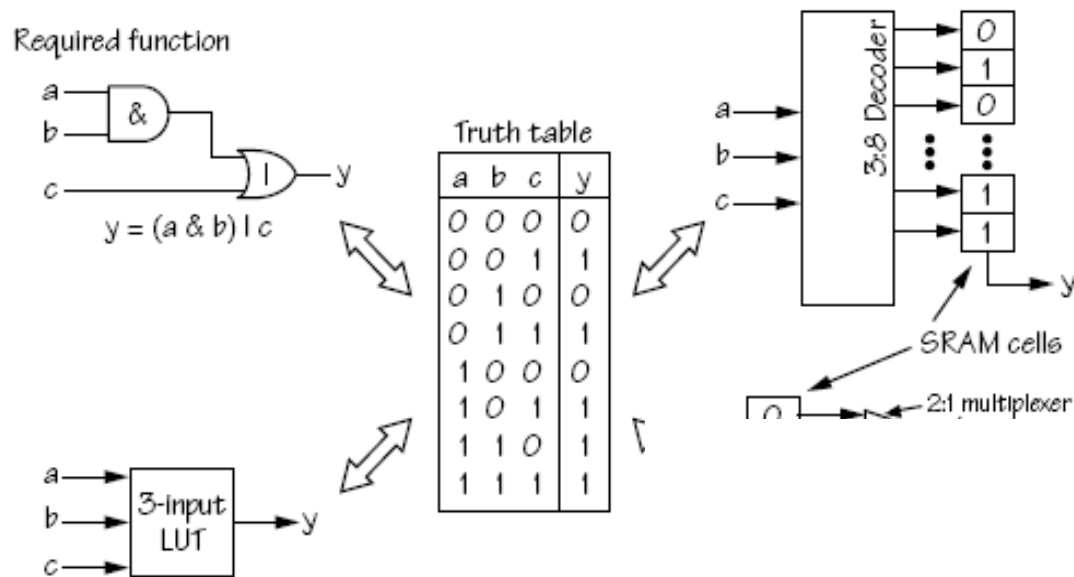
# FPGA - LUT


- LUT contains Memory Cells to implement small logic functions
- Each cell holds '0' or '1'.
- Programmed with outputs of Truth Table
- Inputs select content of one of the cells as output
- Configured by re-programmable **SRAM memory cells**




 
# General FPGA Layout

- Composed of:
  - **LEs** (Logic elements): perform logic
    - **LUTs** (lookup tables): perform combinational logic
    - **Flip-flops**: perform sequential logic
    - **Multiplexers**: connect LUTs and flip-flops)
  - **IOEs** (Input/output elements): interface with outside world
  - **Programmable interconnection**: connect LEs and IOEs
- Some FPGAs include other building blocks such as multipliers and RAMs



# FPGA – Design Flow


- Reading Specs and Define the full definition of the problem
- Detailed Specs and architecture of the project.
- Behavioral design
  - High level Description of Logic Design.
  - Schematic.
  - State machine.
  - Flow chart.
  - Block diagram.
- Function Verification ( Pre-Synthesis Simulation ).
- Synthesis - Target FPGA Device.
  - Place
  - Route
- Timing Verification ( Post-Synthesis Simulation ).
- Device Programming.

Altera's Quartus II

# Synthesis

- Synthesis is an automatic method of converting a higher level of abstraction (RTL) to a lower level of abstraction (gate level Netlists).
- Synthesis produces technology-specific implementation from technology-independent HDL description.
- Not all HDL can be used for synthesis. There are the HDL subset for synthesis and synthesis style description.
- Synthesis is very sensitive to how the HDL is written
  - Good design is still the responsibility of the designer.
  - Junk in - junk out

# System Level Synthesis

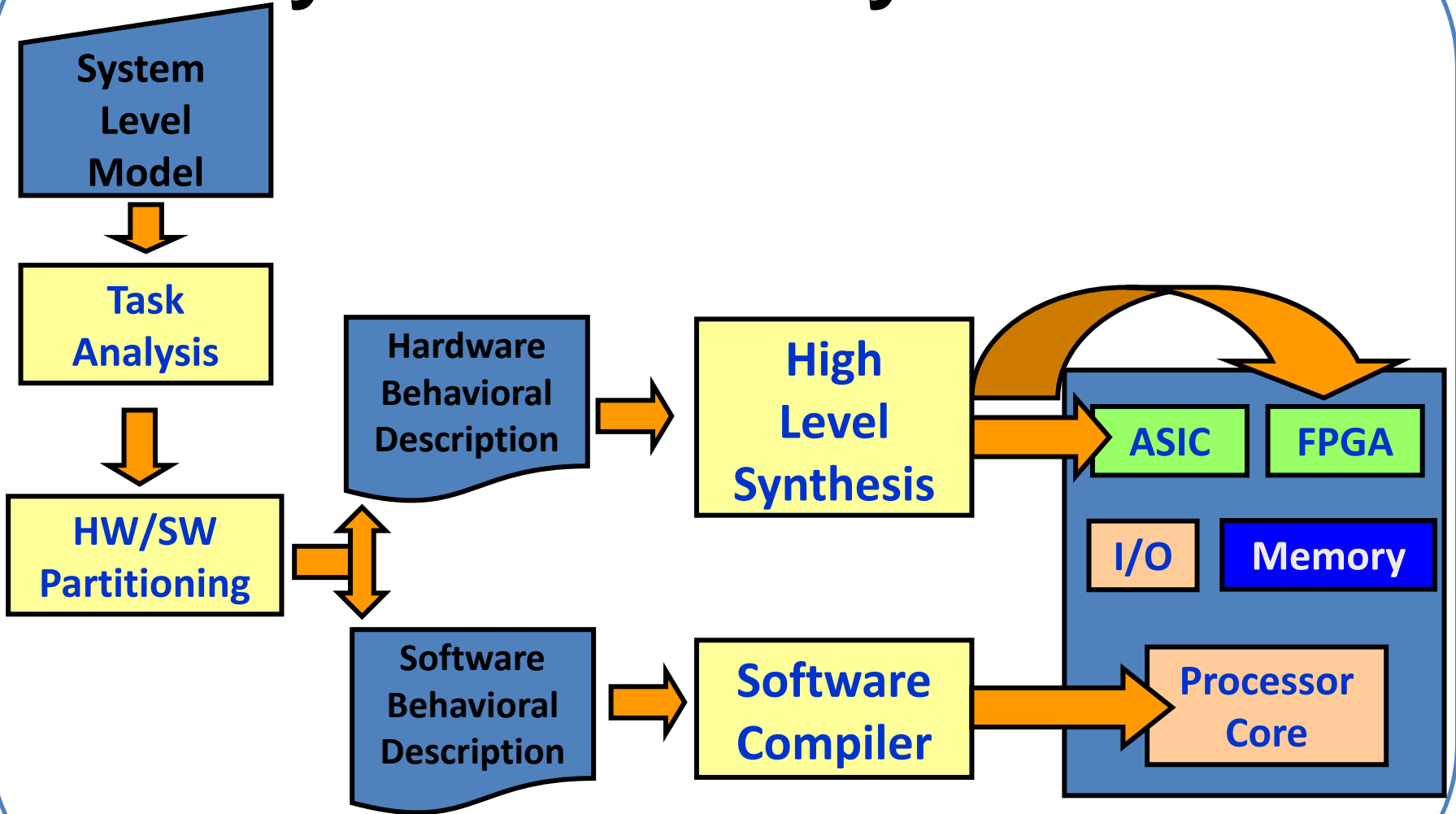




# Verilog

# Overview

# Verilog Overview

- To become familiar with the basic features of the Verilog Hardware Description Language.
- Topics:
  - Modules.
  - Ports.
  - Continuous assignments.
  - Hierarchy.
  - Logic Values.
  - Test fixtures.
  - Initial blocks.

## Modules and Ports

 

```
// An and-or-invert gate
```


```
module AOI (A, B, C, D, F);  
  input A, B, C, D;  
  output F;
```

```
// The function of the AOI module is described here...
```

```
endmodule
```



## Continuous Assignment

 

// An and-or-invert gate

```
module AOI (A, B, C, D, F);  
  input A, B, C, D;  
  output F;  
  
  assign F = ~((A & B) | (C & D));  
  
endmodule
```

&	and
	or
~	not

## Rules and Regulations

All definitions and statements go inside a module

```
// An and-or-invert gate
```

A comment

```
module AOI (A, B, C, D, F);
```

```
    input A, B, C, D;
```

Case sensitive names

```
    output F;
```

; at end of definition/statement

```
    assign F = ~((A & B) | (C & D));
```

```
/*
```

```
These lines are ignored
```

A block comment

```
by the compiler
```

```
*/
```

```
endmodule
```

Lower case keywords

## Single-line vs. Block Comments

```
// Comment out  
// a number of lines  
// using single-line  
// comments
```

```
/* Can nest  
// single-line comments  
// within block comments  
*/
```

```
/* Can't nest  
/* block comments */  
*/
```

Start of comment

End of comment

ERROR!!

# Names

## ? Identifiers

```
AB    Ab    aB    ab    // different!  
G4X$6_45_123$  
Y     Y_    _Y     //different!
```

## ? Illegal!

```
4plus4    $1
```


## ? Escaped identifiers (terminate with white space)

```
\4plus4    \$1    \a+b£$%^&* (
```

## ? Keywords

```
and    default    event    function    wire
```

## Wires

 


```
module AOI (A, B, C, D, F);  
  input A, B, C, D;  
  output F;  
  
  wire F; // The default  
  wire AB, CD, O; // Necessary  
  
  assign AB = A & B;  
  assign CD = C & D;  
  assign O = AB | CD;  
  assign F = ~O;  
  
endmodule
```

**Target (LHS) of *assign* must be a *wire***
 
# Hierarchy

```
module AOI (A, B, C, D, F);  
    ...  
endmodule  
  
module INV (A, F);  
    ...  
endmodule
```



```
module MUX2 (SEL, A, B, F);  
    input SEL, A, B;  
    output F;  
    INV G1 (SEL, SELB);  
    AOI G2 (SELB, A, SEL, B, FB);  
    INV G3 (FB, F);  
endmodule
```

Instances of modules

Ordered mapping

Wires SELB and FB are implicit

## Named Mapping

```
module AOI (A, B, C, D, F);
```

```
...
```

```
endmodule
```

```
module INV (A, F);
```

```
...
```

```
endmodule
```

```
module MUX2 (SEL, A, B, F);
```

```
input SEL, A, B;
```


```
output F;
```

```
INV G1 (.A(SEL), .F(SELB));
```

```
AOI G2 (.A(SELB), .B(A), .C(SEL), .D(B), .F(FB));
```

```
INV G3 (.F(F), .A(FB));
```

```
endmodule
```

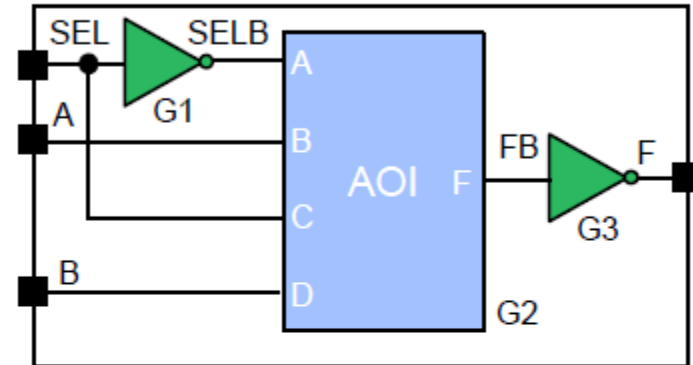

Named mapping

Order doesn't matter

# Primitives

## ? Gates

+ and, nand, or, nor, xor, xnor, buf, not

Built in

## ? Pulls, tristate buffers


+ pullup, pulldown, bufif0, bufif1, notif0, notif1

## ? Switches

+ cmos, nmos, ... tran, ...

```
module MUX2 (SEL, A, B, F);  
  input SEL, A, B;  
  output F;  
  not G1 (SELB, SEL);  
  AOI G2 (SELB, A, SEL, B, FB);  
  not (F, FB);  
endmodule
```


Instances of primitives

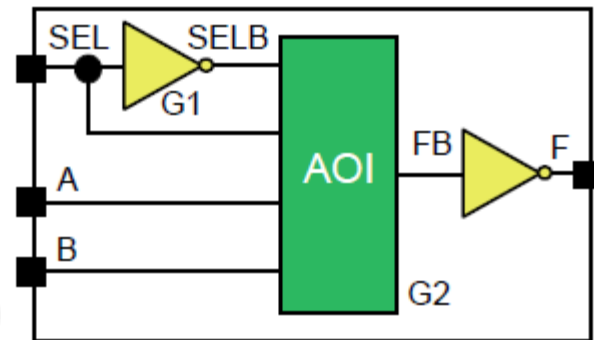

Instance name optional




## Quiz 1

 

```
module ANDOR (
```

```
endmodule
```


## Quiz 1 – Solution

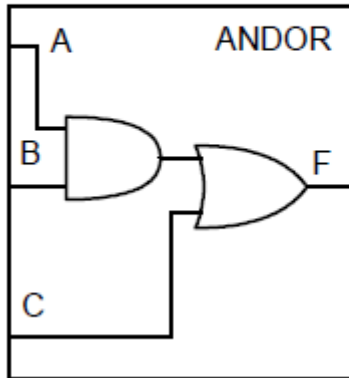

```
module ANDOR (A, B, C, F);  
  input A, B, C;  
  output F;  
  
  assign F = (A & B) | C;  
endmodule
```

```
module ANDOR (A, B, C, F);  
  input A, B, C;  
  output F;  
  wire AB;  
  
  assign AB = A & B;  
  assign F = AB | C;  
endmodule
```

## Quiz 2

 


```
module LOGIC (
```

```
endmodule
```

---

## Quiz 2 – Solution

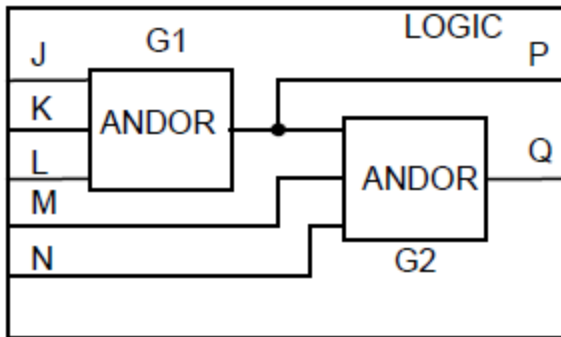


```
module LOGIC (J, K, L, M, N, P, Q);
    input  J, K, L, M, N;
    output P, Q;

    ANDOR G1 (J, K, L, P);
    ANDOR G2 (P, M, N, Q);
endmodule
```

```
module LOGIC (J, K, L, M, N, P, Q);
    input  J, K, L, M, N;
    output P, Q;

    ANDOR G1 (.A(J), .B(K), .C(L), .F(P));
    ANDOR G2 (.A(P), .B(M), .C(N), .F(Q));
endmodule
```

## Vector Ports

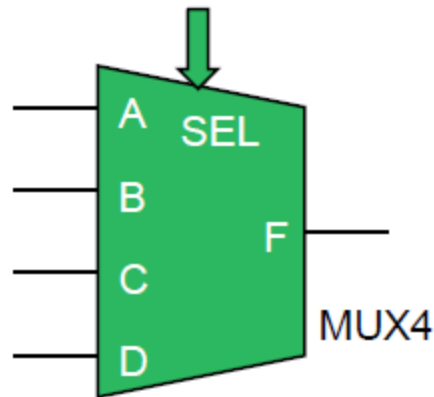

```
module MUX4 (SEL, A, B, C, D, F);  
  input [1:0] SEL;  
  input      A, B, C, D;  
  output     F;  
  
  // ...  
endmodule
```

Separate input declarations

## Verilog Logic Values

? Verilog logic values are:

- † 1'b0 - logic 0, false, ground
- † 1'b1 - logic 1, true, power
- † 1'bX - unknown or uninitialised
- † 1'bZ - high impedance, floating

? A vector is a row of logic values

```
reg [7:0] V;  
V = 8'bXXXX0101;
```


V:

X	X	X	X	0	1	0	1
7	6	5	4	3	2	1	0


```
V[7] = 1'b0;  
V[6] = B & V[0];
```

## Part Selects


```
reg [0:7] V;  
reg [3:0] W;
```

 

```
W = V[2:5];
```

 

```
W[1:0] = 2'b11;
```

 


```
W[0:1] = 2'b11;
```

wrong direction - illegal

```
W[2:2] = 1'b1;
```

OK

# Test Fixtures

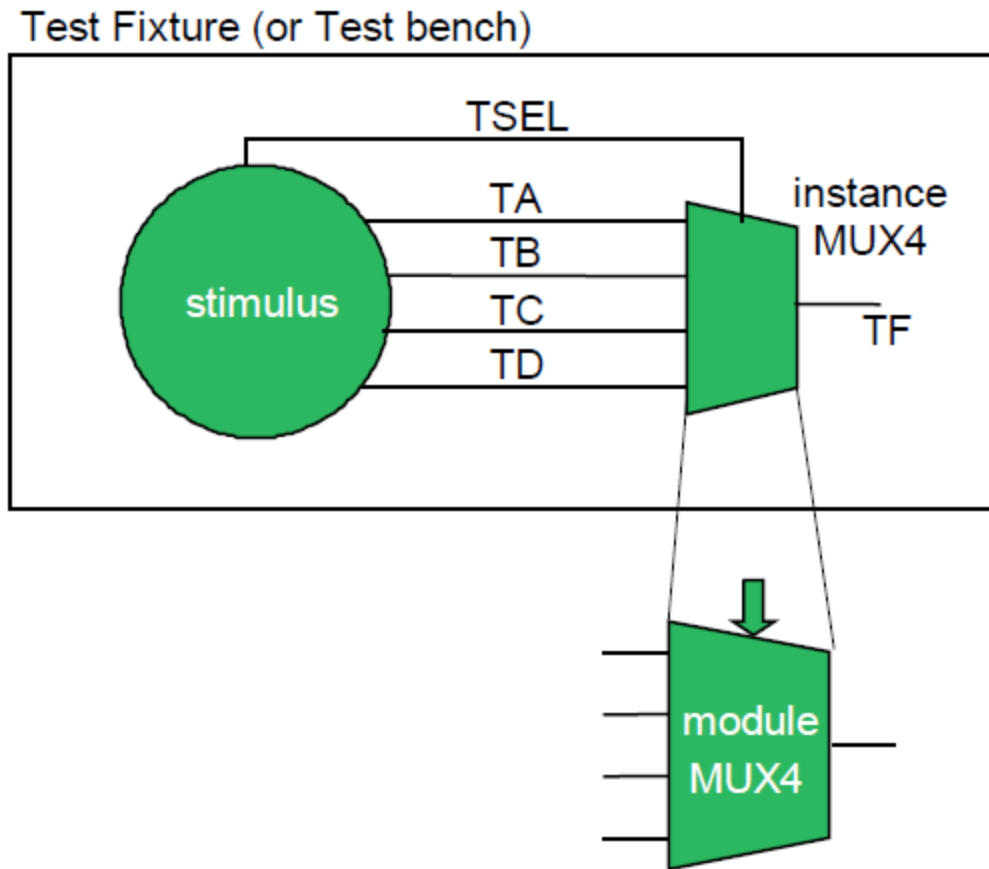



## Outline of Test Fixture for MUX4

```
module MUX4TEST;
```

No ports

```
...
```

Declarations

```
initial
```

```
...
```

Describe stimulus

```
MUX4 M (  
  .SEL (TSEL) ,  
  .A (TA) ,  
  .B (TB) ,  
  .C (TC) ,  
  .D (TD) ,  
  .F (TF) );
```

Instance of module being tested

```
initial
```

```
...
```

Write out Results

```
endmodule
```

# Initial Blocks


```
initial // Stimulus
begin
    TSEL = 2'b00;
    #10 TA = 0;
    #10 TA = 1;
    #10 TSEL = 2'b01;
    #10 TB = 0;
    ...
end
```

Shorthand for 1'b0

Executes once top to bottom

Procedural delay

Procedural assignments

 

# Registers

```
module MUX4TEST;

  reg TA, TB, TC, TD;
  reg [1:0] TSEL;

  wire TF;


  initial // Stimulus
  begin
    TSEL = 2'b00;
    #10 TA = 0;
    #10 TA = 1;
    #10 TSEL = 2'b01;
    #10 TB = 0;
    ...
  end

  MUX4 M (.SEL(TSEL), .A(TA), .B(TB), .C(TC), .D(TD), .F(TF));

  ...
endmodule
```

*A reg is a kind of register*

 *Target (LHS) of procedural assignment must be a register*



# \$monitor

? Can use \$monitor to write a table of results

```
module MUX4TEST;
```

```
  reg TA, TB, TC, TD;  
  reg [1:0] TSEL;
```

```
  wire TF;
```

```
  initial // Stimulus  
    ...
```

```
  MUX4 M (.SEL(TSEL), .A(TA), .B(TB), .C(TC), .D(TD), .F(TF));
```

```
  initial // Analysis  
    $monitor($time,, TSEL,, TA, TB, TC, TD,, TF);
```

```
endmodule
```

0	0	XXXX	X
10	0	0XXX	0
20	0	1XXX	1
30	1	1XXX	X
40	1	10XX	0
...			

begin-end not needed

System function

writes a space

System task

## The Complete Test Fixture

```
module MUX4TEST;
  reg TA, TB, TC, TD;
  reg [1:0] TSEL;
  wire TF

  initial
  begin
    SEL = 2'b00;
    #10 TA = 0;
    #10 TA = 1;
    #10 TSEL = 2'b01;
    #10 TB = 0;
    #10 TB = 1;
    ...
  end
  MUX4 M (.SEL(TSEL), .A(TA), .B(TB), .C(TC), .D(TD), .F(TF));
  initial
    $monitor($time,,TSEL,,TA,TB,TC,TD,,F);
endmodule
```

Declarations

Concurrent statements

# Verilog Basics

# Verilog Basics

- To become familiar with **more** basic features of the Verilog Hardware Description Language.
- Topics:
  - Numbers.
  - Formatted output.
  - Timescales.
  - System Functions ( \$stop and \$finish ).
  - Wires and Regs.
  - Operators and expressions.
  - `define and `include.
  - Conditional compilation.
  - Parameters.
  - Hierarchical names.

## Numbers

```
reg [7:0] V;
```

Numbers are not case sensitive

```
V = 8'b111XX000;
```

Binary 111XX000

```
V = 8'B111X_X000;
```

\_ is ignored in numbers

Binary 111XX000

```
V = 8'hFF;
```

Hex = 8'b1111\_1111

```
V = 8'o77;
```

Leading 0's are added

Octal = 8'b00\_111\_111

```
V = 8'd10;
```

Decimal = 8'b0000\_1010



## “Disguised” Binary Numbers

```
reg [7:0] V;
```

Not binary!

```
V = 10;
```

$10 = 'd10 = 32'd10 = 32'b1010 \rightarrow 8'b00001010$

```
V = -3;
```

$-3 = 32'hFF\_FF\_FF\_FD \rightarrow 8'b1111\_1101$

```
V = "A";
```

$ASCII = 8'd65 \rightarrow 8'b01000001$

## Formatted Output

```
reg [3:0] TA, TB, TC, TD;  
reg [1:0] TSEL;  
wire [3:0] TF;
```

```
initial // Write heading and table of results  
begin  
    $display("           ",  
             "Time TSEL TA    TB    TC    TD    TF");  
    $monitor("%d %b  %b  %b  %b  %b  %b",  
            $time, TSEL, TA, TB, TC, TD, TF);  
end
```

Time	TSEL	TA	TB	TC	TD	TF
0	00	0001	0010	0100	1000	0001
10	00	1110	0010	0100	1000	1110
20	01	1110	0010	0100	1000	0010
30	01	1110	1101	0100	1000	1101

# Formatting

## ? Special formatting strings:

- † %b        binary
- † %o        octal
- † %d        decimal
- † %h        hexadecimal
- † %s        ASCII string
- † %v        value and drive strength
- † %t        time (described later)
- † %m        module instance
- † \n        newline
- † \t        tab
- † \"        \"
- † \nnn      nnn is octal ASCII value of character
- † \\        \

## Formatting Text

- ? **One format string with correct number of values**

```
$display ("%b %b", Expr1, Expr2);
```

- ? **Two format strings**

```
$display ("%b", Expr1, " %b", Expr2);
```

Equivalent

- ? **Too many values**

```
$display ("%b", Expr1, Expr2);
```

Expr2 is written in decimal

- ? **Too few values**

```
$display ("%b %b %b", Expr1, Expr2);
```

ERROR!!

## Always

### ? Clock generator

```
module ClockGen (Clock);  
    output Clock;  
    reg Clock;  
  
    initial  
        Clock = 0;  
  
    always  
        #5 Clock = ~Clock;  
  
endmodule
```

Outputs may be regs

Clock 

### Binary count

```
initial  
    Count = 0;  
  
always #10  
    Count = Count + 1;
```

## Using Registers

- ? **Necessary when assigning in initial or always**
- ? **Only needed when assigning in initial or always**
- ? **Outputs can be regs**

```
module UsesRegs (OutReg);  
  output [7:0] OutReg;  
  reg      [7:0] OutReg;  
  
  reg R;  
  
  initial  
    R = ...  
  
  always  
    OutReg = 8'b...  
  
endmodule
```

Declarations agree

Must be registers

## Using Nets

```
module UsesWires (InWire, OutWire);
```

```
  input  InWire;
```

```
  output OutWire;
```

```
  wire [15:0] InternalBus;
```

```
  AnotherModule U1 (InternalBus, ...);
```

```
  YetAnother    U2 (InternalBus, ...);
```

```
  not (ImplicitWire, InWire);
```

```
  and (AnotherWire, ImplicitWire, ...);
```

```
  assign OutWire = ...
```

```
endmodule
```

inputs, must be nets  
outputs may be nets

Declare internal vectors


Instance outputs must  
connect to nets

assign requires nets
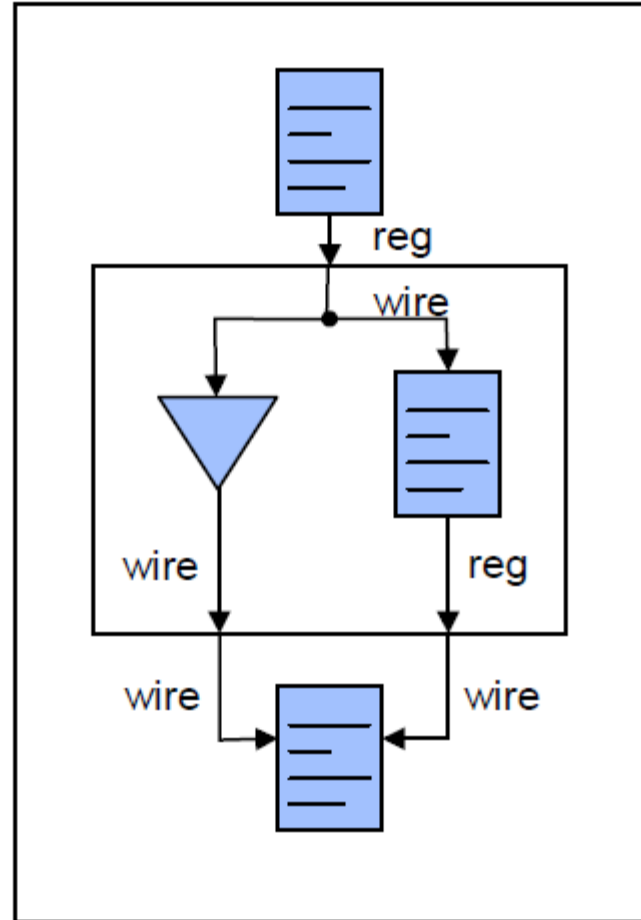
## Module Boundaries

```
module Top;  
  reg R;  
  wire W1, W2;  
  Silly S (.InWire(R), .OutWire(W1),  
          .OutReg(W2));  
  ...  
endmodule
```


```
module Silly (InWire, OutWire,  
             OutReg);  
  input InWire;  
  output OutWire, OutReg;  
  reg OutReg;  
  initial OutReg = InWire;  
  assign OutWire = InWire;  
endmodule
```




 
## Wire vs. Reg – Summary

- ? **You *must* use registers**
  - † when assigning in initial statements
  - † when assigning in always statements
- ? **You *must* use nets**
  - † when assigning in continuous assignments
  - † for inputs and inouts
  - † when connecting module or primitive instance outputs or inouts
- ? **Wires are structural; regs are behavioral**



## Bitwise and Reduction Operators

&	Bitwise and / reduction and
	Bitwise or / reduction or
^	Bitwise xor / reduction xor
~	Bitwise not

For example:

<code>4'b0101 &amp; 4'b1100</code>	<code>4'b0100</code>
<code>4'b0101   4'b1100</code>	<code>4'b1101</code>
<code>4'b0101 ^ 4'b1100</code>	<code>4'b1001</code>
<code>&amp;4'b0101</code>	<code>1'b0</code>
<code> 4'b0101</code>	<code>1'b1</code>
<code>^4'b0101</code>	<code>1'b0</code>
<code>~4'b1100</code>	<code>4'b0011</code>

Parity

Ones complement

## Logical Operators

&&	Logical and
	Logical or
!	Logical not

```
assign f = !((a && b) || (c && d));
```

```
if ( p == q && r == s )  
    ...
```

Non-zero values are considered TRUE in logical expressions:

4'b0101 && 4'b1100	1'b1
!4'b1100	1'b0
!4'b0000	1'b1
4'b0XX0	1'b0
4'b01X0	1'b1

```
if (Expression)  
    $display("Expression is non-zero");  
else if (!Expression)  
    $display("Expression is zero");  
else  
    $display("Expression is unknown");
```

## Comparison Operators

Use to describe logic

Use in test fixtures

==	Logical Equality
!=	Logical Inequality
===	Case Equality
!==	Case Inequality

Logical Equality				
==	0	1	X	Z
0	1	0	X	X
1	0	1	X	X
X	X	X	X	X
Z	X	X	X	X

Case Equality				
===	0	1	X	Z
0	1	0	0	0
1	0	1	0	0
X	0	0	1	0
Z	0	0	0	1

```
if (A == 1'bx)    // Always false!
    F = 1'bx;    // Never executed!
```

## Arithmetic Operators


+	Add
-	Subtract
*	Multiply
/	Divide
%	Modulus

## Concatenation

### ? Concatention operator “{ }” ...

```
reg [7:0] A, B;  
reg [15:0] F;  
...  
F = {A, B};
```

{A,0} is illegal

 

### ? On left-hand side of assignment

```
wire COUT, CIN;  
wire [15:0] A, B, SUM;  
assign {COUT, SUM} = A + B + CIN;
```

# Replication

{N{A}}      Replication

{64{1'b1}}

{I+J{A}}

{32{A,B}}


```
reg [7:0] byte;  
reg [15:0] word;
```

Concatenation

```
word = { {8{byte[7]}}, byte };
```

Replication

Sign extension

 

## Parameters

```
module M;
```

Parameters are declared in a module

```
    parameter Width = 8;
```

```
    parameter Add    = 8'b00111100,  
           Sub      = 8'b00010000,  
           Load     = 8'b01010000,  
           Store    = 8'b11010000,  
           Jump     = 8'b00101111,  
           Halt     = 8'b11111111;
```

Constant values

```
    parameter error_message = "Gone wrong again";
```

Any Verilog "type"



## Using Parameters

### ? Sizes of regs and wires

```
reg [Width-1:0] Bus;  
wire [Width-1:0] BusWire;
```

### ? “Magic Numbers”

```
always @(Bus)  
    if (Bus == Halt)  
        $display("%s", error_message);
```

Not: Bus == 8'b11111111

### ? Size of Numbers

```
assign BusWire = Enable ? Bus : {Width{1'bz}};
```

Replication

Width'bz is illegal