

CS222: Computer Architecture

Instructors:

Dr Ahmed Shalaby <http://bu.edu.eg/staff/ahmedshalaby14#>

الاحترام - الادب - الاخلاق
الطالب - المعيد - الدكتور

Review: Instruction Formats

R-Type

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

J-Type

op	addr
6 bits	26 bits

R-Type

- *Register-type*
- 3 register operands:
 - rs, rt: source registers
 - rd: destination register
- Other fields:
 - op: the *operation code* or *opcode* (0 for R-type instructions)
 - funct: the *function*
with opcode, tells computer what operation to perform
 - shamt: the *shift amount* for shift instructions, otherwise it's 0

R-Type



R-Type Examples

Table B.2 R-type instructions, sorted by funct field—Cont'd

Funct	Name	Description	Operation
100000 (32)	add rd, rs, rt	add	[rd] = [rs] + [rt]
100001 (33)	addu rd, rs, rt	add unsigned	[rd] = [rs] + [rt]
100010 (34)	sub rd, rs, rt	subtract	[rd] = [rs] - [rt]
100011 (35)	subu rd, rs, rt	subtract unsigned	[rd] = [rs] - [rt]

Assembly Code

```
add $s0, $s1, $s2
```

```
sub $t0, $t3, $t5
```

Field Values

op	rs	rt	rd	shamt	funct
0	17	18	16	0	32
0	11	13	8	0	34

6 bits 5 bits 5 bits 5 bits 5 bits 6 bits

Machine Code

op	rs	rt	rd	shamt	funct	
000000	10001	10010	10000	00000	100000	(0x02328020)
000000	01011	01101	01000	00000	100010	(0x016D4022)

6 bits 5 bits 5 bits 5 bits 5 bits 6 bits

Name	Register
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25

Note the order of registers in the assembly code:

```
add rd, rs, rt
```



I-Type

- *Immediate-type*
- 3 operands:
 - *rs, rt*: register operands
 - *imm*: 16-bit two's complement immediate
- Other fields:
 - *op*: the opcode
 - Simplicity favors regularity: all instructions have opcode
 - Operation is completely determined by opcode

I-Type



I-Type Examples

100011 (35) lw rt, imm(rs) load word [rt] = [Address]

101011 (43) sw rt, imm(rs) store word [Address] = [rt]

001000 (8) addi rt, rs, imm add immediate [rt] = [rs] + SignImm

Assembly Code

```
addi $s0, $s1, 5
addi $t0, $s3, -12
lw    $t2, 32($0)
sw    $s1, 4($t1)
```

Field Values

op	rs	rt	imm
8	17	16	5
8	19	8	-12
35	0	10	32
43	9	17	4

6 bits 5 bits 5 bits 16 bits

Name	Register
\$0	0
\$at	1
\$v0-\$v1	2-3
\$a0-\$a3	4-7
\$t0-\$t7	8-15
\$s0-\$s7	16-23
\$t8-\$t9	24-25

Note the differing order of registers in assembly and machine codes:

```
addi rt, rs, imm
lw    rt, imm(rs)
sw    rt, imm(rs)
```

Machine Code

op	rs	rt	imm	
001000	10001	10000	0000 0000 0000 0101	(0x22300005)
001000	10011	01000	1111 1111 1111 0100	(0x2268FFF4)
100011	00000	01010	0000 0000 0010 0000	(0x8C0A0020)
101011	01001	10001	0000 0000 0000 0100	(0xAD310004)

6 bits 5 bits 5 bits 16 bits



I-Type Examples

PC-Relative Addressing

```

0x10          beq    $t0, $0, else
0x14          addi   $v0, $0, 1
0x18          addi   $sp, $sp, i
0x1C          jr     $ra
0x20          else: addi   $a0, $a0, -1
0x24          jal   factorial
  
```

Assembly Code


Field Values

	op	rs	rt	imm	
beq \$t0, \$0, else	4	8	0	3	
(beq \$t0, \$0, 3)	6 bits	5 bits	5 bits	5 bits	6 bits

J-Type

- *Jump-type*
- 26-bit address operand (`addr`)
- Used for jump instructions (`j`)

J-Type


 


J-Type Example


Pseudo-direct Addressing

```

 
 
0x0040005C      jal    sum
...
0x004000A0    sum:   add    $v0, $a0, $a1
    
```



Field Values

 


Machine Code

  

Example Program: In Memory

Instruction	
0x23BDFFFC	addi \$sp, \$sp, -4
0xAFBF0000	sw \$ra, 0 (\$sp)
0x20040002	addi \$a0, \$0, 2
0xAF848000	sw \$a0, 0x8000 (\$gp)
0x20050003	addi \$a1, \$0, 3
0xAF858004	sw \$a1, 0x8004 (\$gp)
0x0C10000B	jal 0x0040002C
0xAF828008	sw \$v0, 0x8008 (\$gp)
0x8FBF0000	lw \$ra, 0 (\$sp)
0x23BD0004	addi \$sp, \$sp, -4
0x03E00008	jr \$ra
0x00851020	add \$v0, \$a0, \$a1
0x03E00008	jr \$ra

Data
f
g
y

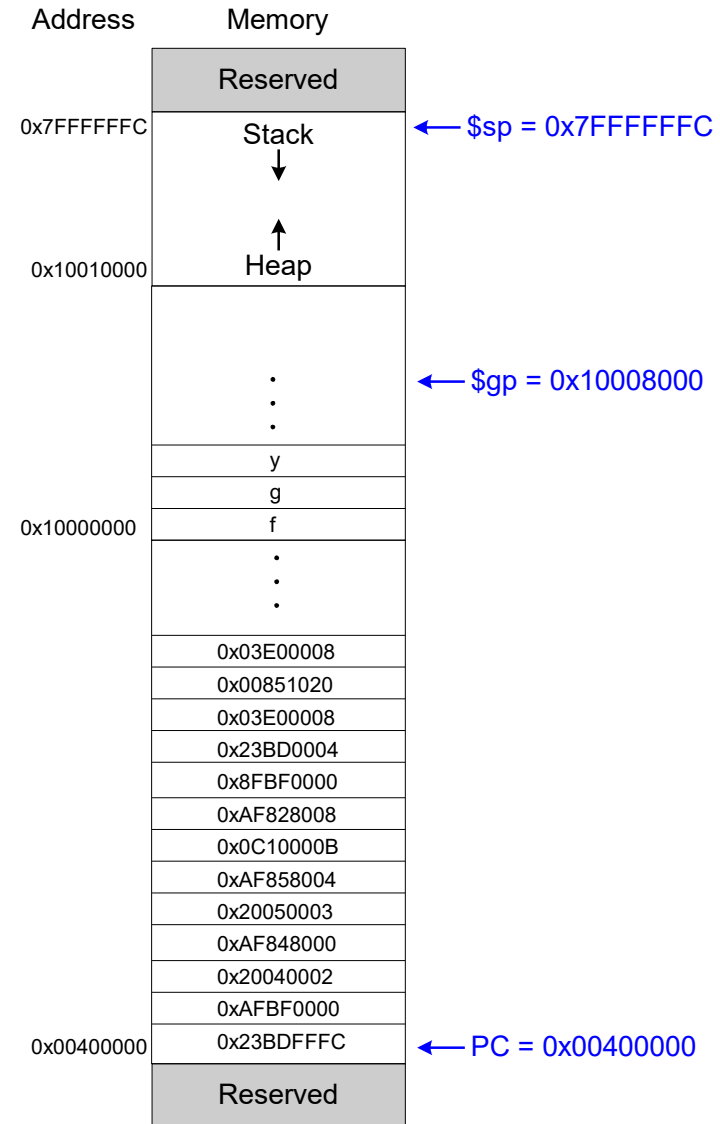




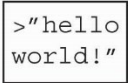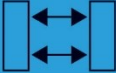
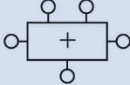

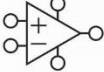


Chapter 7

Digital Design and Computer Architecture, 2nd Edition

David Money Harris and Sarah L. Harris

Chapter 7 :: Topics

- Introduction
- Performance Analysis
- Single-Cycle Processor
- Multicycle Processor
- Pipelined Processor
- Exceptions
- Advanced Microarchitecture

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction

- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons



Microarchitecture

- Multiple implementations for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

Processor Performance

- Program execution time

Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)

- Definitions:
 - CPI: Cycles/instruction
 - clock period: seconds/cycle
 - IPC: instructions/cycle = IPC
- Challenge is to satisfy constraints of:
 - Cost
 - Power
 - Performance


MIPS Processor

- Consider subset of MIPS instructions:
 - R-type instructions: `and`, `or`, `add`, `sub`, `sllt`
 - Memory instructions: `lw`, `sw`
 - Branch instructions: `beq`

Architectural State

- Determines everything about a processor:
 - PC
 - 32 registers
 - Memory

MIPS State Elements

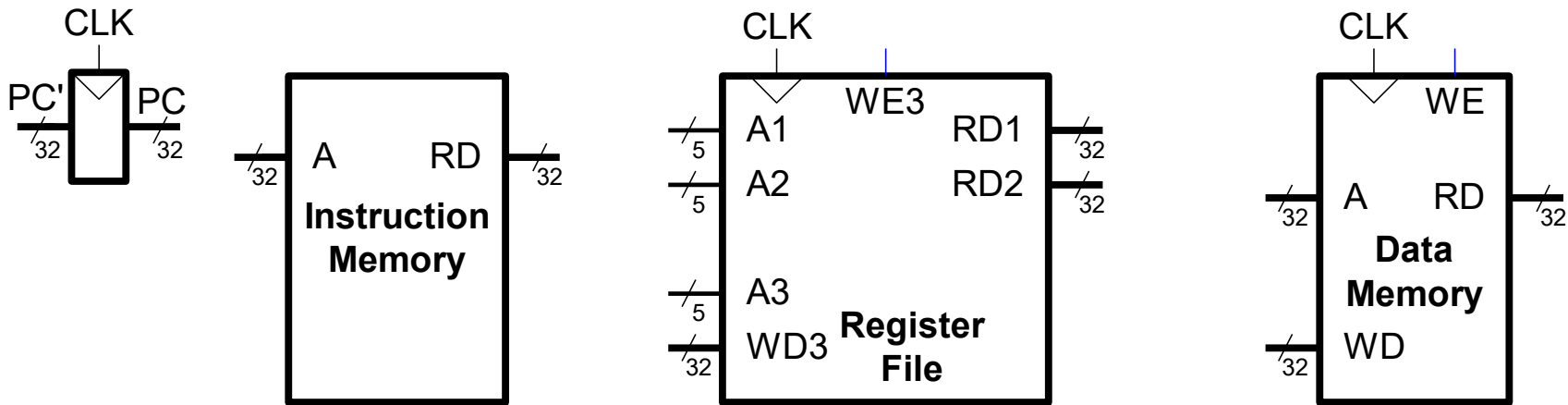


Single-Cycle MIPS Processor

- Datapath
- Control


Single-Cycle Datapath: lw fetch

STEP 1: Fetch instruction

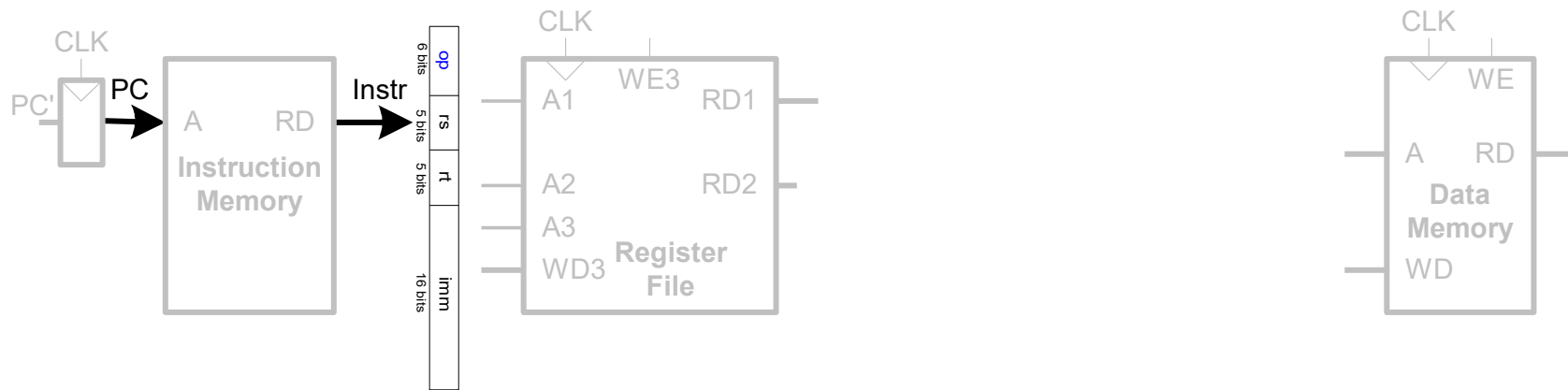


I-Type

lw $rt, imm(rs)$

 

Single-Cycle Datapath: lw Register Read

STEP 2: Read source operands from RF

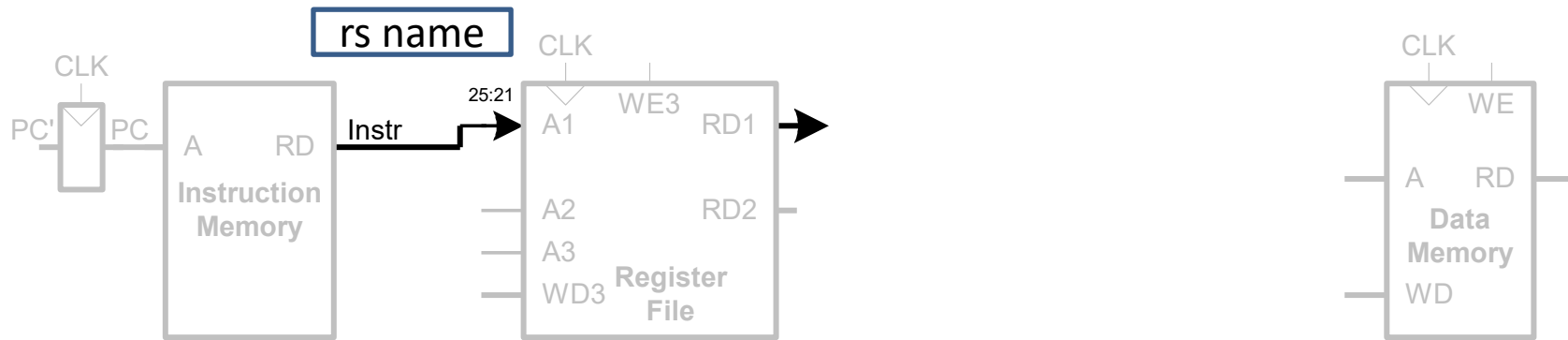


I-Type

$lw\ rt, imm(rs)$



Single-Cycle Datapath: 1_w Immediate


STEP 3: Sign-extend the immediate

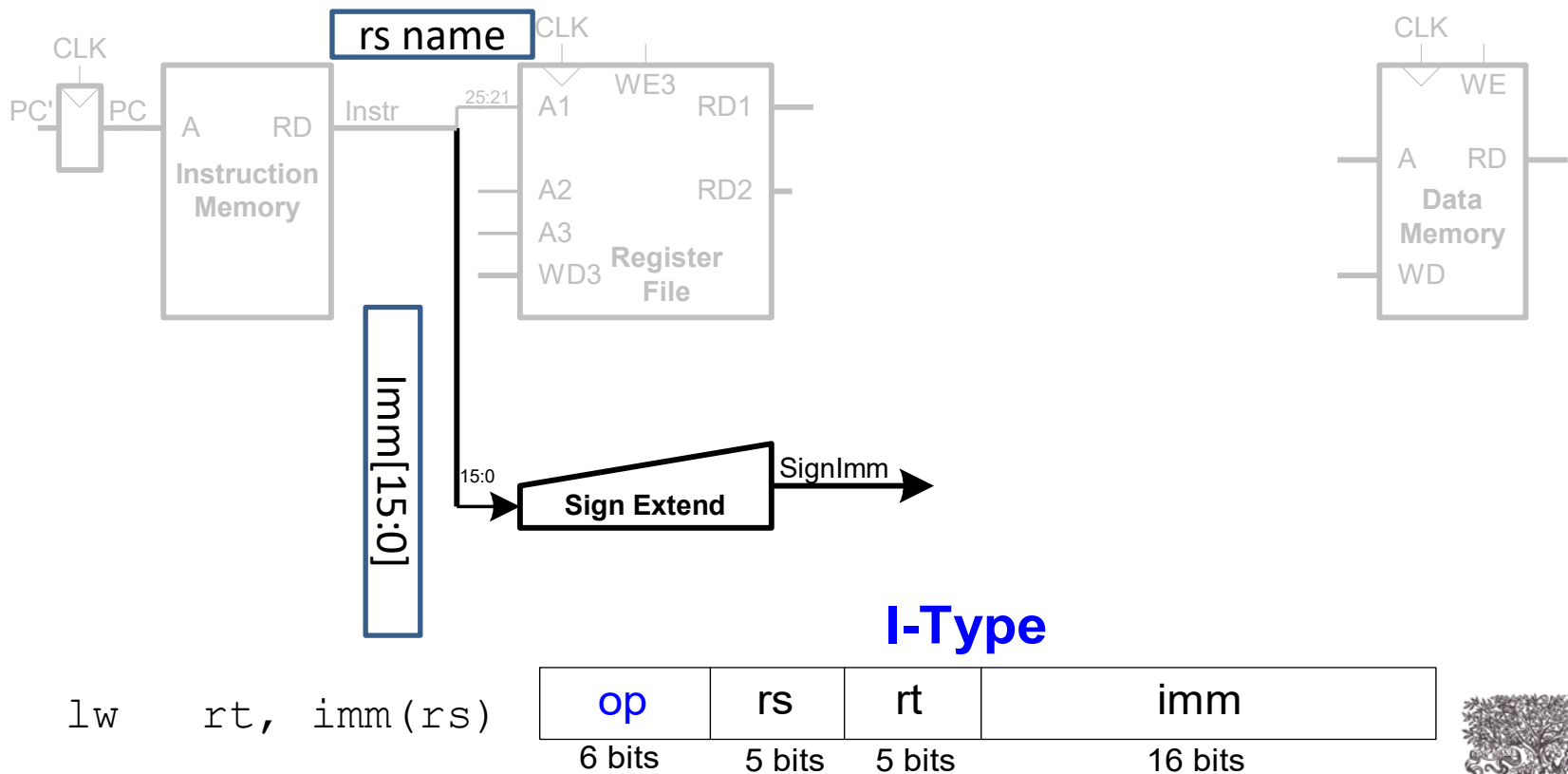

Single-Cycle Datapath: lw address

F _{2:0}	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & ~B
101	A ~B
110	A - B
111	SLT

STEP 4: Compute the memory address

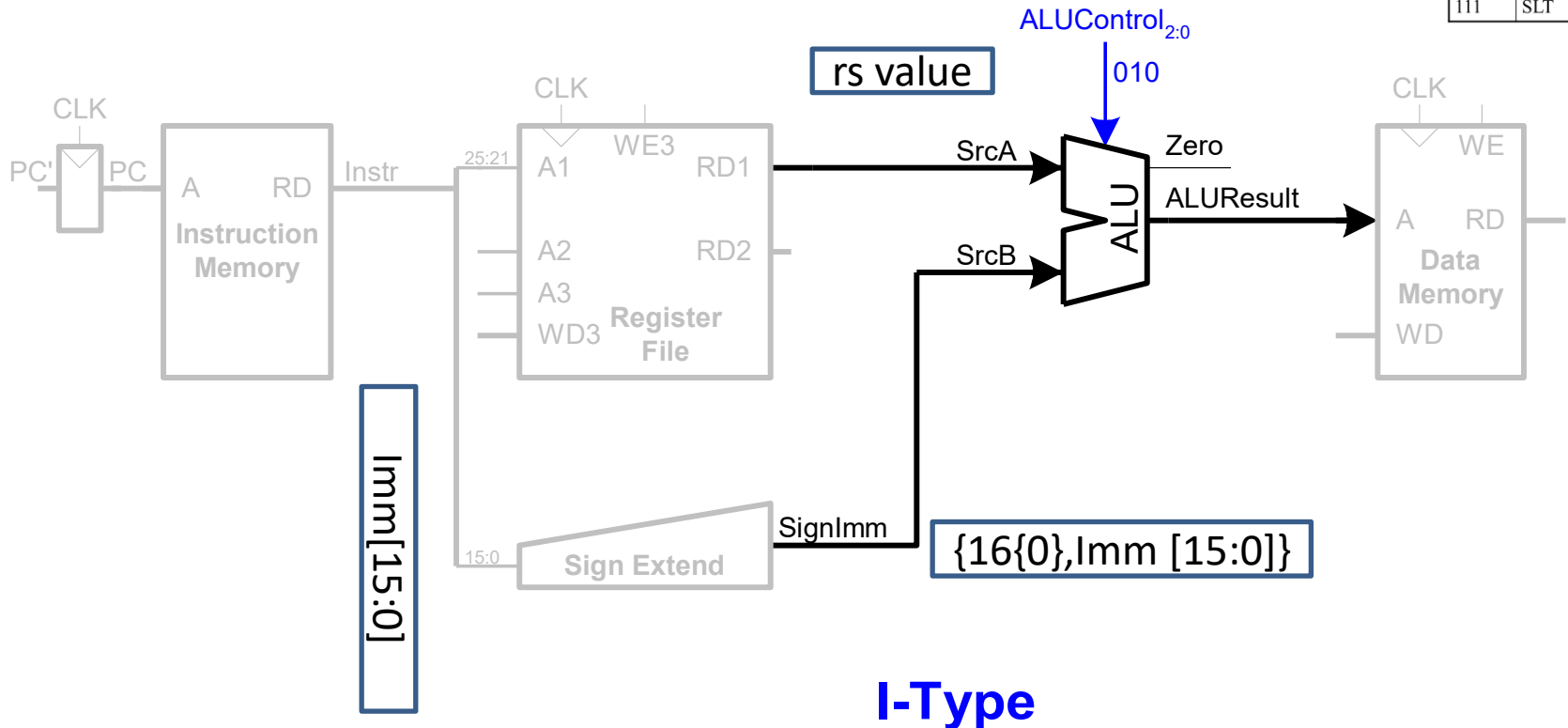


I-Type

`lw rt, imm(rs)`




Single-Cycle Datapath: lw Memory Read

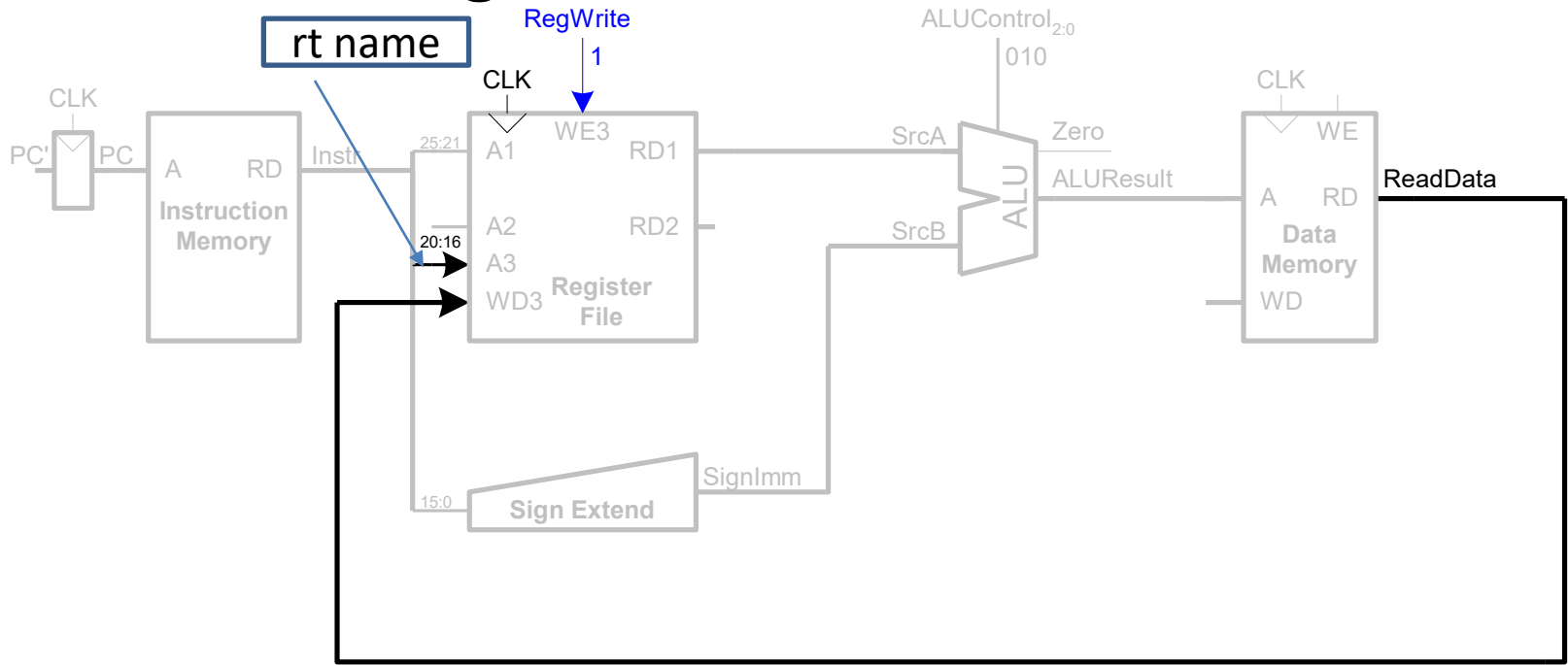- STEP 5:** Read data from memory and write it back to register file




I-Type

 


Single-Cycle Datapath: 1_w PC Increment

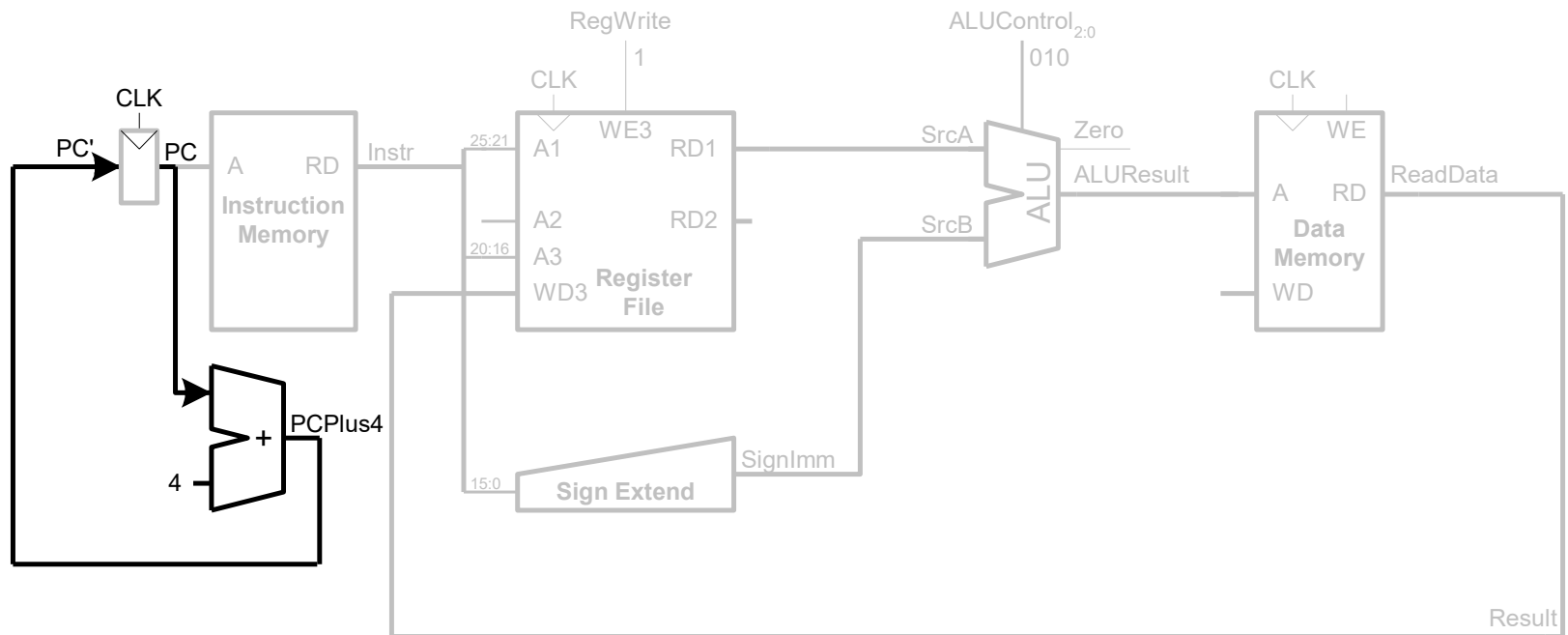STEP 6: Determine address of next instruction



Single-Cycle Datapath: sw

Write data in `rt` to memory

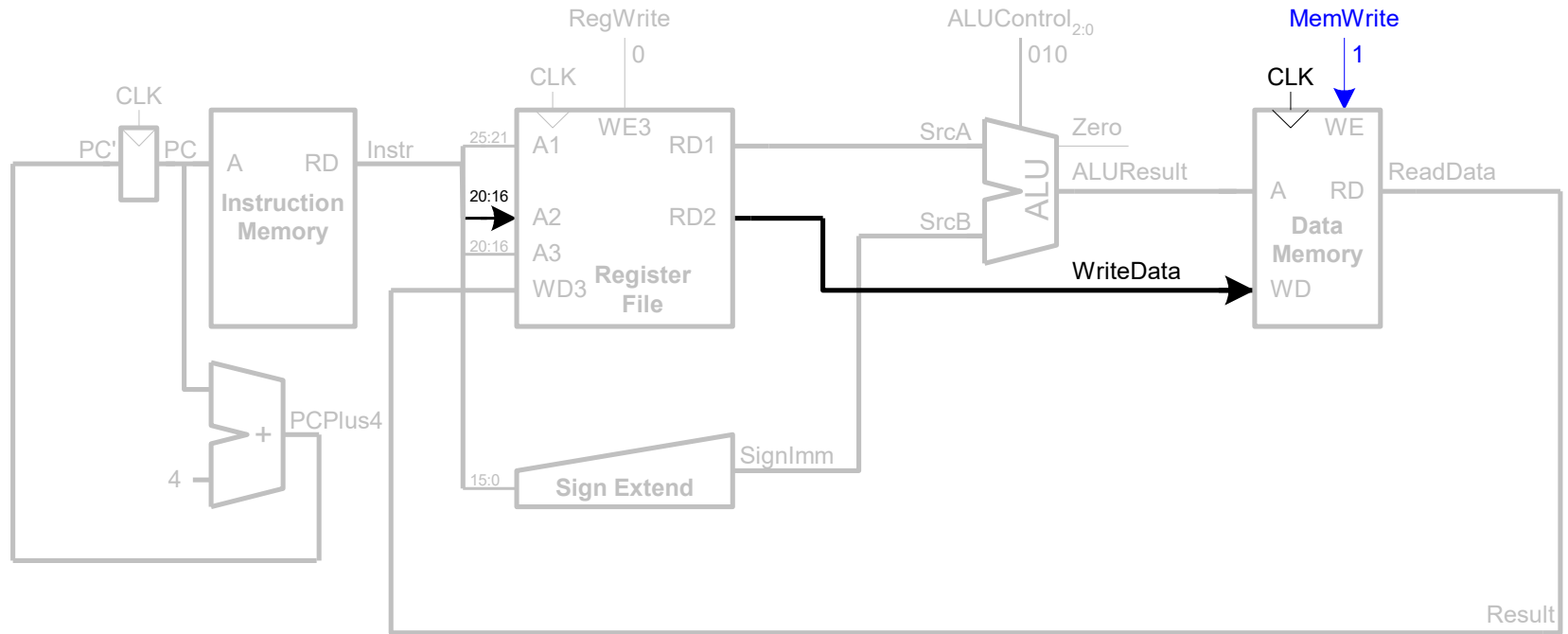

I-Type

sw `rt, imm(rs)`

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits



Single-Cycle Datapath: R-Type


- Read from rs and rt
- Write $ALUResult$ to register file
- Write to rd (instead of rt)

R-Type

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

I-Type


op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

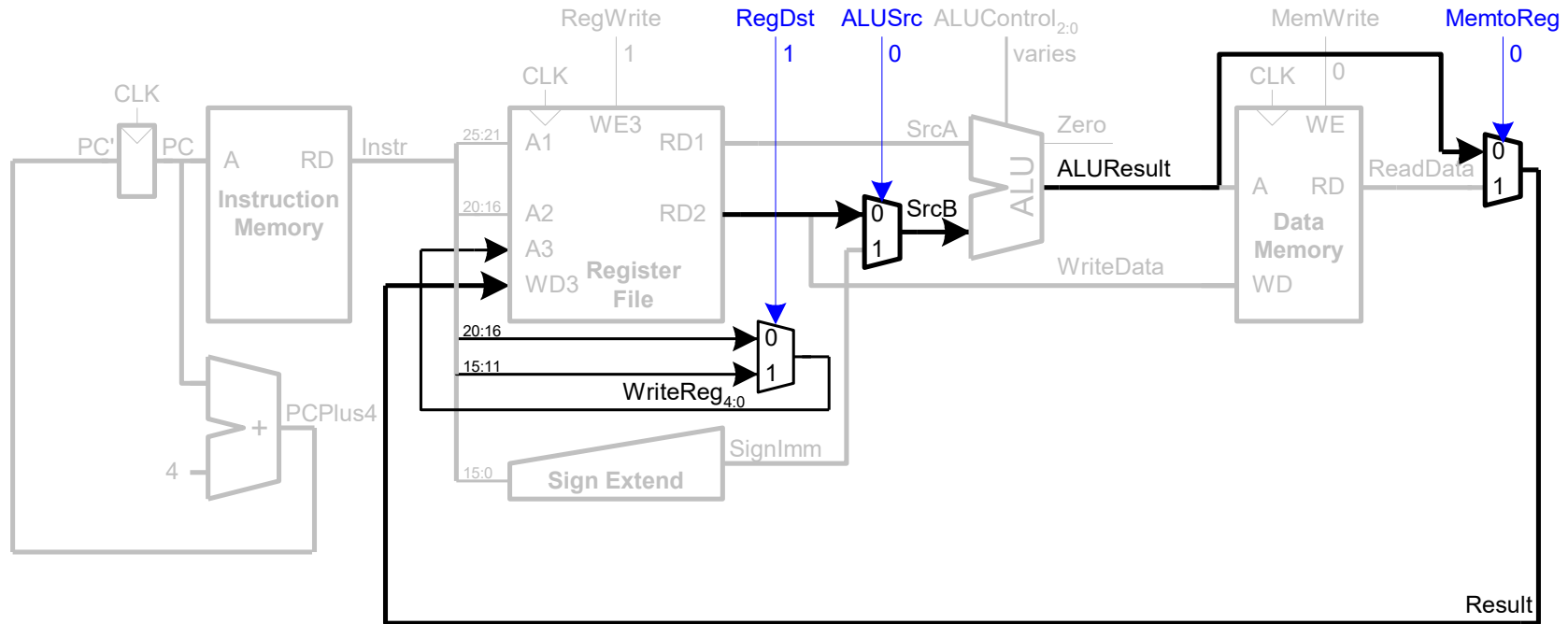

Single-Cycle Datapath: beq

- Determine whether values in `rs` and `rt` are equal
- Calculate branch target address:
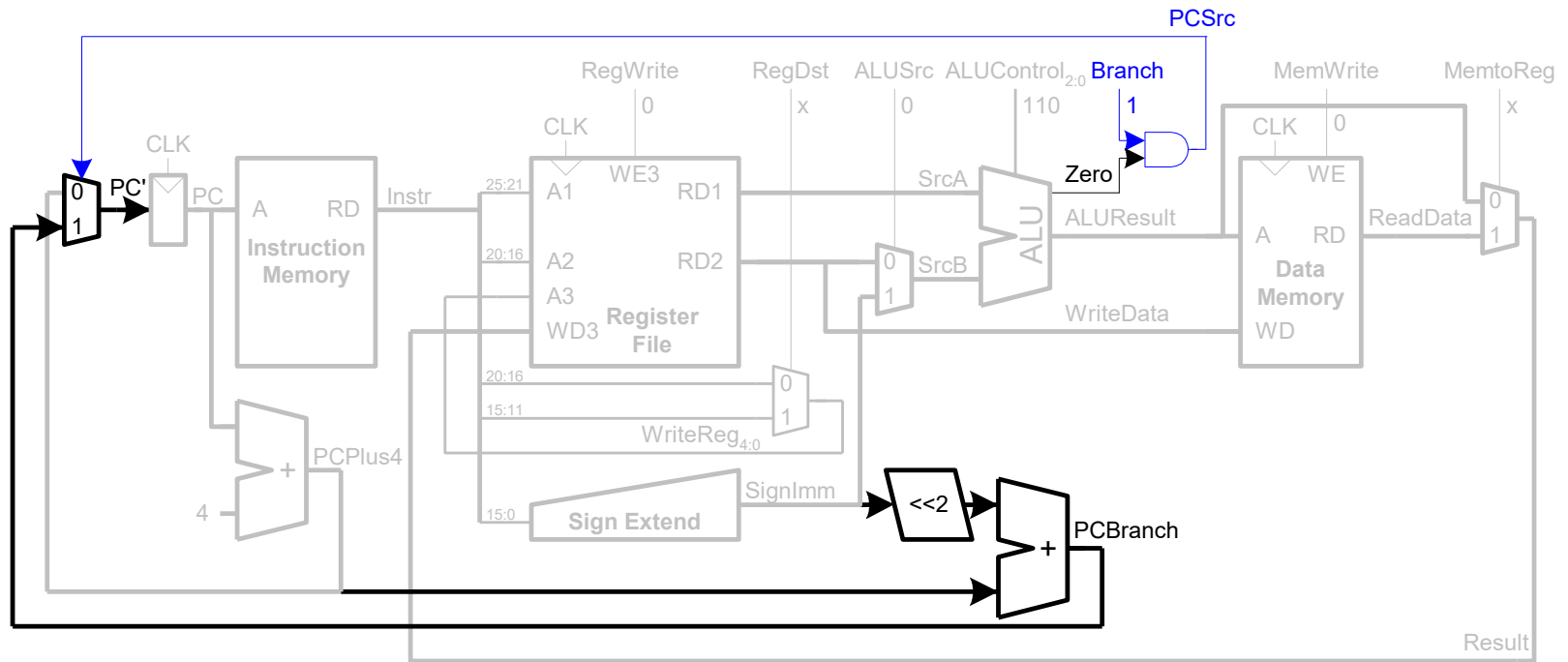
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC}+4)$$



Assembly Code


```
beq $t0, $0, else
(beq $t0, $0, 3)
```

Field Values


op	rs	rt	imm
4	8	0	3
6 bits	5 bits	5 bits	5 bits




Single-Cycle Processor

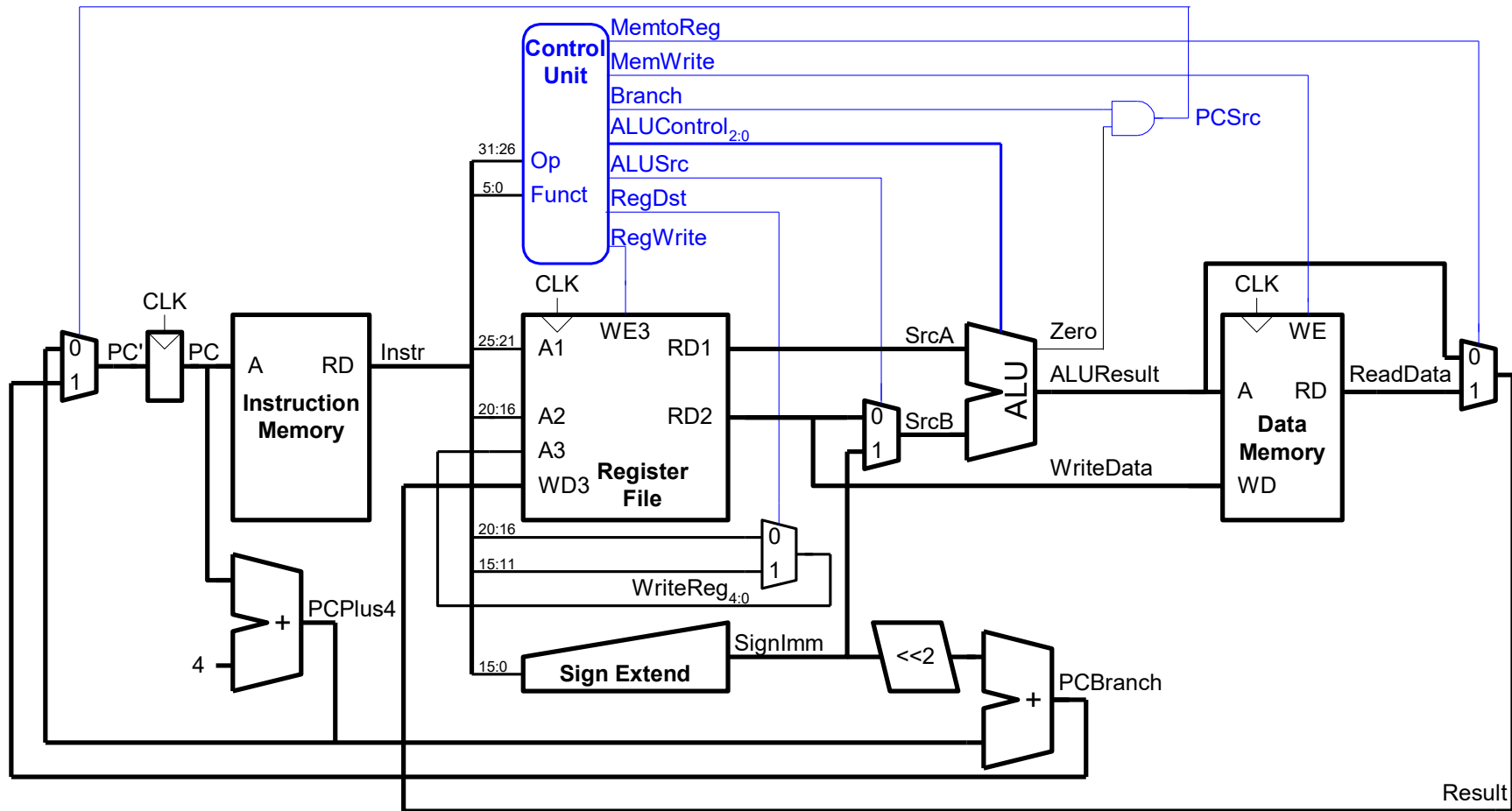

Single-Cycle Control

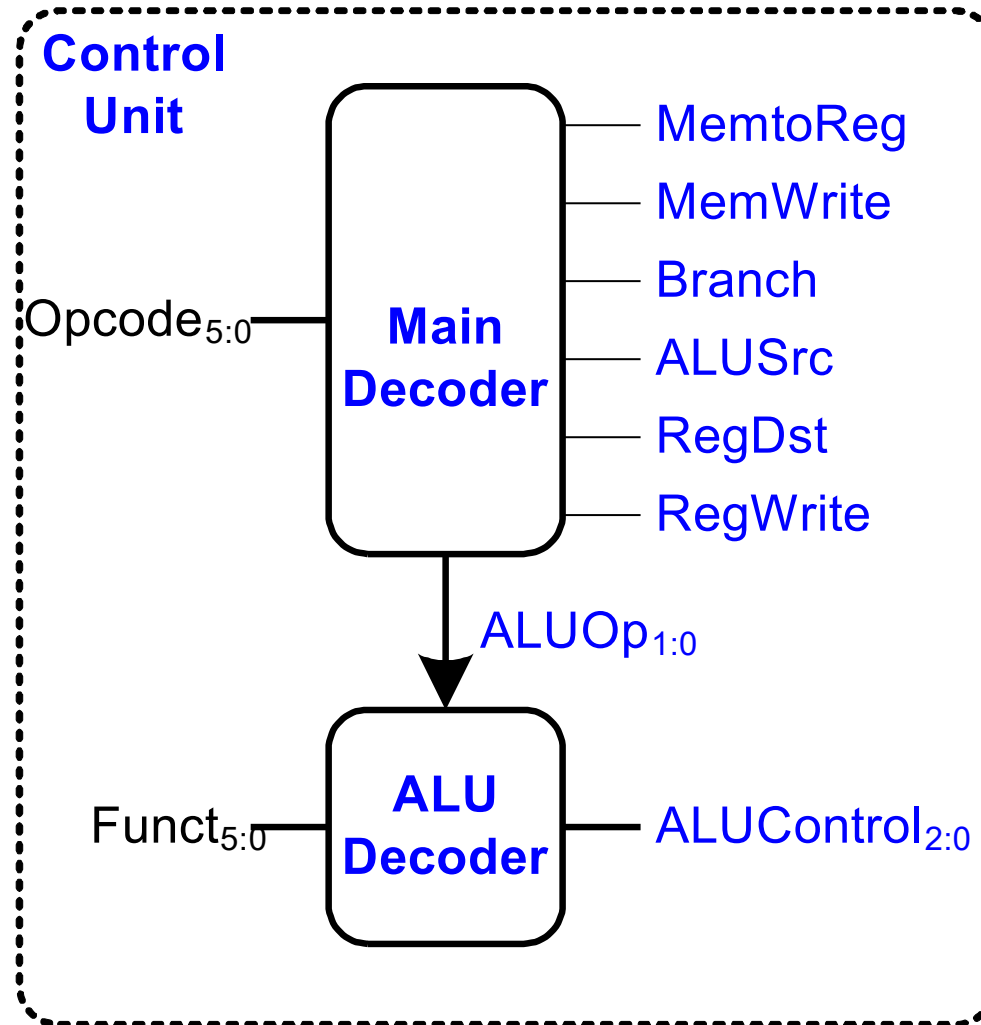


Review: ALU

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

Review: ALU

 

$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT


Control Unit: ALU Decoder

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

R-Type




ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

 

Control Unit Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000							
lw	100011							
sw	101011							
beq	000100							

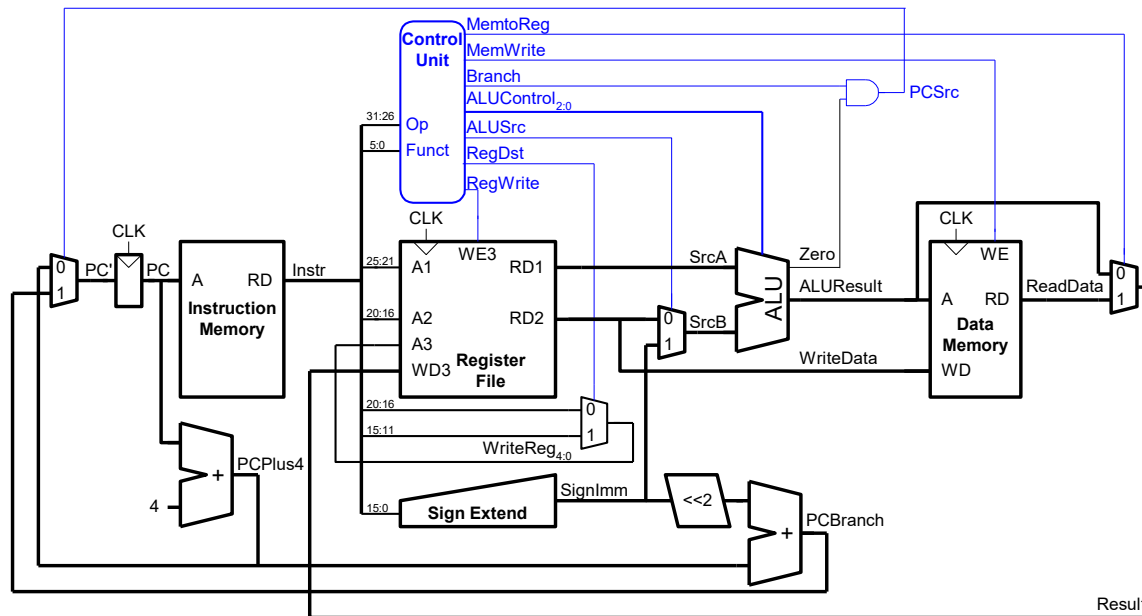


ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used



Control Unit: Main Decoder


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

 

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used



Single-Cycle Datapath: or

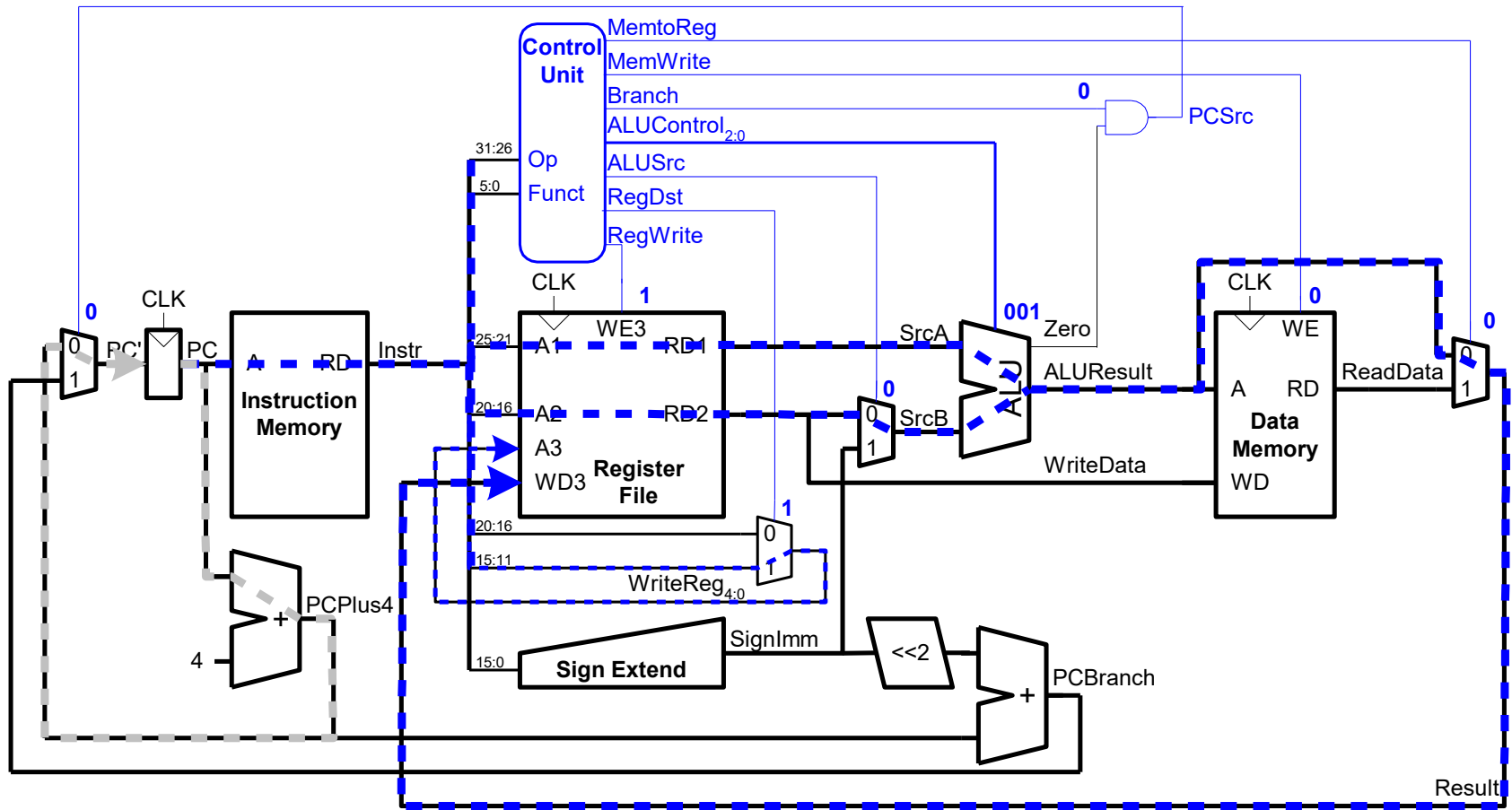

R-Type


op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

F _{2:0}	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & ~B
101	A ~B
110	A - B
111	SLT



ELSEVIER

Extended Functionality: addi

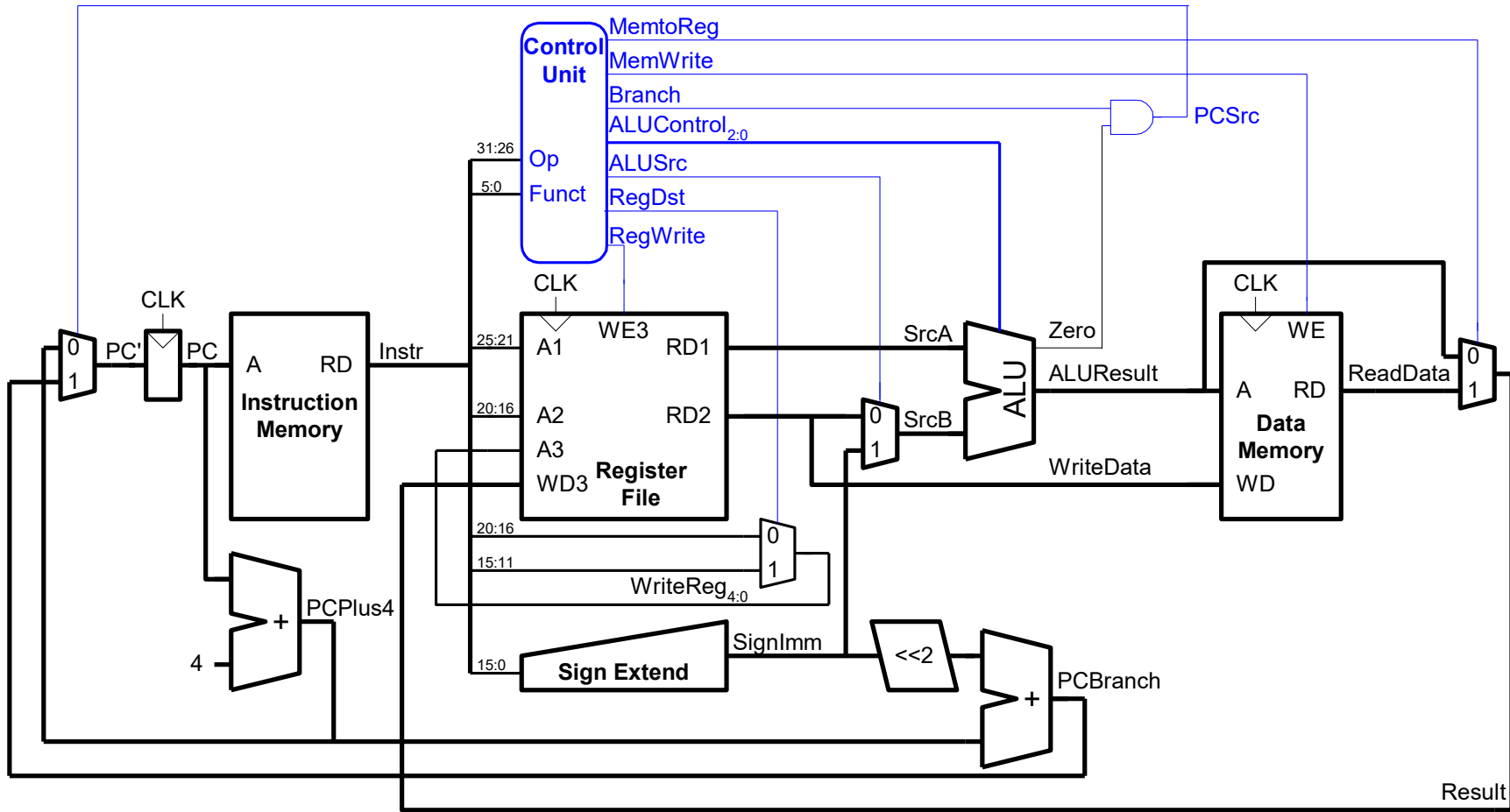


No change to datapath



Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
addi	001000	1	0	1	0	0	0	00


addi rt, rs, imm

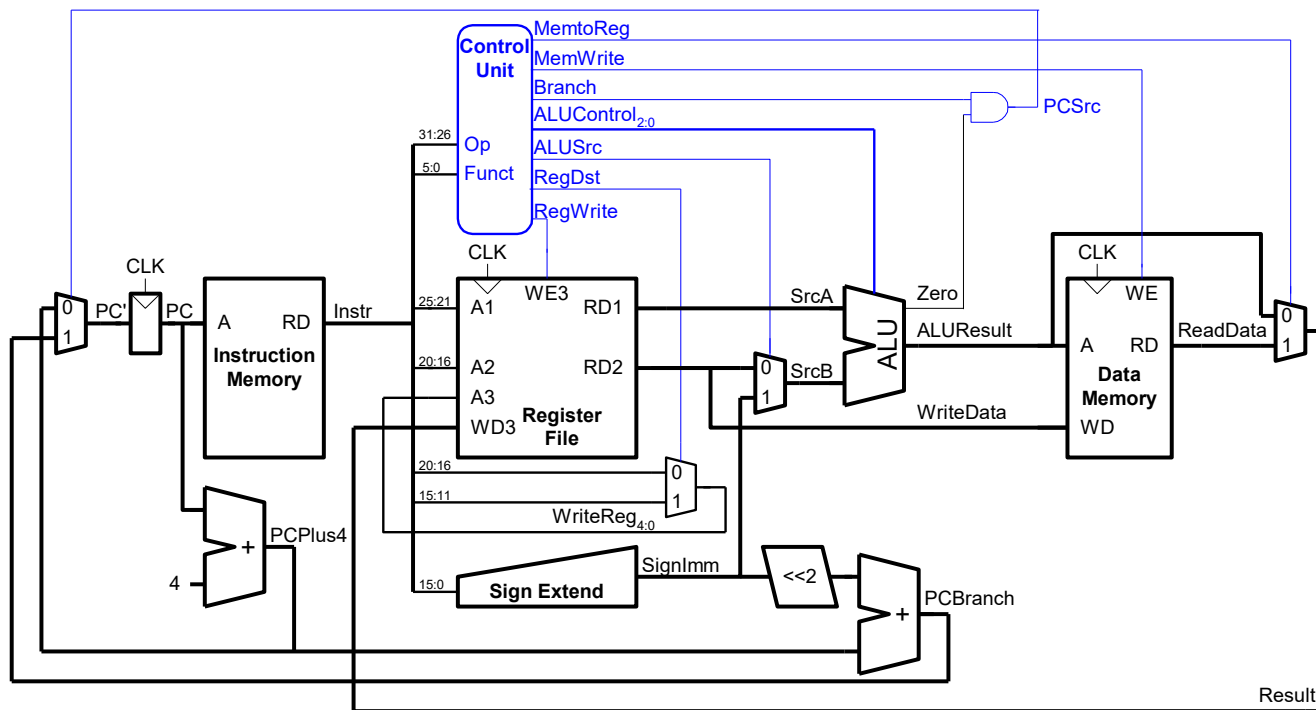


Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00

Extended Functionality: j

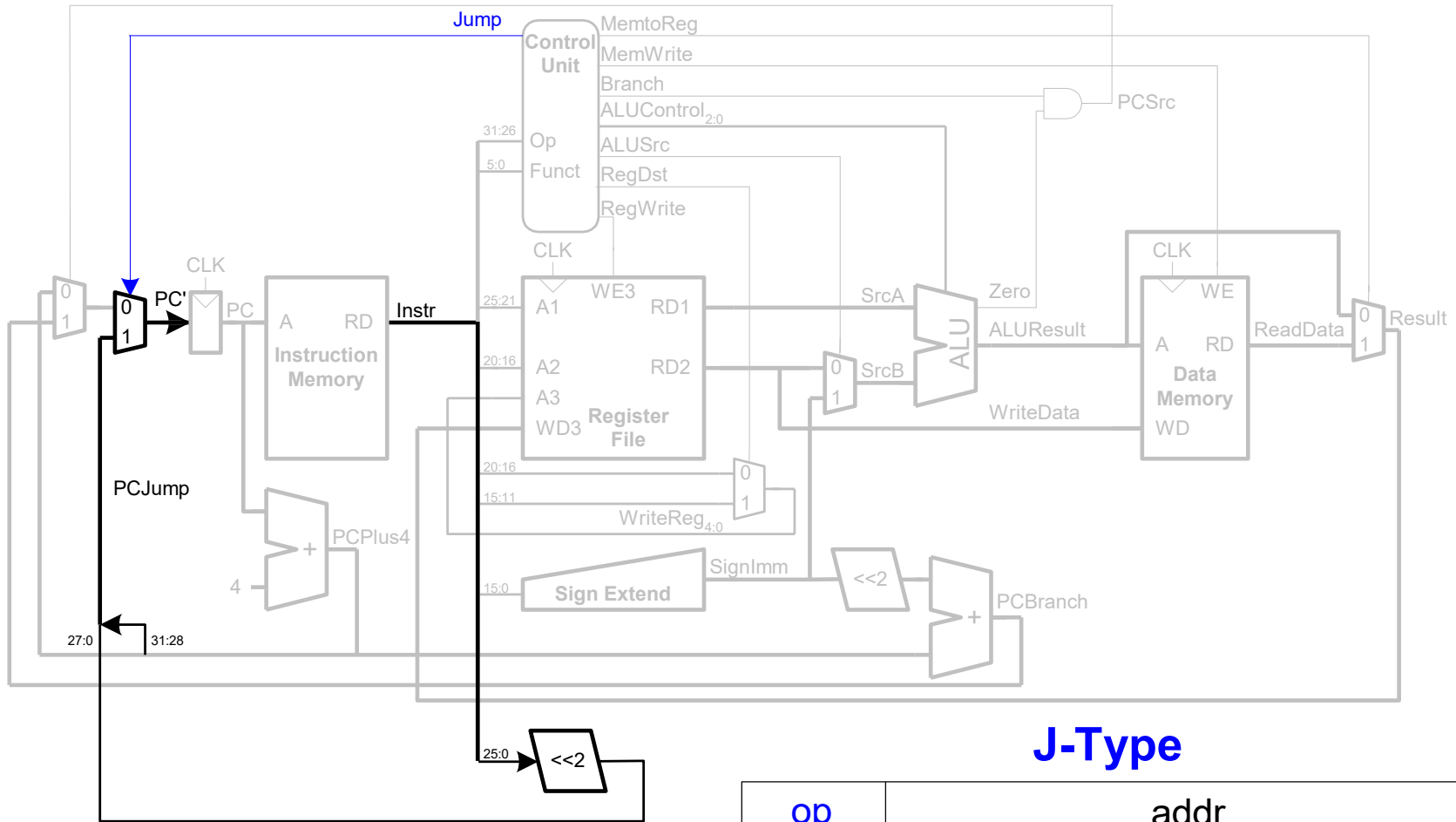

J-Type

 

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000010								

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000010	0	X	X	X	0	X	XX	1