



Assignment no 03: Chapter 4

Note: You can check the exercises after the book Chapter. In our assignment, we are using the 11th edition of “Digital Fundamentals” By Thomas L. Floyd”

8. Identify the Boolean rule(s) on which each of the following equalities is based:

- | | |
|--|---|
| (a) $\overline{\overline{AB} + \overline{CD} + \overline{EF}} = AB + CD + \overline{EF}$ | (b) $A\overline{A}B + AB\overline{C} + AB\overline{B} = AB\overline{C}$ |
| (c) $A(BC + \overline{BC}) + AC = A(BC) + AC$ | (d) $AB(C + \overline{C}) + AC = AB + AC$ |
| (e) $\overline{A}B + \overline{A}BC = \overline{A}B$ | (f) $ABC + \overline{A}B + \overline{A}BCD = ABC + \overline{A}B + D$ |

10. Apply DeMorgan’s theorems to each expression:

- | | |
|---|---|
| (a) $\overline{\overline{AB}(C + \overline{D})}$ | (b) $\overline{AB(CD + EF)}$ |
| (c) $\overline{(A + \overline{B} + C + \overline{D}) + \overline{ABCD}}$ | (d) $\overline{(\overline{A} + B + C + D)(\overline{A}\overline{B}\overline{C}\overline{D})}$ |
| (e) $\overline{\overline{AB}(CD + \overline{EF})(\overline{AB} + \overline{CD})}$ | |

13. Write the Boolean expression for each of the logic circuits in Figure 4–57.

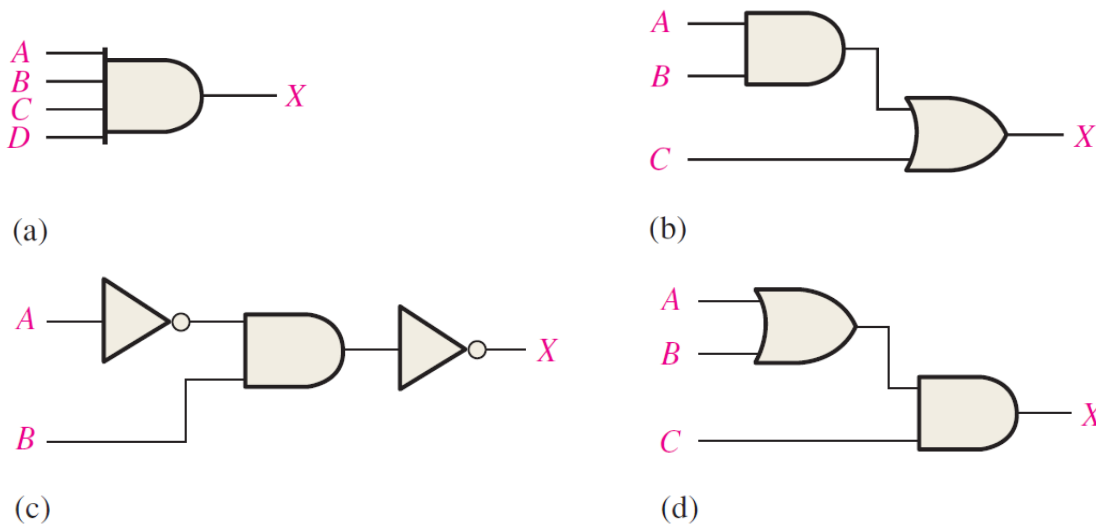



Figure 4–57

14. Draw the logic circuit represented by each of the following expressions:


- | | |
|---------------------|---------------|
| (a) $A + B + C + D$ | (b) $ABCD$ |
| (c) $A + BC$ | (d) $ABC + D$ |



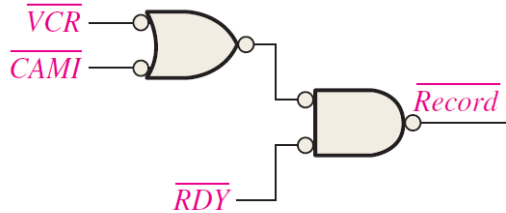17. Develop the truth table for each of the circuits in Figure 4–58.



(a)

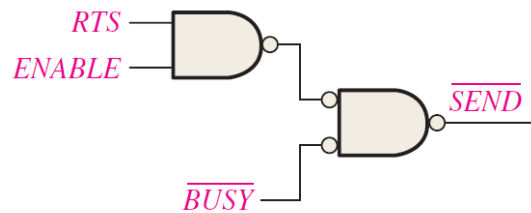

(b)

Figure 4–58

18. Construct a truth table for each of the following Boolean expressions:

(a) $A + B + C$

(b) ABC

(c) $AB + BC + CA$

(d) $(A + B)(B + C)(C + A)$

(e) $A\bar{B} + B\bar{C} + C\bar{A}$

20. Using Boolean algebra, simplify the following expressions:

(a) $(\bar{A} + B)(A + C)$


(b) $A\bar{B} + A\bar{B}C + A\bar{B}CD + A\bar{B}CDE$

(c) $BC + \overline{BCD} + B$


(d) $(B + \bar{B})(BC + BCD)$

(e) $BC + (\bar{B} + \bar{C})D + BC$

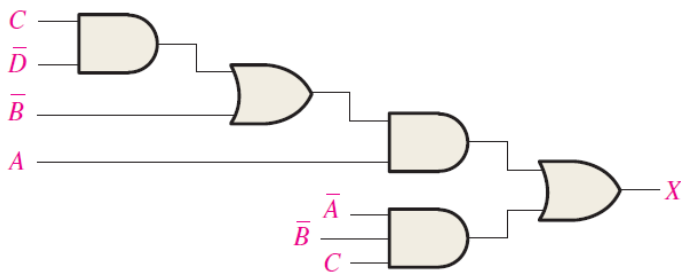
22. Determine which of the logic circuits in Figure 4–59 are equivalent.




(a)

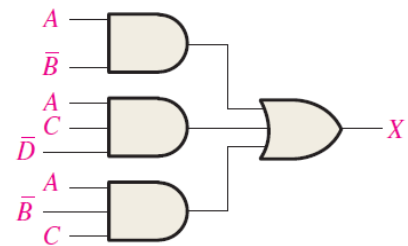

(b)

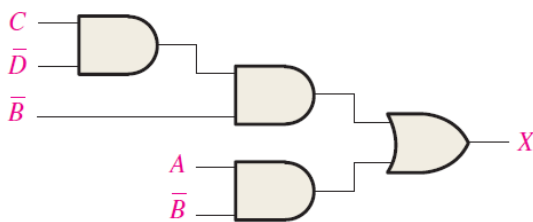

(c)

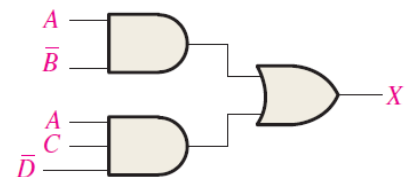

(d)

Figure 4–59



40. Use a Karnaugh map to **find** the minimum SOP form for each expression:

(a) $\overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C}$

(b) $AC(\overline{B} + C)$

(c) $\overline{A}(BC + \overline{B}\overline{C}) + A(\overline{B}C + B\overline{C})$

(d) $\overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C}$

44. Use a Karnaugh map to **reduce** each expression to a minimum SOP form:

(a) $A + B\overline{C} + CD$

(b) $\overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + ABCD + ABC\overline{D}$

(c) $\overline{A}B(\overline{C}\overline{D} + \overline{C}D) + AB(\overline{C}\overline{D} + \overline{C}D) + \overline{A}\overline{B}\overline{C}\overline{D}$

(d) $(\overline{A}\overline{B} + A\overline{B})(CD + \overline{C}\overline{D})$

(e) $\overline{A}\overline{B} + A\overline{B} + \overline{C}\overline{D} + C\overline{D}$

46. Use the Karnaugh map method to **implement** the minimum SOP expression for the logic function specified in truth Table 4–17.

TABLE 4–17

Inputs				Output
A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1



48. Use a Karnaugh map to **find** the minimum POS for each expression:

(a) $(A + B + C)(\bar{A} + \bar{B} + \bar{C})(A + \bar{B} + C)$

(b) $(X + \bar{Y})(\bar{X} + Z)(X + \bar{Y} + \bar{Z})(\bar{X} + \bar{Y} + Z)$

(c) $A(B + \bar{C})(\bar{A} + C)(A + \bar{B} + C)(\bar{A} + B + \bar{C})$

52. **Convert** each of the following POS expressions to minimum SOP expressions using a Karnaugh map:

(a) $(A + \bar{B})(A + \bar{C})(\bar{A} + \bar{B} + C)$

(b) $(\bar{A} + B)(\bar{A} + \bar{B} + \bar{C})(B + \bar{C} + D)(A + \bar{B} + C + \bar{D})$

54. **List** the minterms in the expression

$$X = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}BCD + A\bar{B}CD$$