



Assignment no 7: Chapter 7

Note: You can check the exercises after the book Chapter. In our assignment, we are using the 11th edition of “Digital Fundamentals” By Thomas L. Floyd”

2. Solve problem 1 for the input waveforms in Figure 7–71 applied to an active-LOW \bar{S} – \bar{R} latch.

 


FIGURE 7-71

4. For a gate \bar{S} – \bar{R} latch, **Determine** the Q and \bar{Q} outputs for the inputs in Figure 7–73. **Show** them in proper relation to the enable input. Assume the Q starts LOW.

 


FIGURE 7-73

6. **Determine** the output of a gated D latch for the inputs in Figure 7–75.



FIGURE 7-75



CS221: Logic Design

8. Two edge-triggered J-K flip-flops are shown in Figure 7-77. If the inputs are as shown, Draw the Q output of each flip-flop relative to the clock, and Explain the difference between the two.

The flip-flops are initially RESET.

 


FIGURE 7-77

10. Draw the Q output relative to the clock for a D flip-flop with the inputs as shown in Figure 7-79. Assume positive edge-triggering and Q initially LOW.

 


FIGURE 7-79

12. for a positive edge-triggered D flip-flop with the input as shown in Figure 7-81. Determine the Q output relative to the clock. Assume that Q starts LOW.

 


FIGURE 7-81



14. Determine the Q waveform relative to the clock if the signals shown in Figure 7-83 are applied to the inputs of the J-K flip-flop. Assume that Q is initially LOW.

 


FIGURE 7-83