

CS221: Logic Design

Instructors:

Dr. Ahmed Shalaby <http://bu.edu.eg/staff/ahmedshalaby14#>

Dr. Fatma Sakr

Digital Fundamentals


CHAPTER 3 Logic Gates

Logic Gates

- **Inverter Gate**
- **AND Gate**
- **NAND Gate**
- **OR Gate**
- **NOR Gate**
- **Exclusive-OR Gate**
- **Exclusive-NOR Gate**

Logic Gates – Inverter

The Inverter

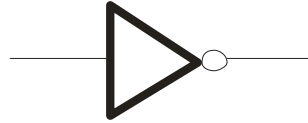


The inverter performs the Boolean **NOT** operation. When the input is LOW, the output is HIGH; when the input is HIGH, the output is LOW.

Input	Output
A	X
LOW (0)	HIGH (1)
HIGH (1)	LOW(0)


The **NOT** operation (complement) is shown with an overbar. Thus, the Boolean expression for an inverter is $X = \overline{A}$.

Logic Gates – Inverter


The Inverter

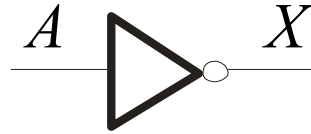

Example waveforms:

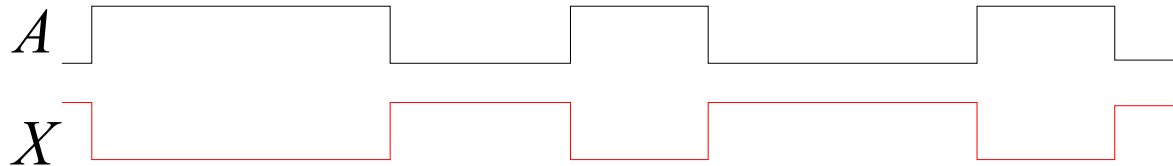


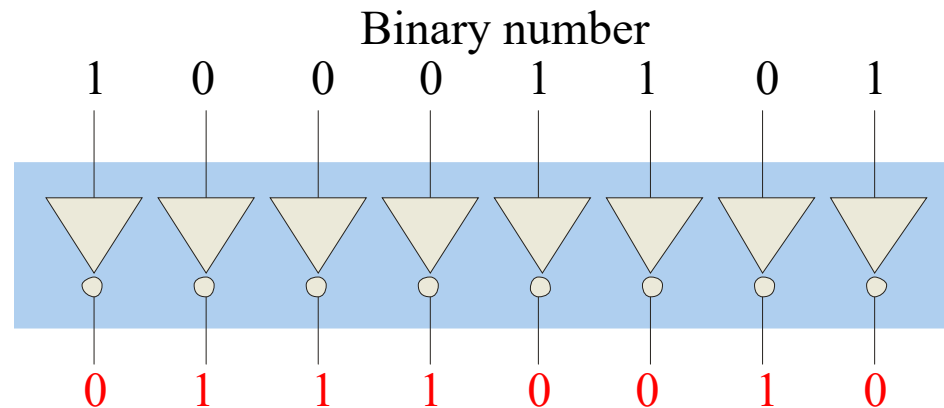A group of inverters can be used to form the 1's complement of a binary number:




CMOS Transistor Function


nMOS

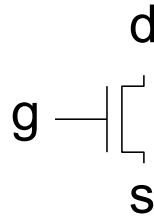




$g = 0$

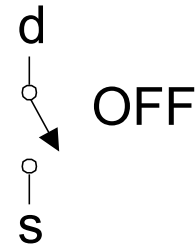

$g = 1$

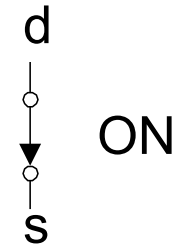


pMOS

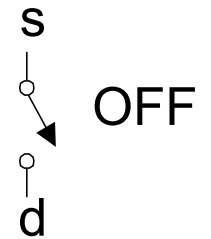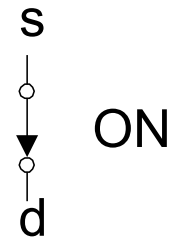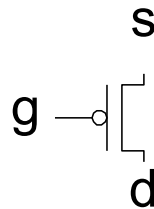

CMOS Gates – Inverter


NOT

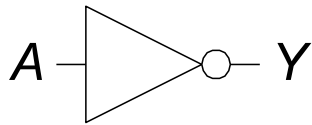

$$Y = \overline{A}$$



A	Y
0	1
1	0

A	P1	N1	Y
0	ON	OFF	1
1	OFF	ON	0

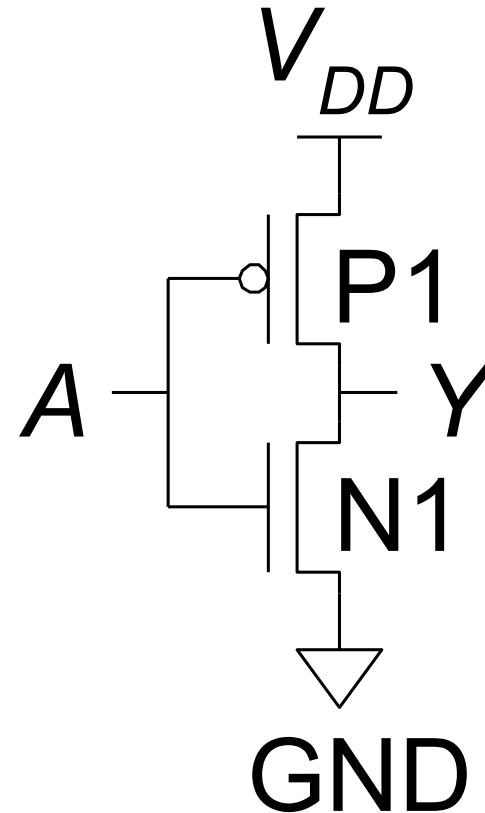

Logic Gates – AND

The AND Gate

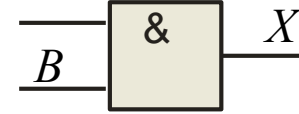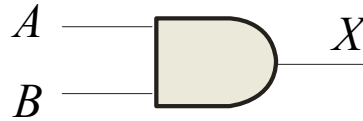



The **AND** gate produces a HIGH output when all inputs are HIGH; otherwise, the output is LOW. For a 2-input gate, the truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1


The **AND** operation is usually shown with a dot between the variables but it may be implied (no dot). Thus, the AND operation is written as $X = A \cdot B$ or $X = AB$.

Logic Gates – AND

The AND Gate

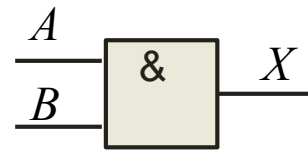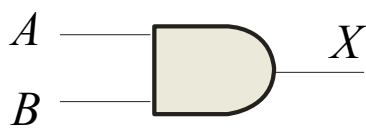

Example waveforms:


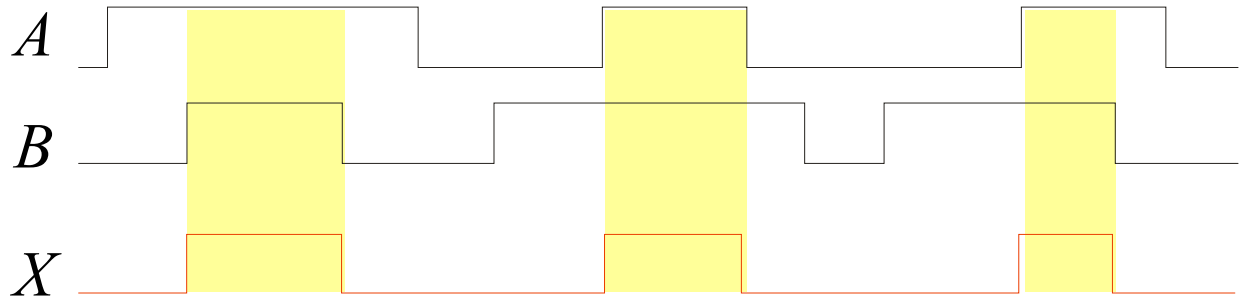


The AND operation is used in computer programming as a selective mask. If you want to retain certain bits of a binary number but reset the other bits to 0, you could set a mask with 1's in the position of the retained bits.

Example If the binary number 10100011 is ANDed with the mask 00001111, what is the result? **00000011**

Logic Gates – NAND

The NAND Gate

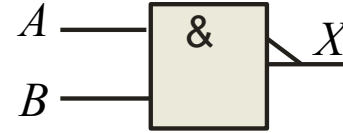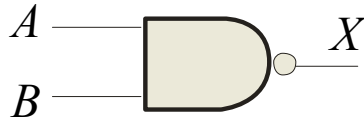



The **NAND** gate produces a LOW output when all inputs are HIGH; otherwise, the output is HIGH. For a 2-input gate, the truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0


The **NAND** operation is shown with a dot between the variables and an overbar covering them. Thus, the **NAND** operation is written as $X = \overline{A \cdot B}$ (Alternatively, $X = \overline{AB}$.)

Logic Gates – NAND

The NAND Gate

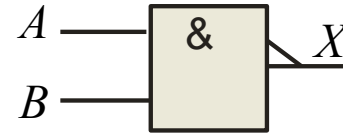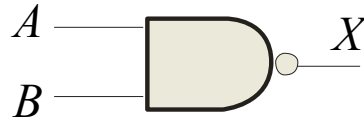


Example waveforms:

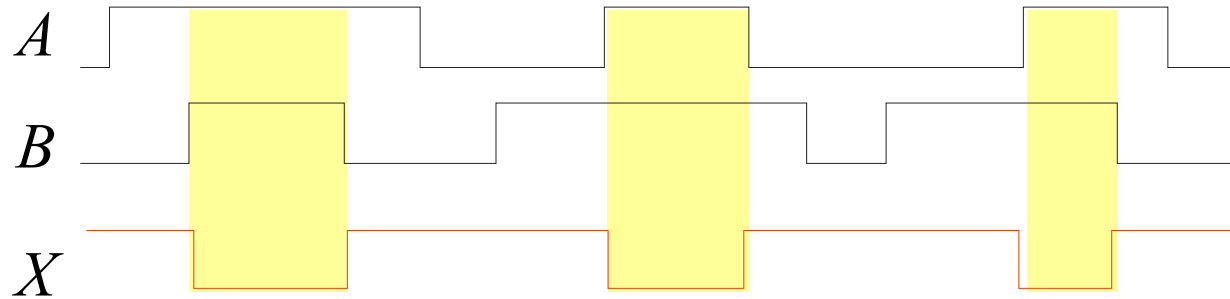

The NAND gate is particularly useful because it is a “universal” gate – all other basic gates can be constructed from NAND gates.


Logic Gates – NAND

NAND

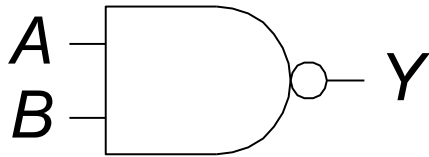



$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

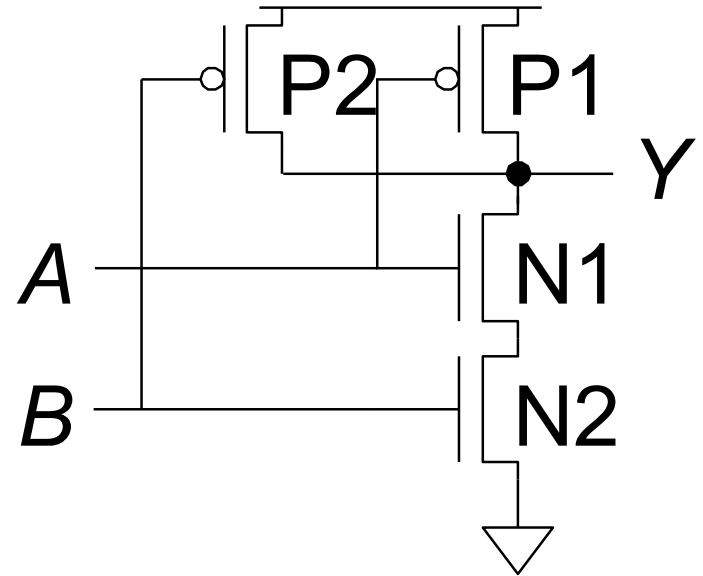



A	B	P1	P2	N1	N2	Y
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0

Logic Gates – AND

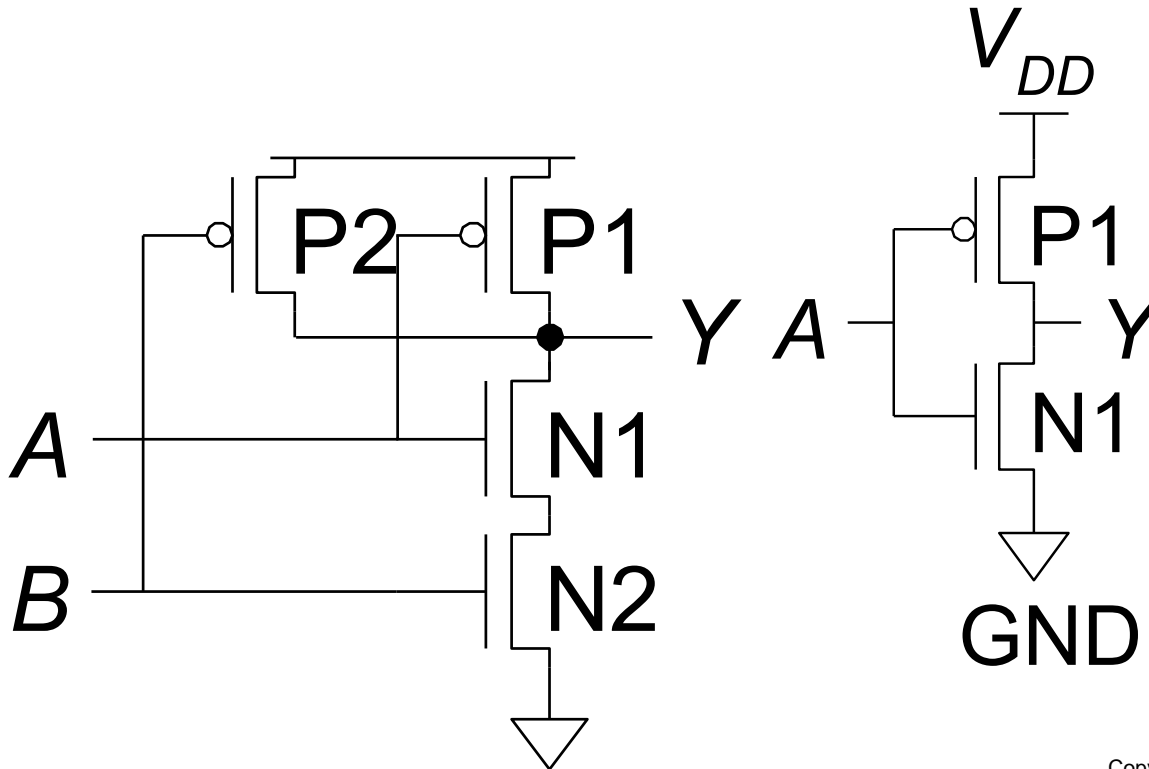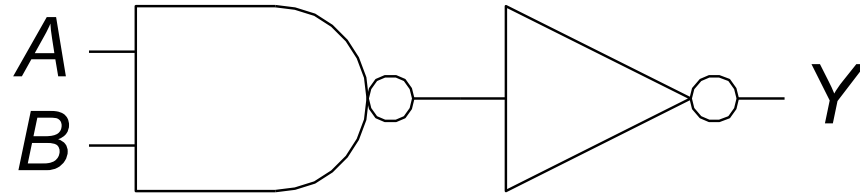

Logic Gates – OR

The OR Gate

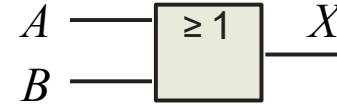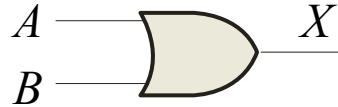



The **OR gate** produces a HIGH output if any input is HIGH; if all inputs are LOW, the output is LOW. For a 2-input gate, the truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	1


The **OR** operation is shown with a plus sign (+) between the variables. Thus, the OR operation is written as $X = A + B$.

Logic Gates – OR

The OR Gate

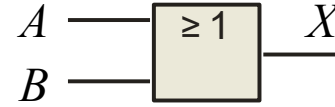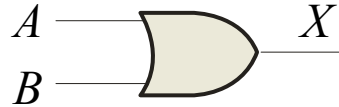

Example waveforms:

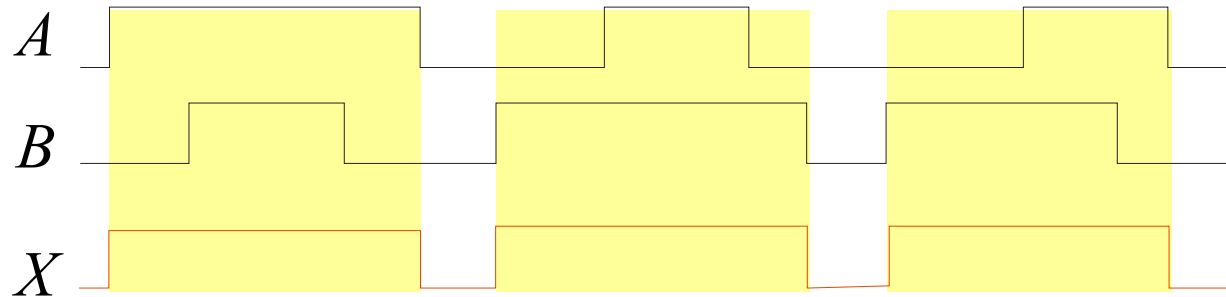



The OR operation can be used in computer programming to set certain bits of a binary number to 1.

Example ASCII letters have a 1 in the bit 5 position for lower case letters and a 0 in this position for capitals. (Bit positions are numbered from right to left starting with 0.) What will be the result if you OR an ASCII letter with the 8-bit mask 00100000?

Solution The resulting letter will be lower case.

Logic Gates – NOR

The NOR Gate

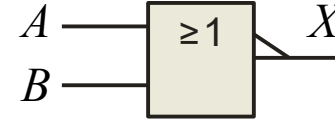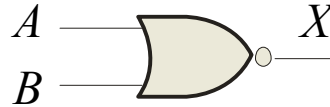



The **NOR** gate produces a LOW output if any input is HIGH; if all inputs are HIGH, the output is LOW. For a 2-input gate, the truth table is

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0


The **NOR** operation is shown with a plus sign (+) between the variables and an overbar covering them. Thus, the NOR operation is written as $X = \overline{A + B}$.

Logic Gates – NOR

The NOR Gate

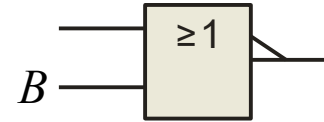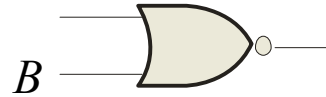


Example waveforms:

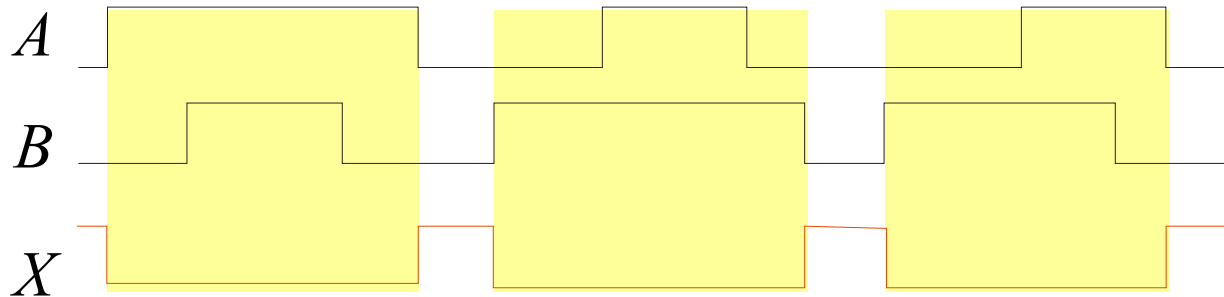

The NOR operation will produce a LOW if any input is HIGH.

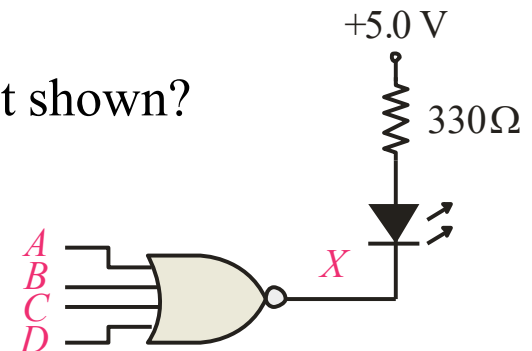Example When is the LED is ON for the circuit shown?


Solution The LED will be on when any of the four inputs are HIGH.



QUIZ

Question How do you build a two-input NOR gate?

NOR

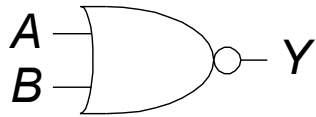



$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

A	B	P1	P2	N1	N2	Y
0	0					
0	1					
1	0					
1	1					

Logic Gates – XOR

The XOR Gate

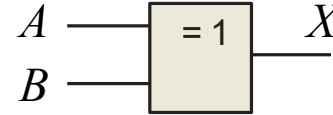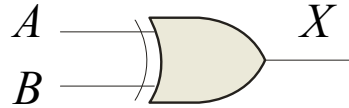

The **XOR** gate produces a HIGH output only when both inputs are at opposite logic levels. The truth table is



Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0

The **XOR** operation is written as $X = \bar{A}B + A\bar{B}$.


Alternatively, it can be written with a circled plus sign between the variables as $X = A \oplus B$.

Logic Gates – XOR

The XOR Gate

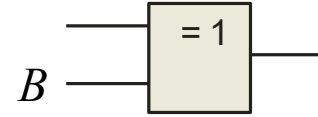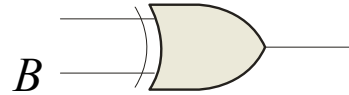

Example waveforms:

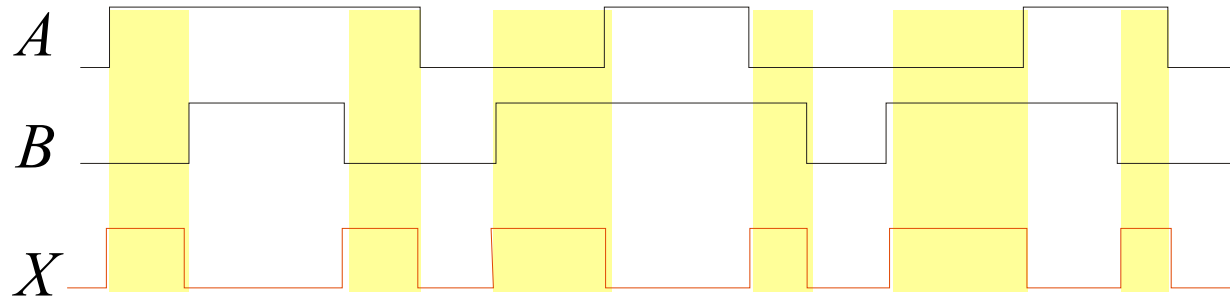



Notice that the XOR gate will produce a HIGH only when exactly one input is HIGH.

Question If the A and B waveforms are both inverted for the above waveforms, how is the output affected?

There is no change in the output.

Logic Gates – XNOR

The XNOR Gate

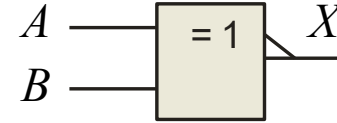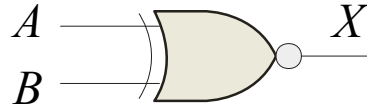



The **XNOR** gate produces a HIGH output only when both inputs are at the same logic level. The truth table is

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1


The **XNOR** operation shown as $X = \overline{A}\overline{B} + AB$. Alternatively, the XNOR operation can be shown with a circled dot between the variables. Thus, it can be shown as $X = A \odot B$.

Logic Gates – XNOR

The XNOR Gate

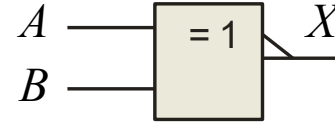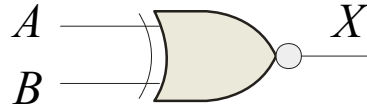

Example waveforms:

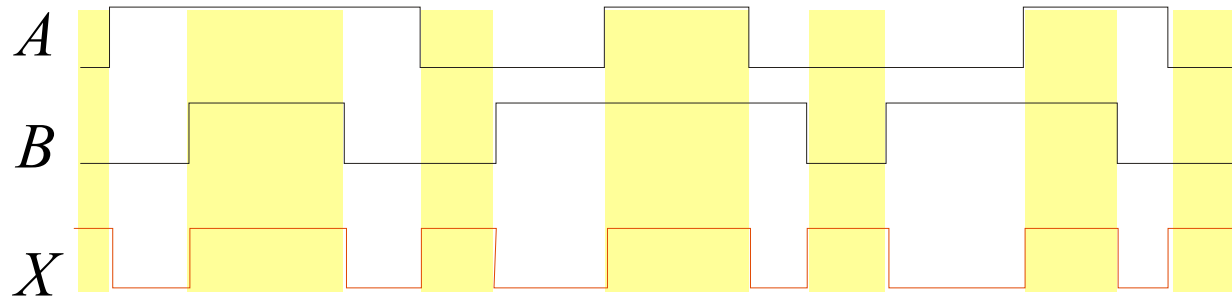

Notice that the XNOR gate will produce a HIGH when both inputs are the same. This makes it useful for comparison functions.


Question If the A waveform is inverted but B remains the same, how is the output affected?

The output will be inverted.


Logic Gates

Fixed Function Logic

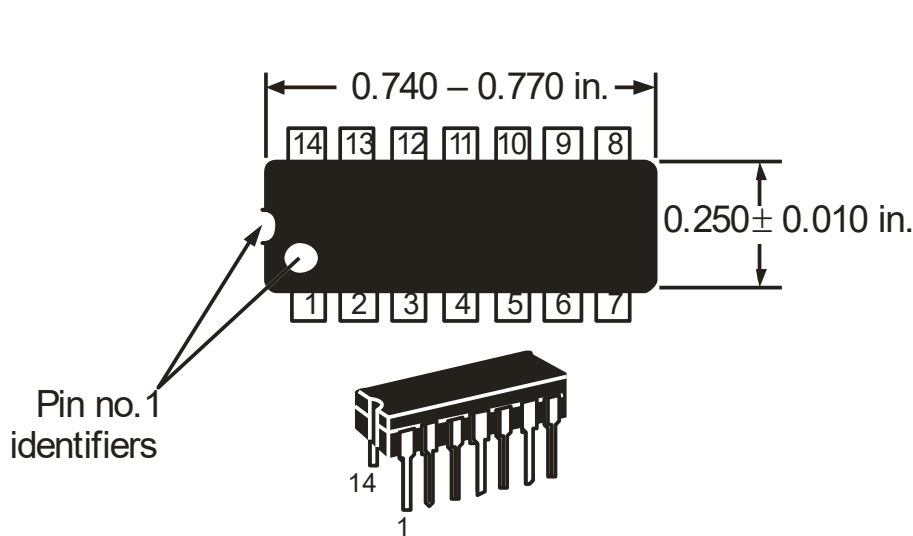Two major fixed function logic families are TTL and CMOS. A third technology is BiCMOS, which combines the first two. Packaging for fixed function logic is shown.



DIP package

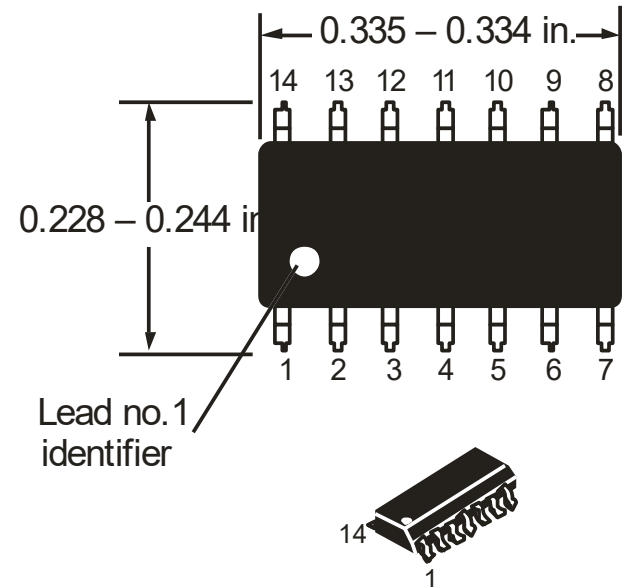


SOIC package


Logic Gates

Fixed Function Logic

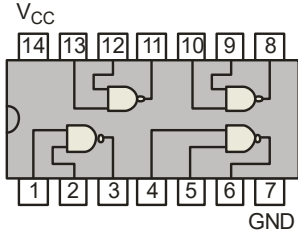
Some common gate configurations are shown.




'00

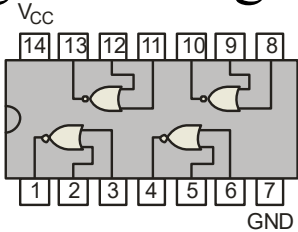


'02

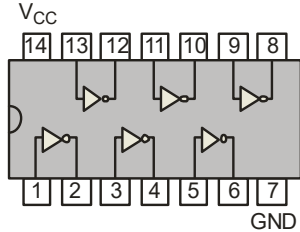


'04

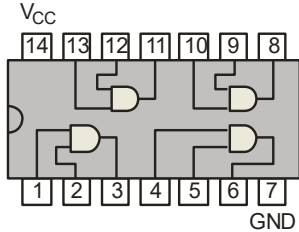


'08

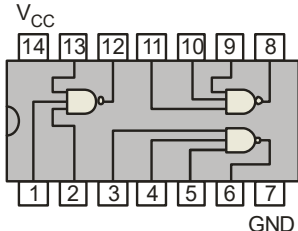


'10

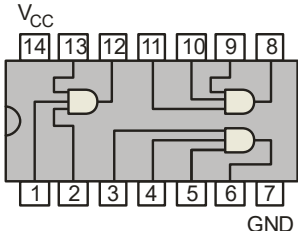


'11

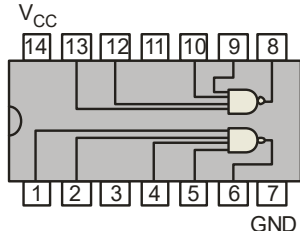


'20

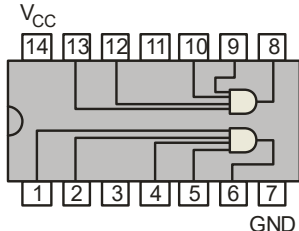


'21

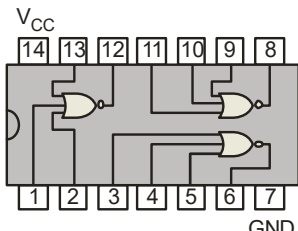


'27

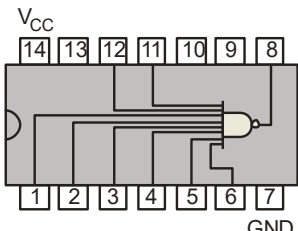

'30

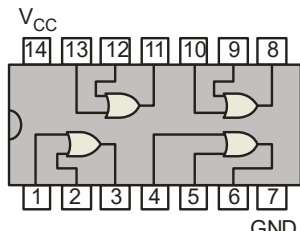

'32


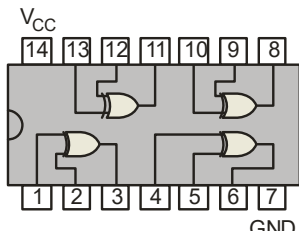


'86

Logic Gates

Fixed Function Logic

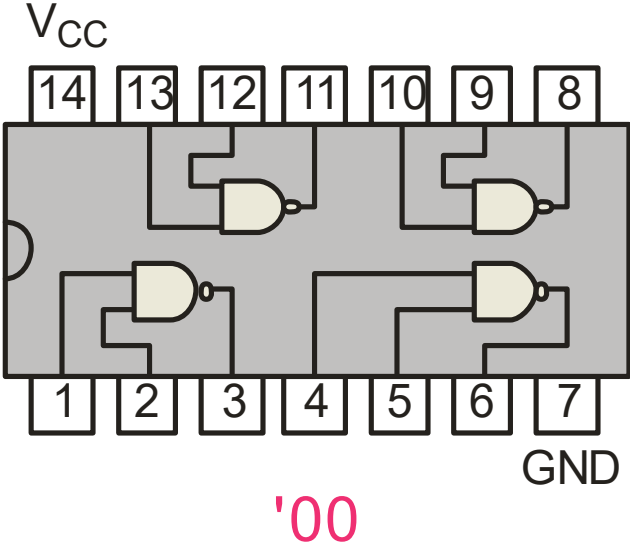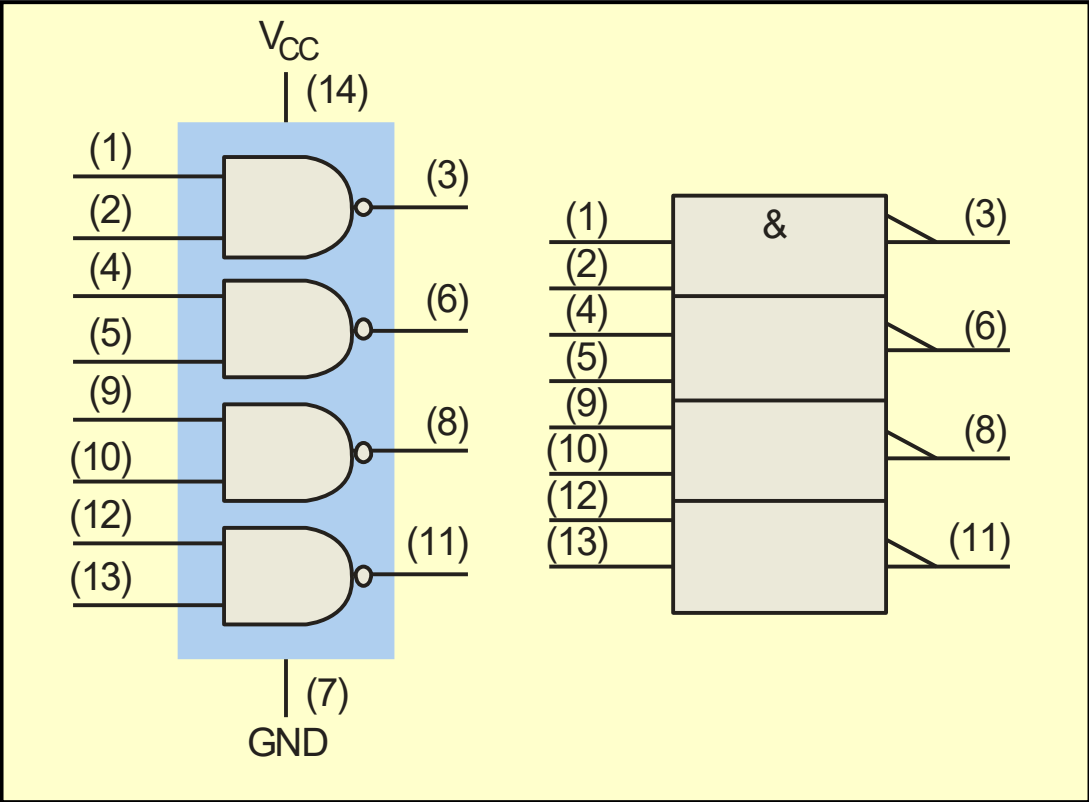Logic symbols show the gates and associated pin numbers.



Logic Gates

Fixed Function Logic

Data sheets include limits and conditions set by the manufacturer as well as DC and AC characteristics. For example, some maximum ratings for a 74HC00A are:


MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
V_{CC}	DC Supply Voltage (Referenced to GND)	-0.5 to + 7.0 V	V
V_{in}	DC Input Voltage (Referenced to GND)	-0.5 to V_{CC} +0.5 V	V
V_{out}	DC Output Voltage (Referenced to GND)	- 0.5 to V_{CC} +0.5 V	V
I_{in}	DC Input Current, per pin	± 20	mA
I_{out}	DC Output Current, per pin	± 25	mA
I_{CC}	DC Supply Current, V_{CC} and GND pins	± 50	mA
P_D	Power Dissipation in Still Air, Plastic or Ceramic DIP † SOIC Package † TSSOP Package †	750 500 450	mW
T_{stg}	Storage Temperature	-65 to + 150	°C
T_L	Lead Temperature, 1 mm from Case for 10 Seconds Plastic DIP, SOIC, or TSSOP Package Ceramic DIP	260 300	°C

Logic Gates - Programmable Logic

Programmable Logic

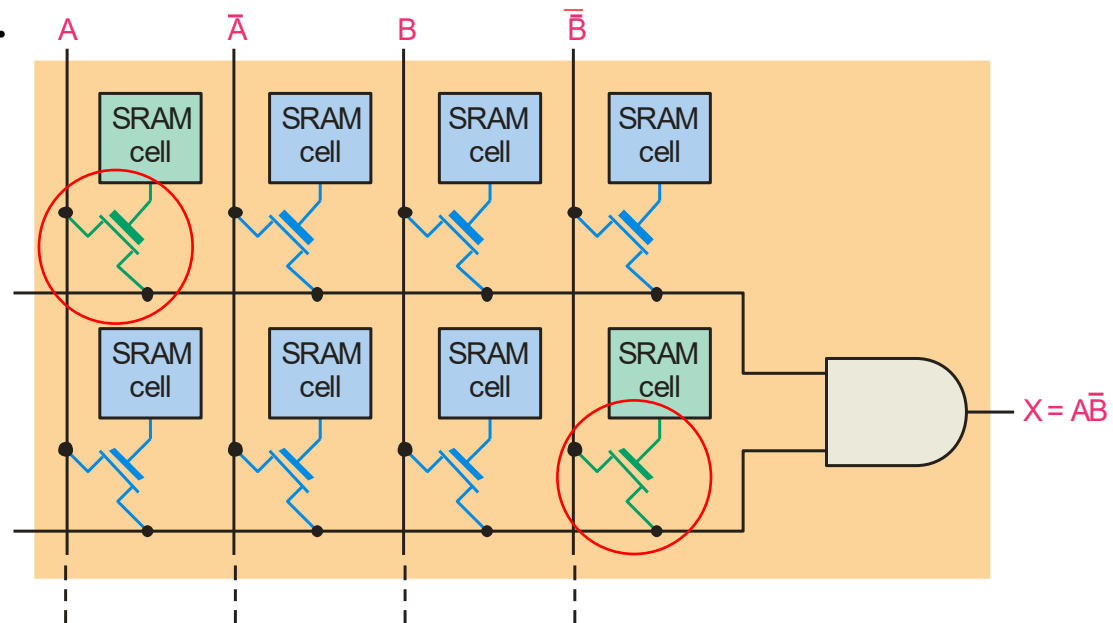A Programmable Logic Device (PLD) can be programmed to implement logic. There are various technologies available for PLDs. Many use an internal array of AND gates to form logic terms. Many PLDs can be programmed multiple times.



Logic Gates - Programmable Logic

Programmable Logic

In general, the required logic for a PLD is developed with the aid of a computer. The logic can be entered using a Hardware Description Language (HDL) such as VHDL. Logic can be specified to the HDL as a text file, a schematic diagram, or a state diagram.

Example A text entry for programming a PLD in VHDL as a 2-input NAND gate is shown for reference in the following slide. In this case, the inputs and outputs are first specified. Then the signals are described. Although you are probably not familiar with VHDL, you can see that the program is simple to read.


Logic Gates - Programmable Logic

Programmable Logic

```
entity NandGate is  
    port(A, B: in bit;  
        LED: out bit);  
end entity NandGate;  
  
architecture GateBehavior of NandGate is  
signal A, B: bit;  
begin  
    X <= A nand B;  
    LED <= X;  
end architecture GateBehavior;
```

Logic Gates


BUF

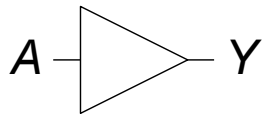

$$Y = A$$

A	Y
0	0
1	1


NOT

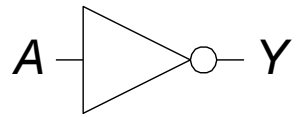

$$Y = \bar{A}$$

A	Y
0	1
1	0


AND

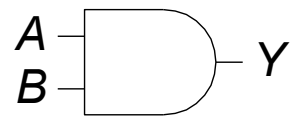

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR

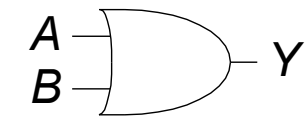


$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Logic Gates


XOR

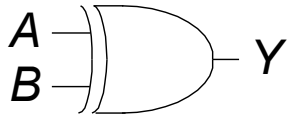

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


NAND

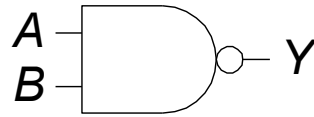

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR

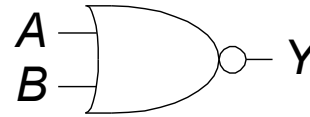

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

XNOR

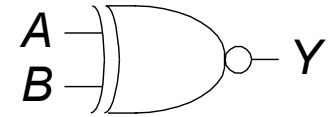


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Multiple-Input Logic Gates


NOR3

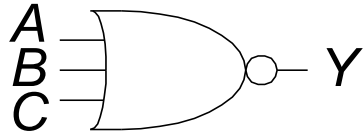

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


AND3

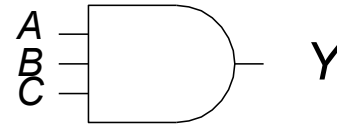

$$Y = ABC$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Logic Gates - Lab

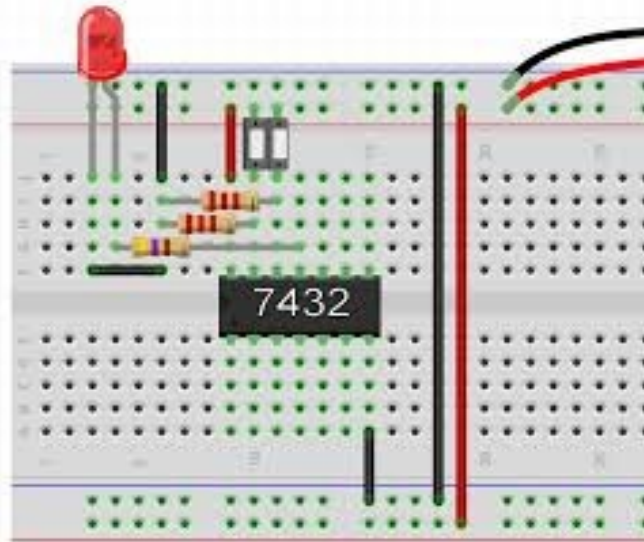

wiseGI

Logic Gates - Lab

- **Breadboard Power Supply.**
- **Power Source (Battery, PowerBank, Laptop)**
- **USB Cable (female – female)**
- **LEDs (10 units – different colors)**
- **Resistor (10 units – 330 Ohm)**
- **Jumpers – Group of wires**
- **NAND Gate(00), NOR Gate(02), NOT Gate (04)**

[Logic Design Lab](#)

Project Lab

- Breadboard
- Logic Gates