

# CS221: Logic Design

## Instructors:

Dr. Ahmed Shalaby <http://bu.edu.eg/staff/ahmedshalaby14#>

Dr. Fatma Saker

# QUIZ

As part of an aircraft's functional monitoring system, a circuit is required to indicate the status of the landing gears prior to landing.

A green LED display turns on if all three gears are properly extended when the "gear down" switch has been activated in preparation for landing. A red LED display turns on if any of the gears fail to extend properly prior to landing.

When a landing gear is extended, its sensor produces a LOW voltage. When a landing gear is retracted, its sensor produces a HIGH voltage.

**Implement a circuit to meet this requirement.**

# SOP & POS

## EXAMPLE 4-20

Develop a truth table for the standard SOP expression  $\overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$ .

TABLE 4-6

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	
0	0	1	1	$\overline{A}\overline{B}C$
0	1	0	0	
0	1	1	0	
1	0	0	1	$A\overline{B}\overline{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	$ABC$

TABLE 4-7

Inputs			Output	Sum Term
A	B	C	X	
0	0	0	0	$(A + B + C)$
0	0	1	1	
0	1	0	0	$(A + \overline{B} + C)$
0	1	1	0	$(A + \overline{B} + \overline{C})$
1	0	0	1	
1	0	1	0	$(\overline{A} + B + \overline{C})$
1	1	0	0	$(\overline{A} + \overline{B} + C)$
1	1	1	1	

## EXAMPLE 4-21

Determine the truth table for the following standard POS expression:

$$(A + B + C)(A + \overline{B} + C)(A + \overline{B} + \overline{C})(\overline{A} + B + \overline{C})(\overline{A} + \overline{B} + C)$$


# Digital Fundamentals

## CHAPTER 5 Combinational Logic Analysis

# Combinational Logic Analysis
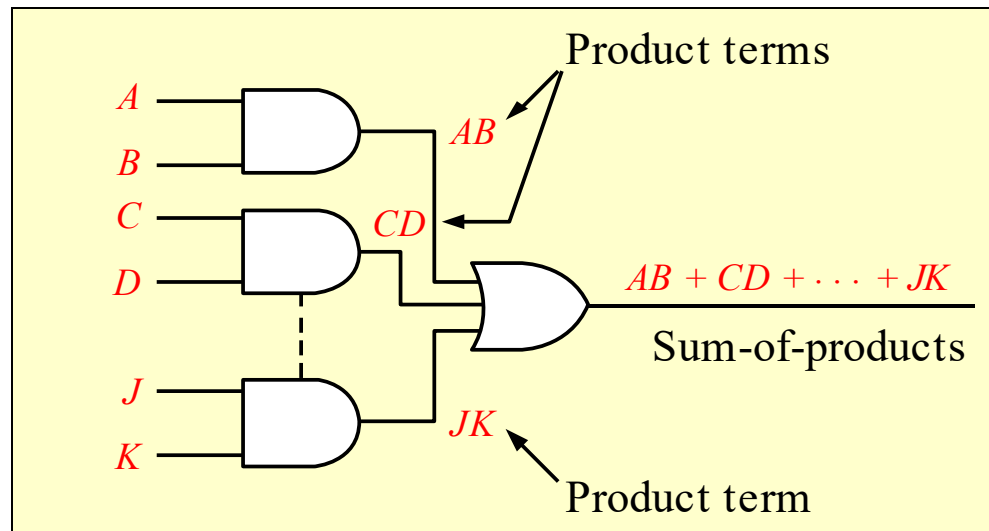
## Combinational Logic Circuits


In Sum-of-Products (SOP) form, basic combinational circuits can be directly implemented with AND-OR combinations if the necessary complement terms are available.



# Combinational Logic Analysis
 
## Combinational Logic Circuits

An example of an SOP implementation is shown. The SOP expression is an **AND-OR combination** of the input variables and the appropriate complements.




# Combinational Logic Analysis
 
## Combinational Logic Circuits

When the output of a **SOP** form is inverted, the circuit is called an **AND-OR-Invert (AOI)** circuit. The AOI configuration lends itself to product-of-sums (POS) implementation.

An example of an AOI implementation is shown. The output expression **can be changed to a POS expression** by applying DeMorgan's theorem twice.



# Combinational Logic Analysis

## Exclusive-OR Logic


The truth table for an exclusive-OR gate is

Notice that the output is HIGH whenever  $A$  and  $B$  disagree.

The Boolean expression is  $X = \bar{A}B + A\bar{B}$

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


The circuit can be drawn as

 

Symbols:



Distinctive shape

 

Rectangular outline



# Combinational Logic Analysis

## Exclusive-NOR Logic


The truth table for an exclusive-NOR gate is

Notice that the output is HIGH whenever *A* and *B* agree.


The Boolean expression is  $X = \overline{A}\overline{B} + AB$

Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1


The circuit can be drawn as

 

Symbols:

 

Distinctive shape

 


Rectangular outline

# Combinational Logic Analysis
 
## Example

For each circuit, determine if the LED should be on or off.



## Solution

Circuit (a): XOR, inputs agree, output is LOW, LED is ON.

Circuit (b): XNOR, inputs disagree, output is LOW, LED is ON.

Circuit (c): XOR, inputs disagree, output is HIGH, LED is OFF.


# Implementing Combinational Logic

## Implementing Combinational Logic

Implementing a **SOP expression** is done by first forming the AND terms; then the terms are ORed together.

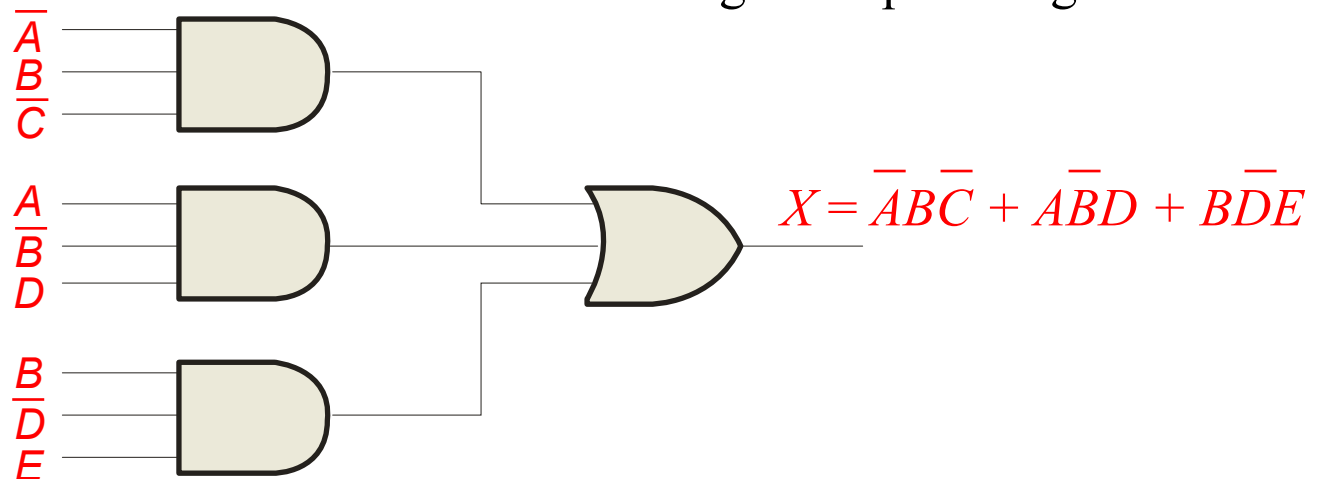**Example** Show the circuit that will implement the Boolean expression  $X = \overline{A}BC + A\overline{B}D + B\overline{D}E$ . (Assume that the variables and their complements are available.)

**Solution** Start by forming the terms using three 3-input AND gates. Then combine the three terms using a 3-input OR gate.




# Implementing Combinational Logic

## Karnaugh Map Implementation

For basic combinational logic circuits, the Karnaugh map can be read and the circuit drawn as a minimum SOP.

 **Example** A Karnaugh map is drawn from a truth table. Read the minimum SOP expression and draw the circuit.



## Solution


1. Group the 1's into two overlapping groups as indicated.
2. Read each group by eliminating any variable that changes across a boundary.
3. The vertical group is read  $\bar{A}\bar{C}$ .
4. The horizontal group is read  $\bar{A}B$ .

*The circuit is on the next slide:*

# Implementing Combinational Logic

## Solution *continued...*

Circuit:

 

The result is shown as a sum of products.

It is a **simple matter to implement this form using only NAND gates** as shown in the text and following example.

# The Universal Property of NAND and NOR Gates


**NAND and NOR gates are “universal” because they can be used to produce any of the other logic functions.**

# Combinational Logic Analysis


## Universal Gates

NAND gates are sometimes called **universal** gates because they can be used to produce the other basic Boolean functions.


Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	1
1	0	1
1	1	0

 


Inverter

 

AND gate

 

OR gate

 


NOR gate

# Combinational Logic Analysis


## Universal Gates

NOR gates are also **universal** gates and can form all of the basic gates.


Inputs		Output
$A$	$B$	$X$
0	0	1
0	1	0
1	0	0
1	1	0

 


Inverter

 

OR gate

 

AND gate

 


NAND gate





# Combinational Logic Analysis

**Solution**

*continued...Slide 12*

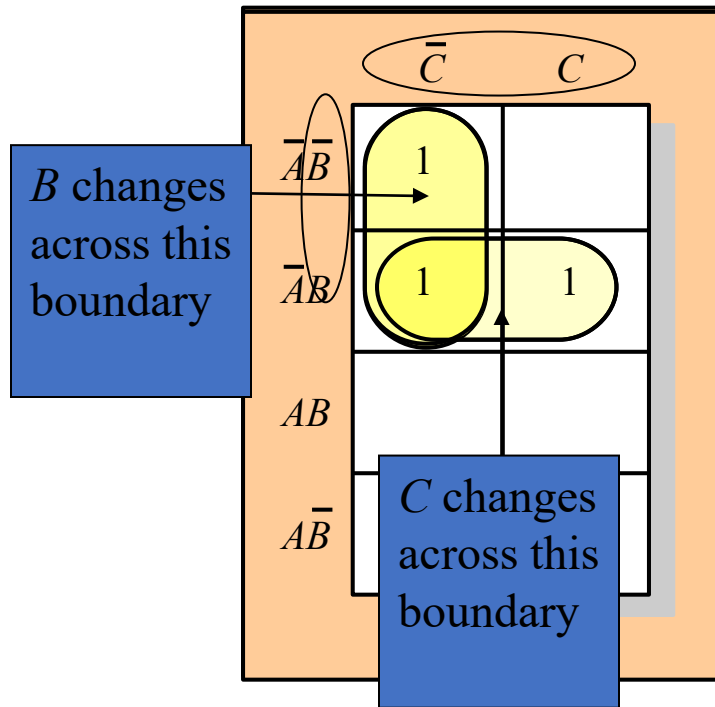

Circuit:

  


Recall from Boolean algebra **that double inversion cancels**. By adding inverting bubbles to above circuit, it is **easily converted to NAND gates**.

# Combinational Logic Analysis
 
## NAND Logic


Recall from **DeMorgan's theorem** that  $\overline{AB} = \overline{A} + \overline{B}$ .

By using equivalent symbols, it is simpler to read the logic of SOP forms. The earlier example shows the idea:



Inputs		Output	
A	B	$\overline{AB}$	$\overline{A} + \overline{B}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

 
The logic is easy to read if you (mentally) cancel the two connected bubbles on a line.



# Combinational Logic Analysis

 
## NOR Logic

Alternatively, DeMorgan's theorem can be written as  $\overline{A + B} = \overline{A} \overline{B}$ . By using equivalent symbols, it is simpler to read the logic of POS forms. For example,



Inputs		Output	
A	B	$\overline{A + B}$	$\overline{A} \overline{B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

 
Again, the logic is easy to read if you cancel the two connected bubbles on a line.



# Combinational Logic Analysis
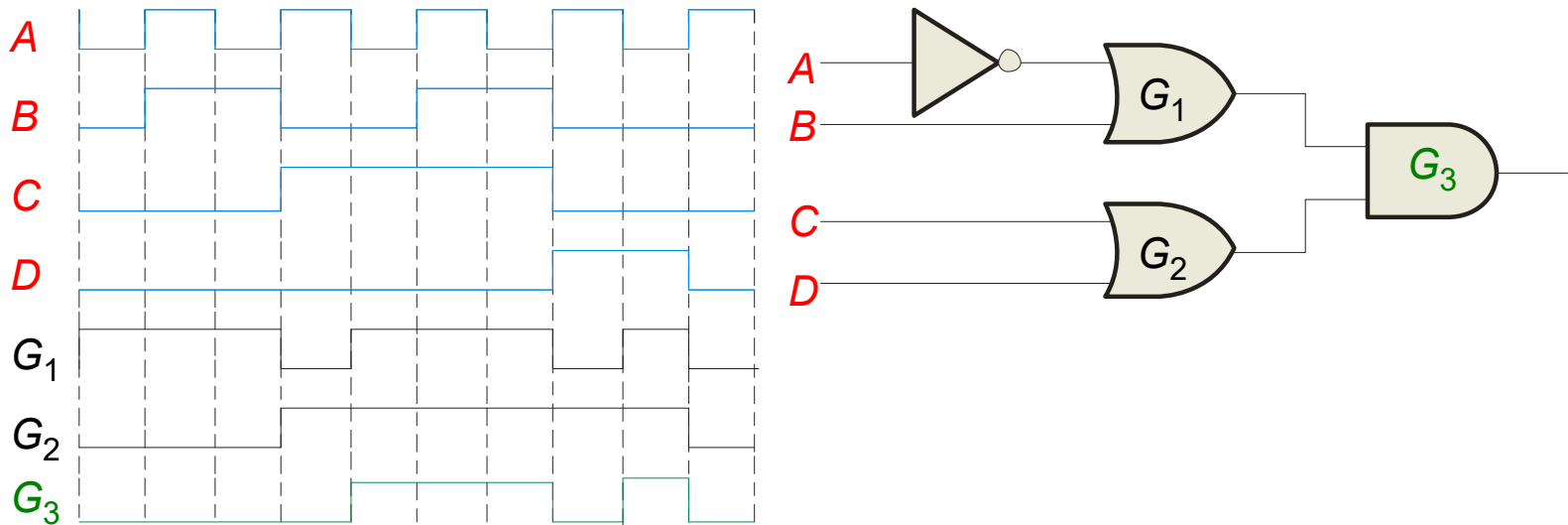
## Pulsed Waveforms


For combinational circuits with pulsed inputs, the output can be predicted **by developing intermediate outputs and combining the result**. For example, the circuit shown can be analyzed at the outputs of the OR gates:



# Combinational Logic Analysis
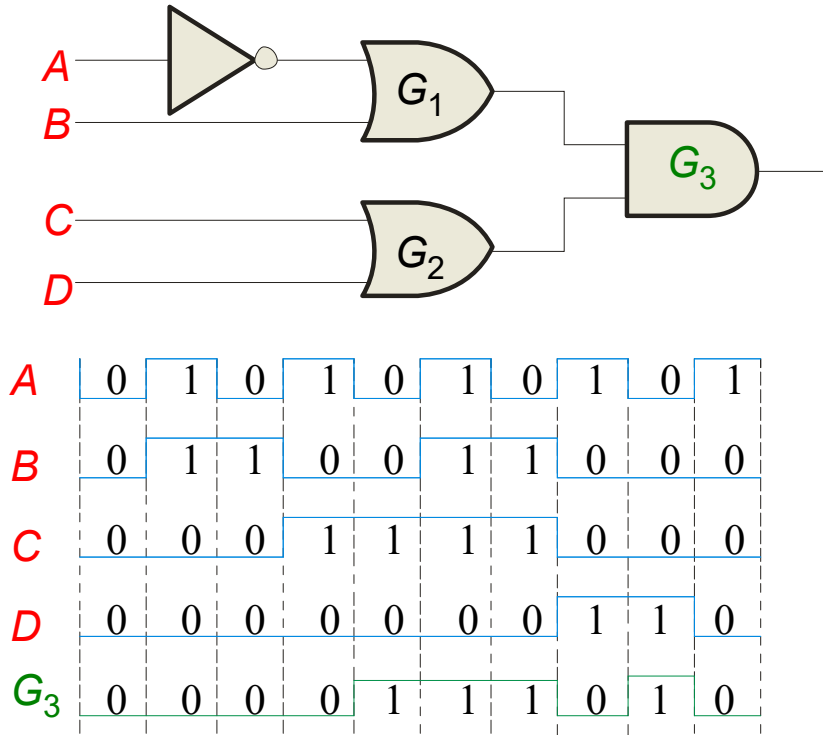
## Pulsed Waveforms

Alternatively, you can develop the truth table for the circuit and enter 0's and 1's on the waveforms. Then read the output from the table.



Inputs				Output
A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

# Combinational Logic Analysis

- Universal gate*** Either a NAND or a NOR gate. The term universal refers to a property of a gate that permits any logic function to be implemented by that gate or by a combination of gates of that kind.
- Negative-OR*** The dual operation of a NAND gate when the inputs are active-LOW.
- Negative-AND*** The dual operation of a NOR gate when the inputs are active-LOW.

# QUIZ

Analyze the Output of the shown Circuit Using timing diagram and truth tables for the input waveforms.

